

Mansi Uniyal
19EE10039.

Determination of equivalent circuit parameters of 3 phase 3 winding Transformer.

Results : Open Circuit Test :-

Primary winding $\rightarrow 1'$ (Supply)

Secondary winding $\rightarrow 2'$ {open circuit}

Tertiary winding $\rightarrow 3'$

Values wrt primary side.

$$V_{oc} = 132.8 \text{ V} \quad (\text{single phase})$$

$$P_{oc} = 134.8 \text{ W} \quad (\text{3 phase})$$

$$I_{oc} = 0.539 \text{ A} \quad (\text{single phase})$$

Calculations :-

(i) Equivalent admittance of shunt branch

$$Y = \frac{|I_{oc}|}{|V_{oc}|} = \frac{0.539}{132.8} = 4.0587 \times 10^{-3} \Omega^{-1}$$

$$Y = G_i + jB_m$$

$$G_i = \frac{P_{oc}}{\sqrt{V_{oc}^2}} = \frac{134.8/3}{132.8^2}$$

$$= 2.548 \times 10^{-3} \Omega^{-1}$$

$$B_m = \sqrt{Y^2 - G_i^2}$$

$$= 3.159 \times 10^{-3} \Omega^{-1}$$

Coreless Resistance,

$$R_i = \frac{1}{G_i} = 392.465 \Omega$$

magnetizing Resistance,

$$X_m = \frac{1}{\rho_m} = 316.556 \Omega$$

$$\text{magnetizing inductance} = \frac{X_m}{2\pi f}$$
$$= 1.051 \text{ H}$$

Results:-

Short Circuit Test :-

- Test 1
 - Short circuit secondary
 - Open circuit tertiary
 - Voltage supply primary.

$$T_{sec} = 14.80 \text{ A.}$$

$$I_{sec} = 7.36 \text{ A}$$

$$V_{sec} = 2.19 \text{ V}$$

$$P_{sec} = 11.07 \text{ W}$$

Test 2 { Short circuit tertiary
Open circuit Secondary
Voltage supply primary

$$I_{ter} = 14.78 \text{ A}$$

$$I_{sc_2} = 7.42 \text{ A}$$

$$V_{sc_2} = 2.48 \text{ V}$$

$$P_{sc_2} = 13.06 \text{ W}$$

Test 3 { Short circuit tertiary
Open circuit ~~secondary~~ primary
Voltage supply secondary

$$I_{ter} = 14.48 \text{ A}$$

$$I_{sc_3} = 14.65 \text{ A}$$

$$V_{sc_3} = 1.06 \text{ V}$$

$$P_{sc_3} = 10.63 \text{ W}$$

Calculations :-

$$(ii) Z_{12} = \frac{V_{sc_1}}{I_{sc_1}} = \frac{2.19}{7.36} = 0.2976 \Omega$$

$$Z_{13} = \frac{V_{SC13}}{I_{SC13}} = \frac{2.48}{7.42} = 0.3342 \Omega$$

$$Z_{23} = \frac{V_{SC23}}{I_{SC23}} = \frac{1.06}{14.65} = 0.0724 \Omega$$

Leakage Impedances :-

$$\text{(iii)} \quad Z_1 = Y_2 (Z_{12} + Z_{13} - Z_{23}) \\ = 0.5 (0.2976 + 0.3342 - 0.0724) \\ = 0.5 (0.5594) = \underline{\underline{0.2797 \Omega}}$$

$$Z_2 = Y_2 (Z_{12} + Z_{23} - Z_{13}) \\ = 0.5 (0.2976 + 0.0724 - 0.3342) \\ = 0.5 (0.0358) = \underline{\underline{0.0179 \Omega}}$$

$$Z_3 = Y_2 (Z_{13} + Z_{23} - Z_{12}) \\ = 0.5 (0.0724 + 0.3342 - 0.2976) \\ = 0.5 (0.109) = \underline{\underline{0.0545 \Omega}}$$