

Power Electronics Lab Experiment-3

Swarnendu Paul

19EE3FP18

Part B:-

1.

Average DC output voltage, $V_{DC} = 380V$

Line-to-line RMS voltage, $V_{LL} = 440V$


We know, $V_{DC} = \frac{3\sqrt{2}}{\pi} V_{LL} \cos \alpha$

So, $\cos \alpha = \frac{380 \times \pi}{440 \times 3\sqrt{2}} = 0.6395$

So, firing angle $\alpha = 50.245^\circ$


2.

Load voltage:-

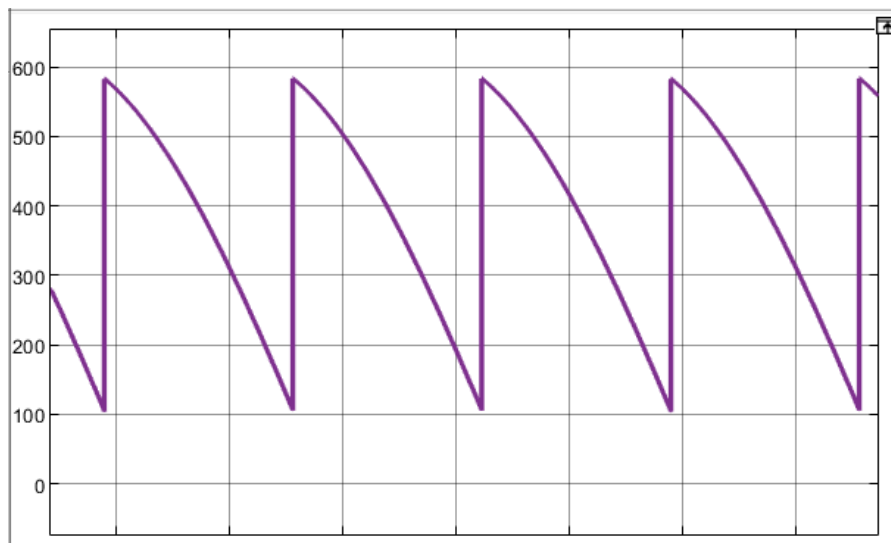

$V_{DC,avg} = 379.4V$

AC side current waveforms for 3 phases:-

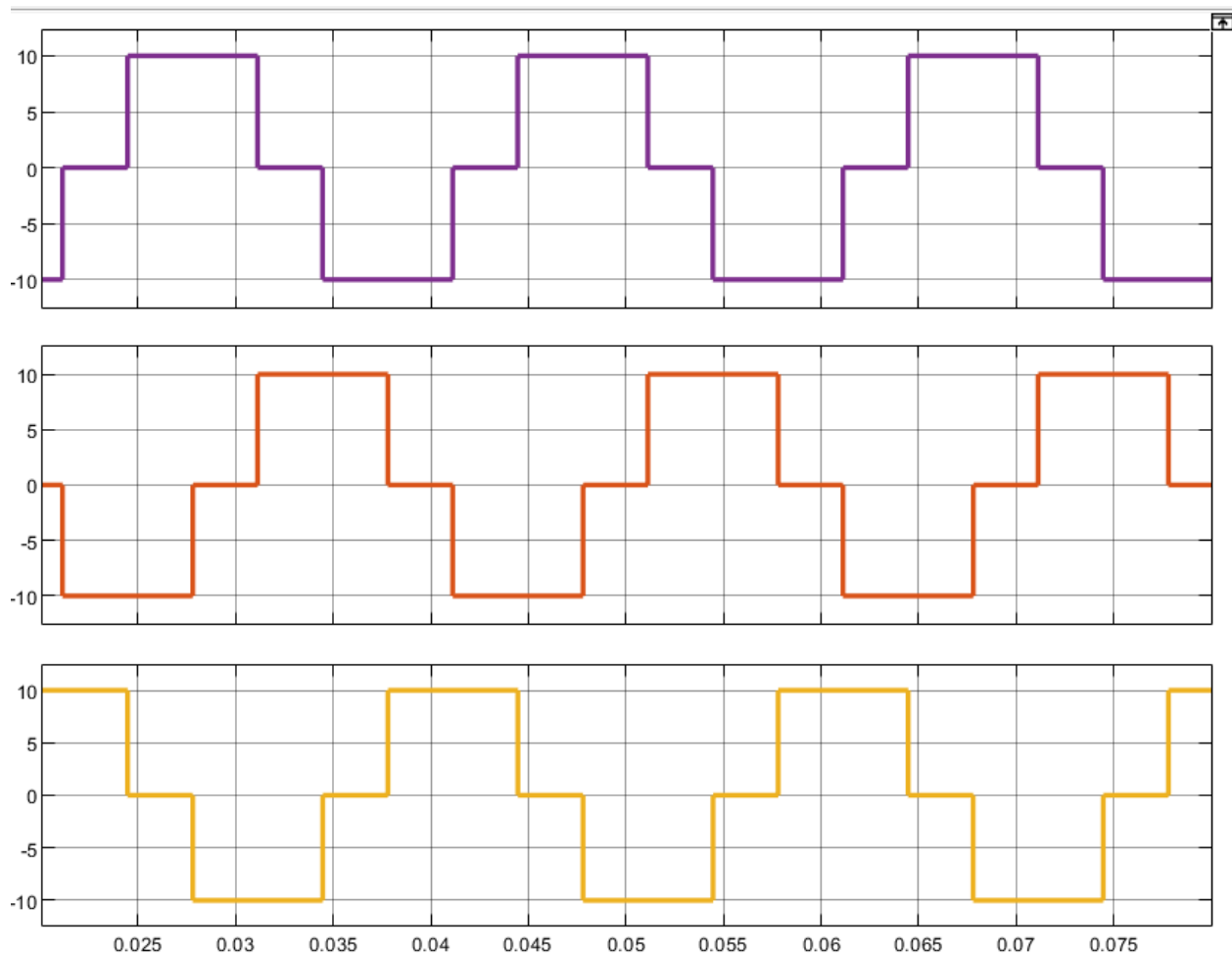


3.

Maximum reverse voltage across the thyristor = -622.2V

4.


Now we will vary α from 0° to 60° and note the output voltage and AC side currents.

For $\alpha=0^\circ$, V_{DC}

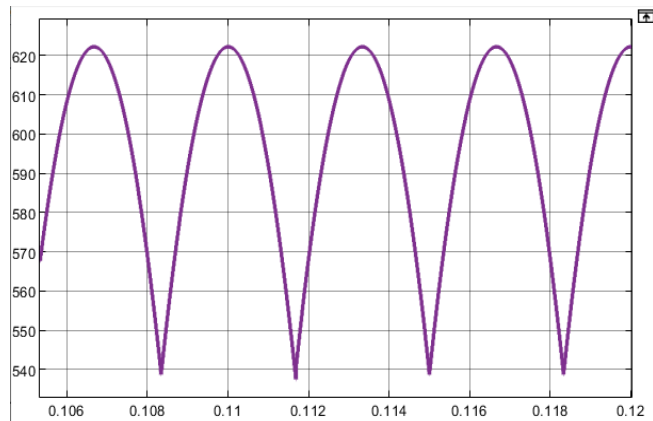


Average = 594.1V Calculated = 594.2V

AC side currents

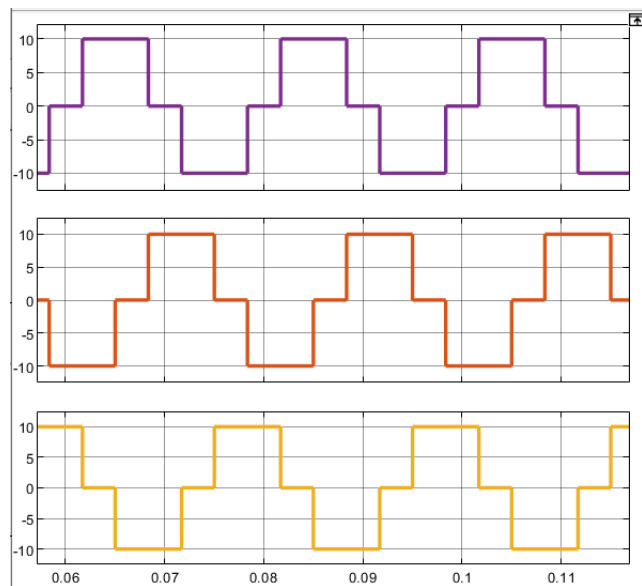


For $\alpha=15^\circ$, V_{DC}

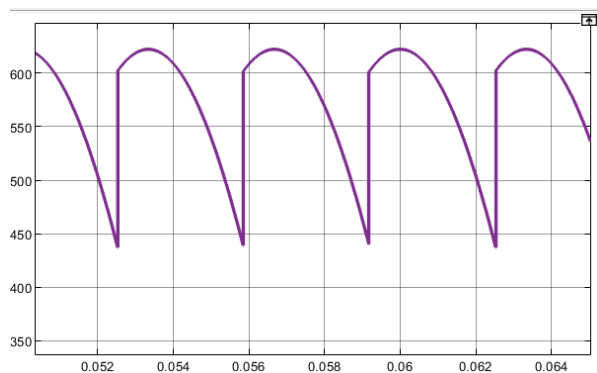


Average = 573.1V Calculated = 573.96V

AC side currents

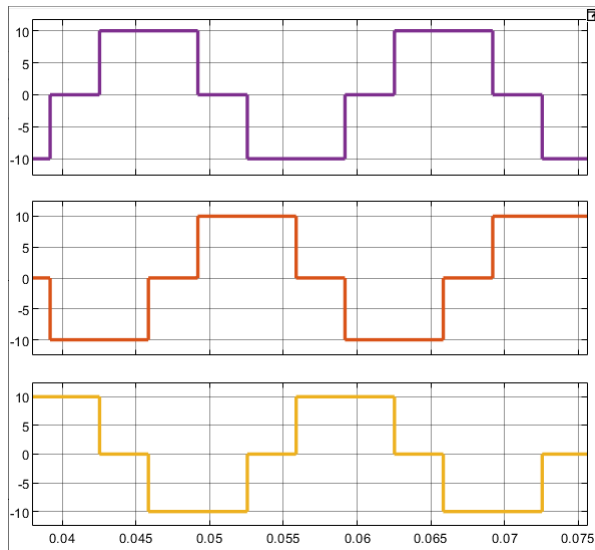


For $\alpha=30^\circ$, V_{DC}

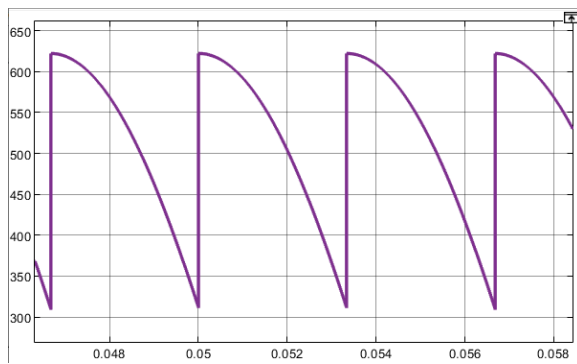


Average = 513.5V Calculated = 514.6V

AC side currents

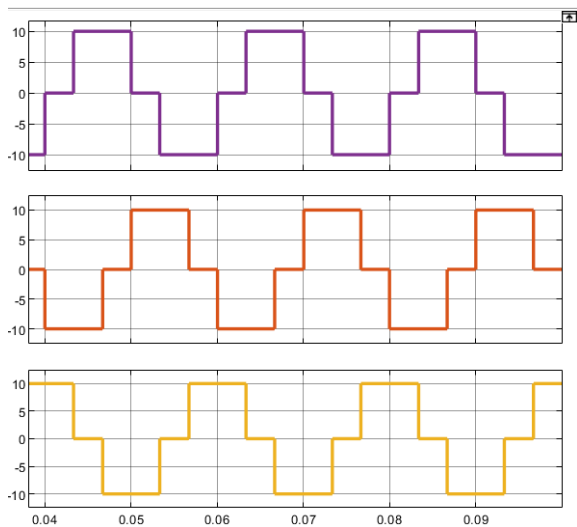


For $\alpha=45^\circ$, V_{DC}

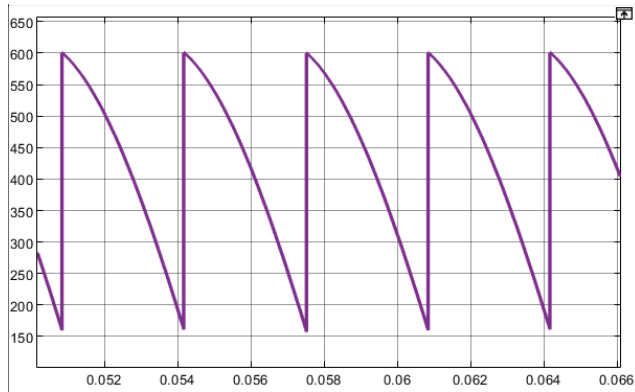


Average = 420.8V Calculated = 420.17V

AC side currents

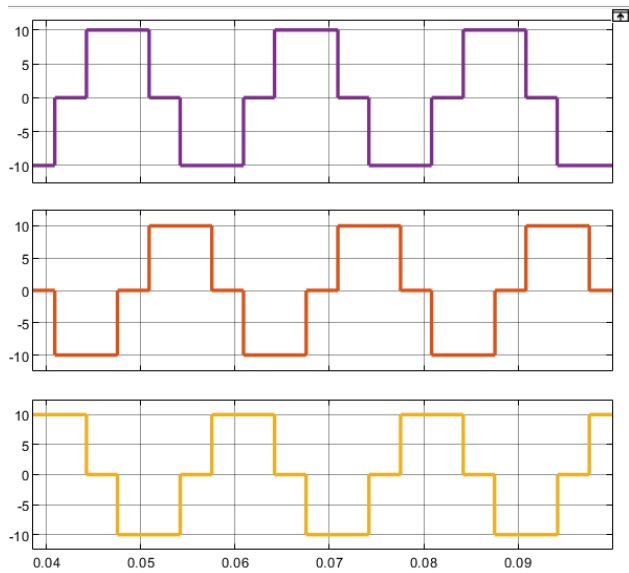


For $\alpha=60^\circ$, V_{DC}

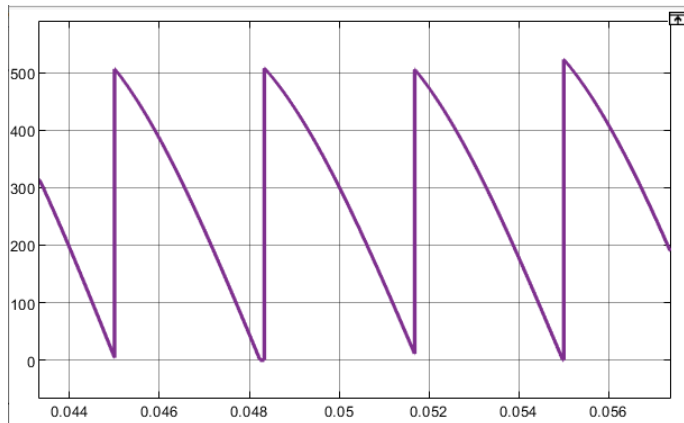

Average = 290.6V Calculated = 297.1V


AC side currents

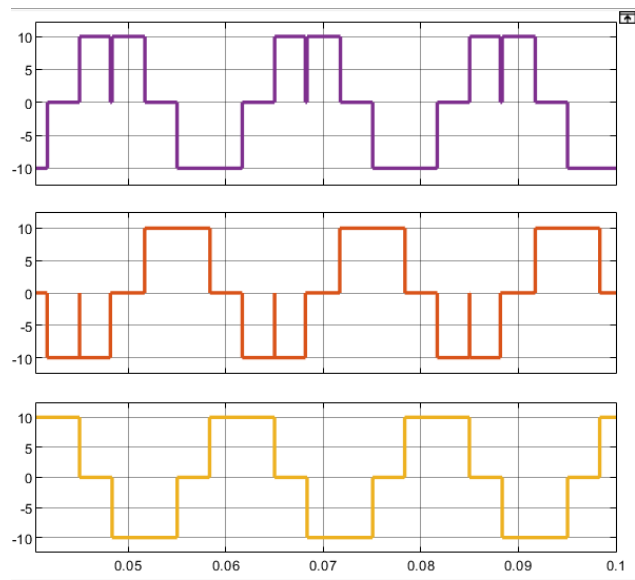

5.


Source inductance = 5mH

Load voltage:-

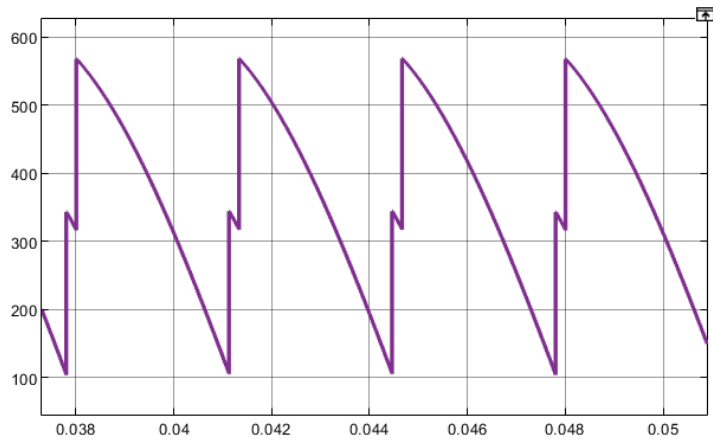

$$V_{DC,avg} = 365.4V$$

AC side current waveforms for 3 phases:-

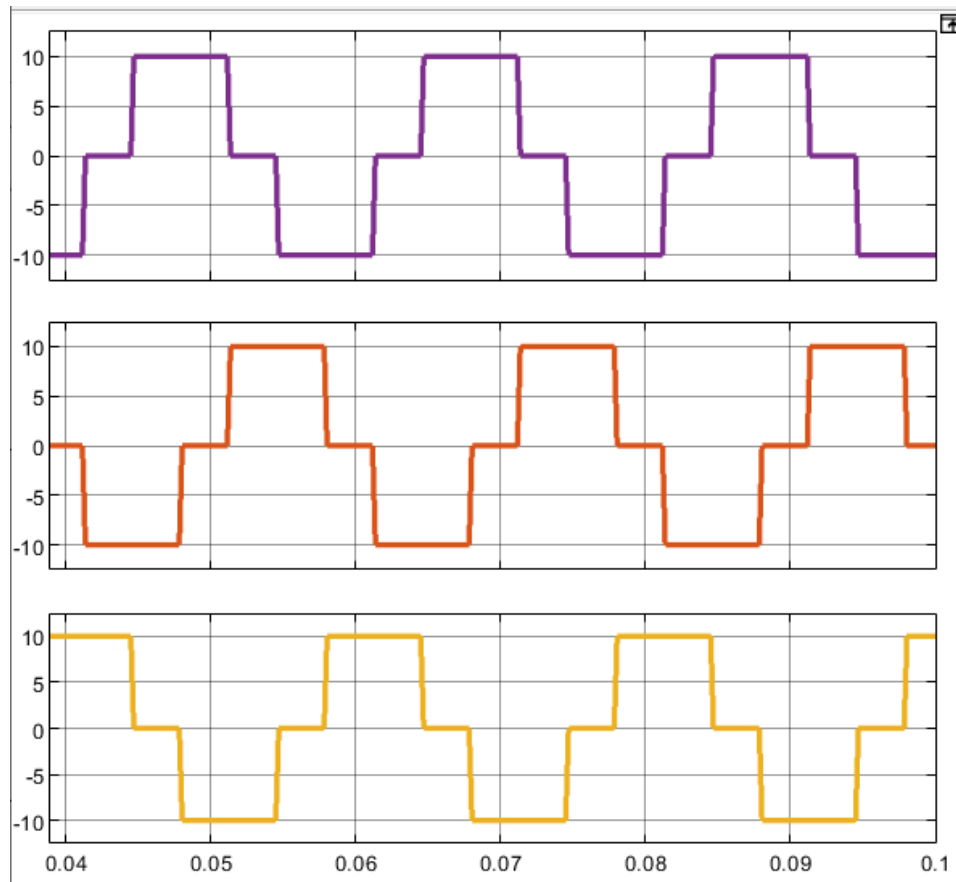

PART-C:-

1.

We know $V_{DC} = \frac{3\sqrt{2}}{2\pi} V_{LL} (1 + \cos\alpha)$


α is given, 45°

Hence $V_{DC} = \frac{3\sqrt{2}}{2\pi} \times 440 \times (1 + \frac{1}{\sqrt{2}}) = 507.189V$

For 10A Load current, $R_{Load} = 50.7189\Omega$


2.

Load voltage:-

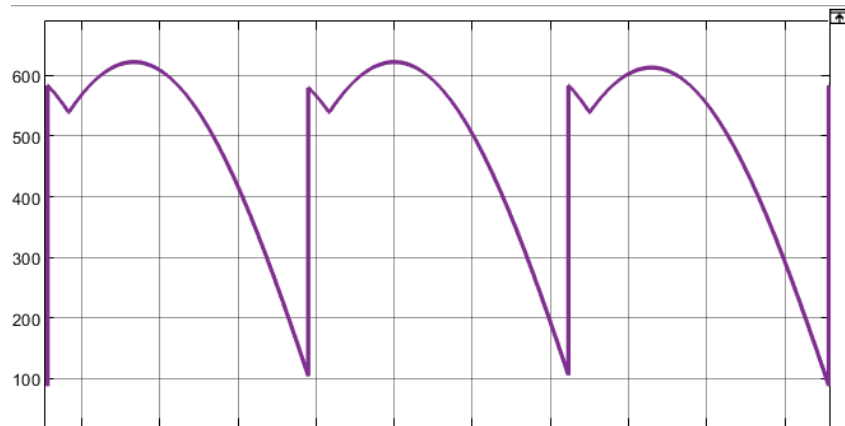

$$V_{DC,avg} = 481.4V$$

AC side current waveforms for 3 phases:-

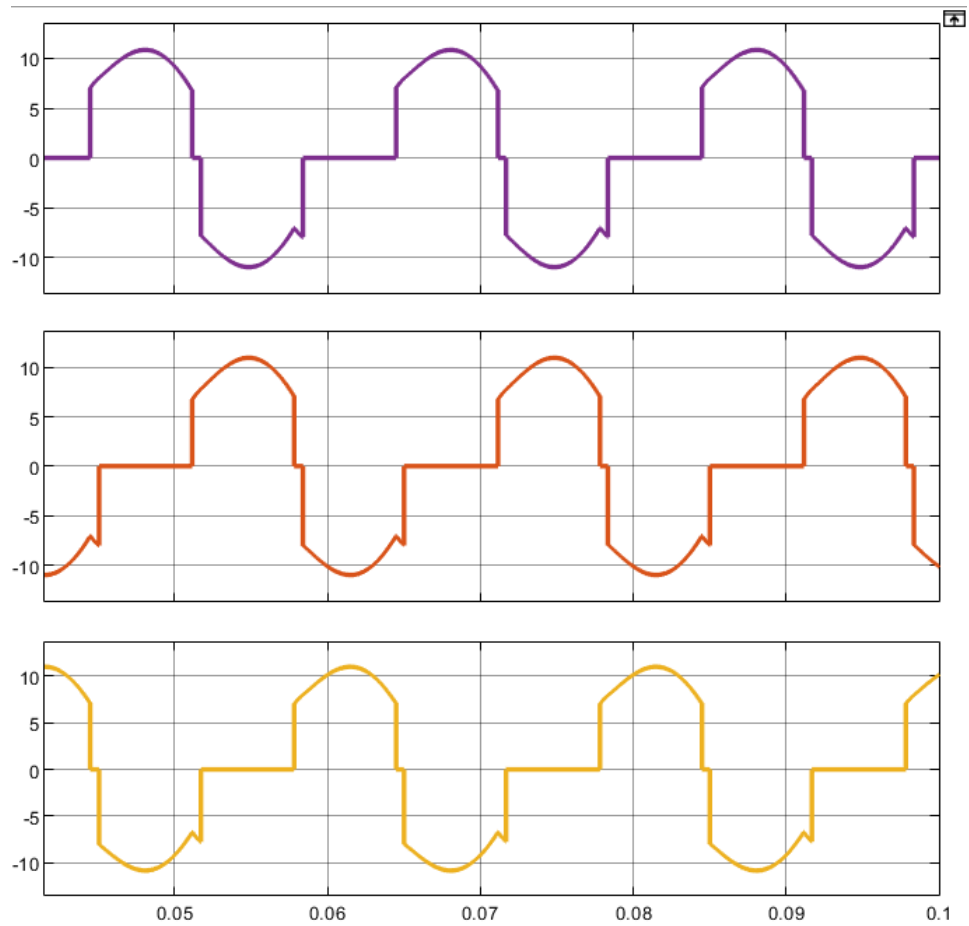

Part-D:-

$$\alpha = 30^\circ$$

Hence the output voltages of,

3-phase full controlled rectifier will be, $V_{DC} = 514.6V$

3-phase semi controlled rectifier will be, $V_{DC} = 554.4V$

Parameter	Full-controlled converter	Semi-controlled converter
AC side current(RMS)	8.1573	8.1604
Fundamental component of AC side currents(RMS)	7.788	7.524
THD(in%) of the AC side currents	31.16%	41.99%
Input power factor	0.8268	0.8906
Fundamental active power(W)	8903.13	9592.45
Fundamental Reactive power(VAr)	5140.08	2570.52