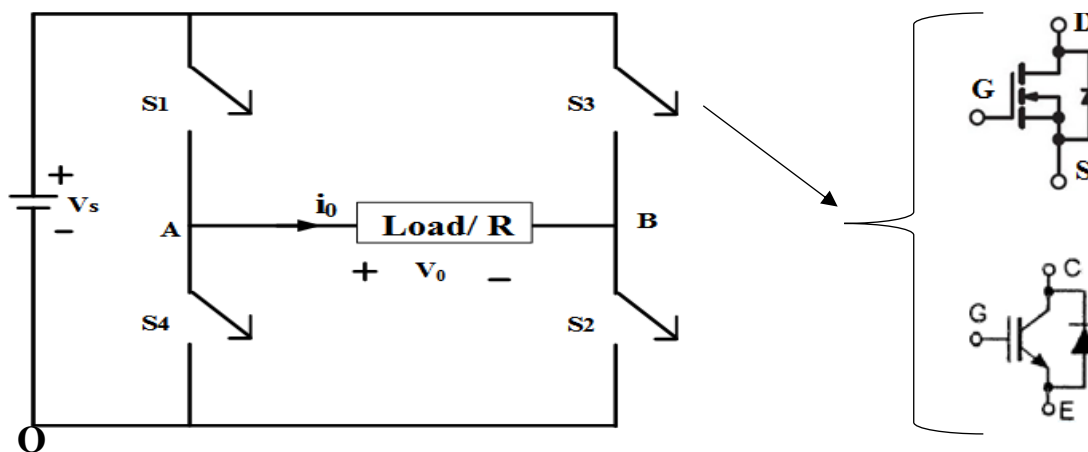


STUDY OF SINGLE-PHASE AND THREE PHASE INVERTERS AND THEIR MODULATION TECHNIQUES


Single Phase Voltage Source Inverter:

Circuit diagram:




Various Modulation schemes:

A. SQUARE WAVE MODULATION:

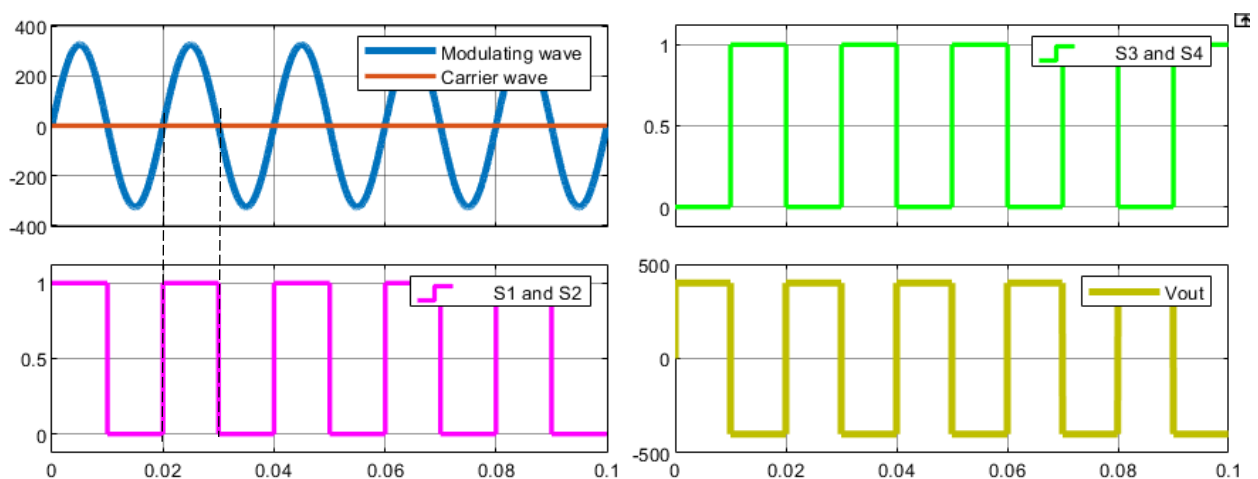

B. QUASI SQUARE WAVE MODULATION:

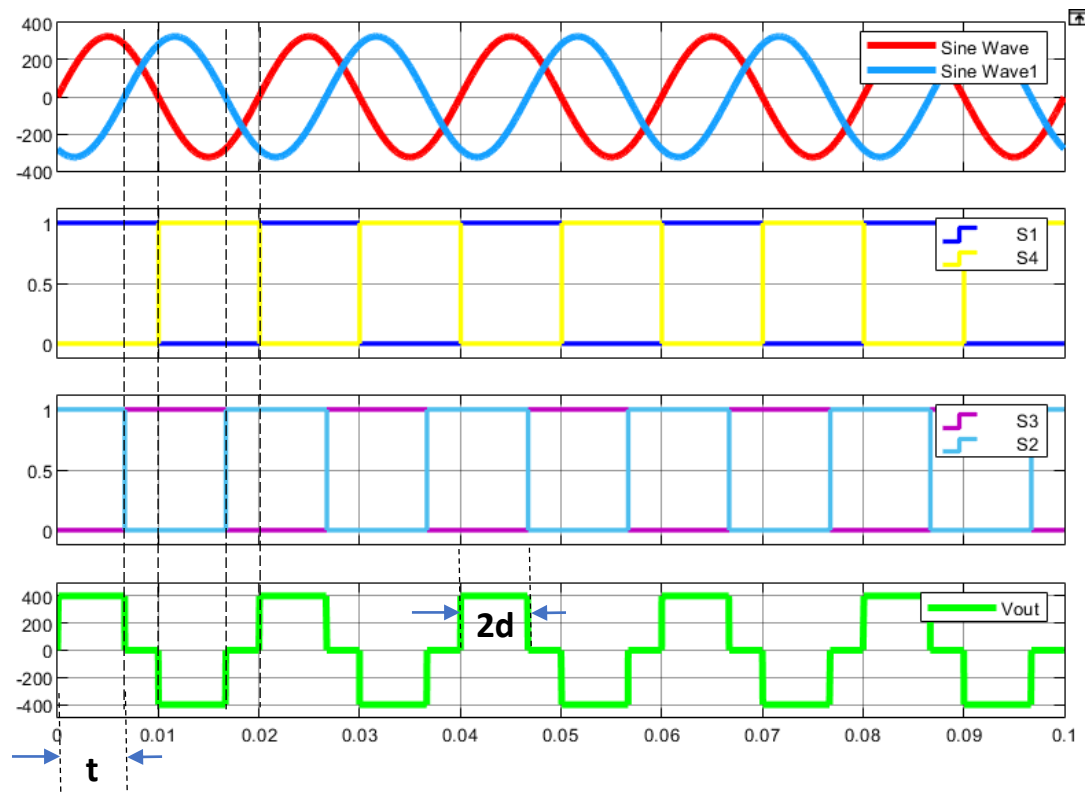

The output voltage can be calculated as

$$v_0 = \sum_{n=1,3,5\dots}^{\infty} \frac{4V_s}{n\pi} * \sin \frac{n\pi}{2} * \sin nd * \sin nwt$$

Now, if " $2d$ " is made equal to π , then the peak value of the fundamental output voltage can be written as

$$v_{01m} = \frac{4V_s}{\pi}$$


For other values $2d < \pi$,

$$v_{01m} = \frac{4V_s}{\pi} * \sin d$$


The phase shift between the two modulating signals can be calculated as:

$$\alpha = \frac{2\pi t}{T} \text{ radians}$$

C. UNIPOLAR MODULATION SCHEME:

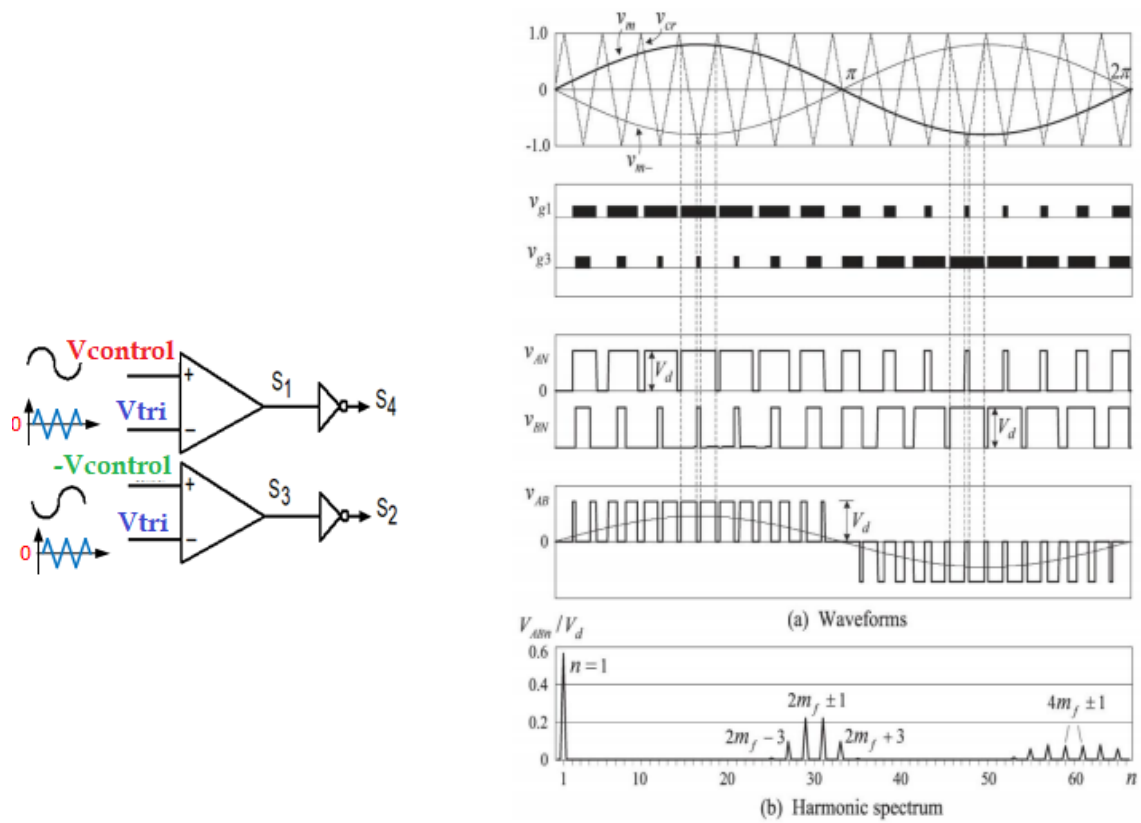


D. BIPOLAR MODULATION SCHEME:

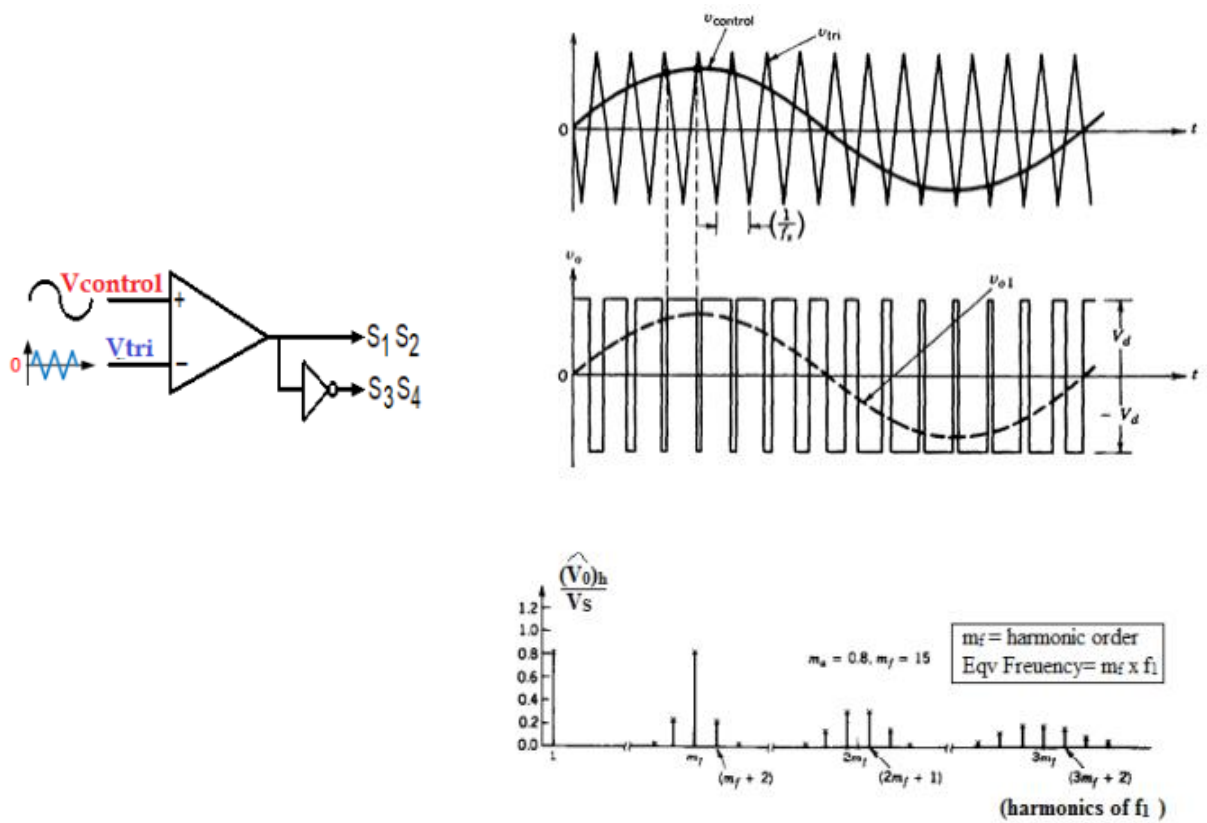


Three Phase Voltage Source Inverter:

Circuit diagram:

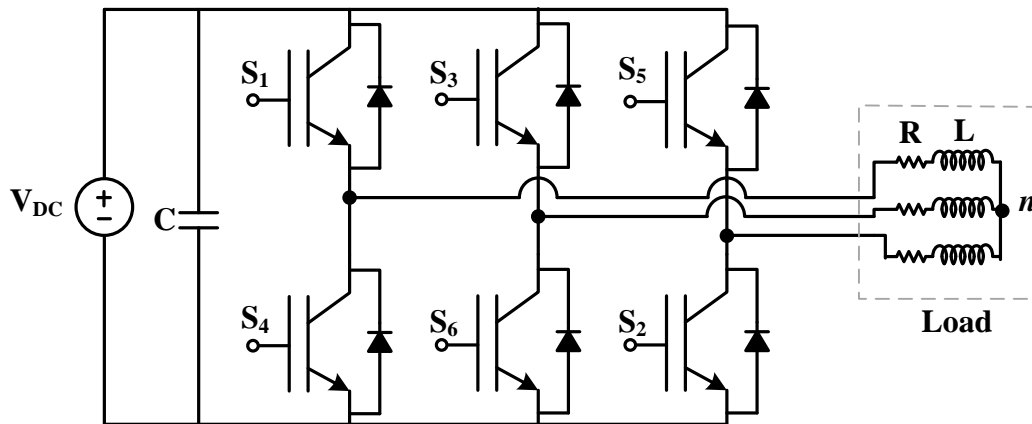


SPWM Modulation scheme:

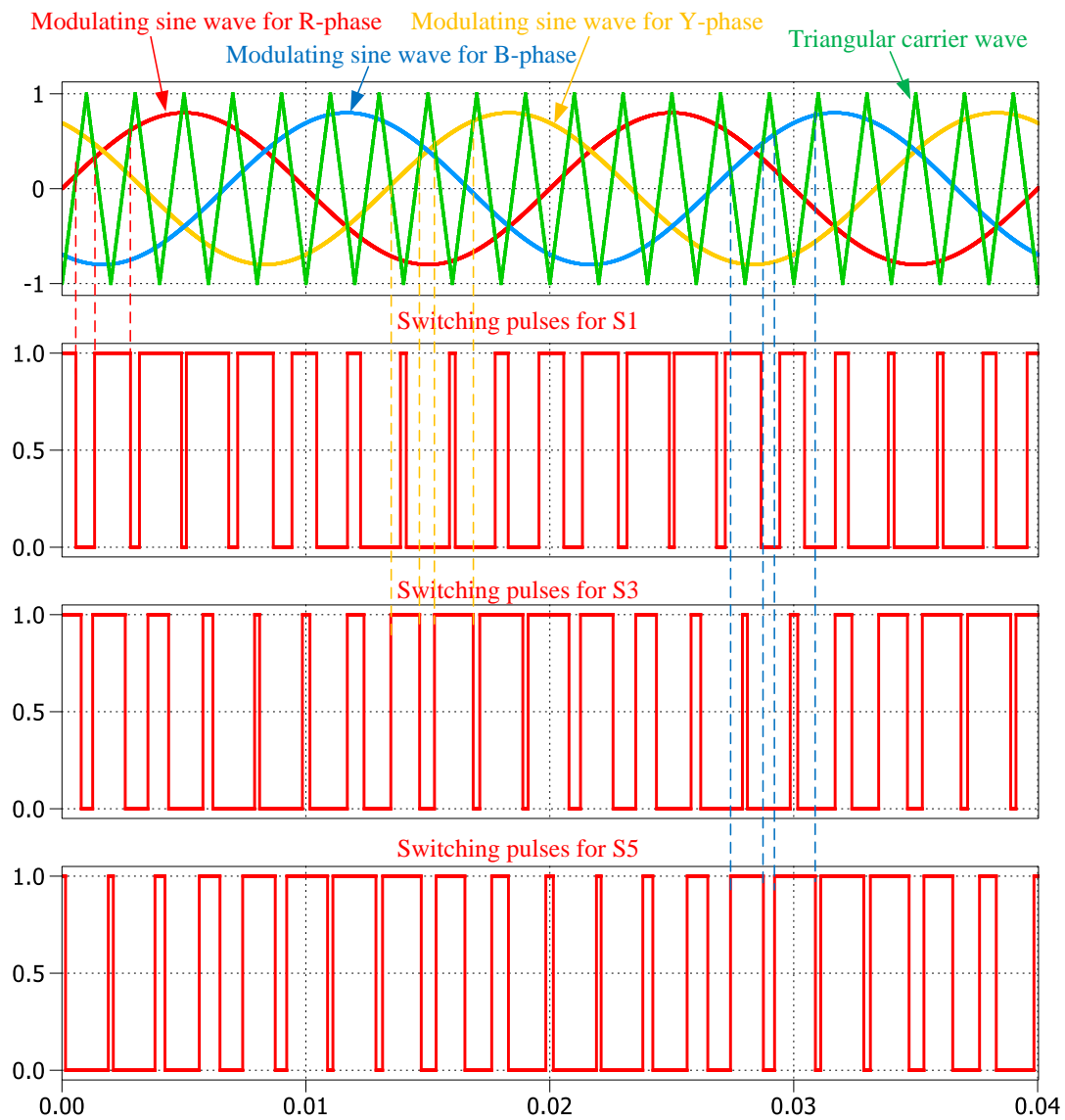

Switches in the same leg will have complementary switching pulses.


Analog scheme for SPWM implementation:

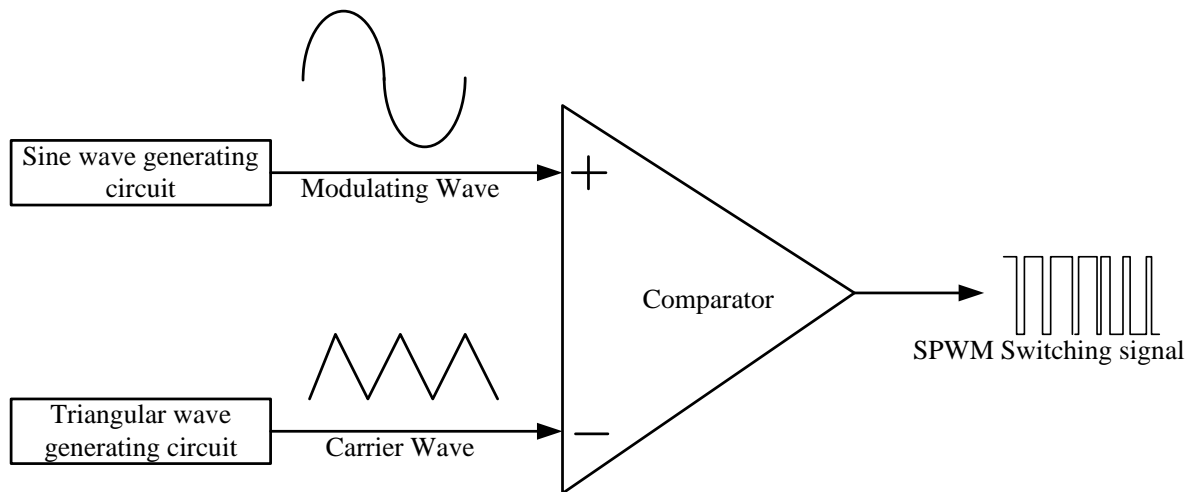

Advantages of SPWM compared to 180-degree mode of operation:

- The output voltage control can be obtained without addition of any external components.
- Minimizes the lower order harmonics, while the higher order harmonics can be eliminated using a filter.
- Easy to implement and control.
- Compatible with today's digital microprocessors.
- Allows linear amplitude control of the output voltage/current.
- Lower switching losses.
- Lower power dissipation and better utilization of DC power supply.

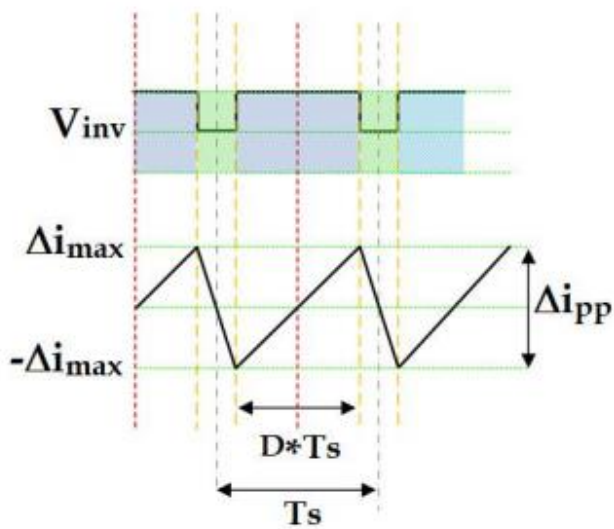Filter selection for single phase off grid inverter:



$$\Delta i_{pp} = \frac{D \times T_s \times (V_{DC} - V_{out})}{L_f}$$

$$\Delta i_{pp} = \frac{V_{DC} \times T_s \times m_a \times \sin(\omega t) \times (1 - m_a \sin(\omega t))}{L_f}$$

The ripple will be maximum at $\sin(\omega t) = \frac{1}{2 \times m_a}$

The L can be calculated as

$$\Delta i_{pp}|_{max} = \frac{V_{DC} \times T_s}{4 \times L_f}$$


$$L_f = \frac{V_{DC}}{4 \times F_{sw} \times \Delta i_{pp}|_{max}}$$

The filter capacitance can be calculated considering the cut-off frequency of the filter is at max 1/10th of the switching frequency

$$F_{cut-off} = \frac{1}{2 \pi \sqrt{L_f C_f}}$$

$$C_f = \frac{1}{L_f (2 \pi F_{cut-off})^2}$$

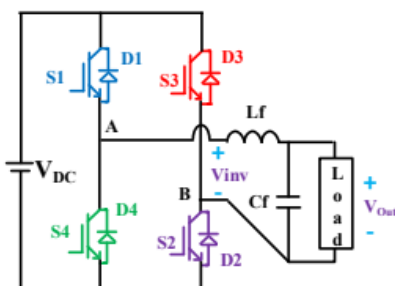Loss calculation for single phase Inverter:



$$D_{S1} = \frac{1}{2} + \frac{M_a \sin \omega t}{2}$$

$$D_{S4} = D_{S3} = (1 - D_{S1})$$

$$D_{S3} = \frac{1}{2} - \frac{M_a \sin \omega t}{2}$$

➤ The average currents for the switches and diodes can be calculated as

$$I_{S1}(avg) = \frac{1}{2\pi} \int_0^\pi (i_L * D_{S1}) d\theta$$

$$I_{S1}(avg) = \frac{1}{2\pi} \int_0^\pi (I_m \sin(\omega t - \Phi) * (\frac{1}{2} (1 + M_a \sin \omega t))) d\theta$$

$$I_{S1}(avg) = I_m (\frac{1}{2\pi} + \frac{M_a \cos \Phi}{8})$$

$$D_{S4} = 1 - D_{S1} = \frac{1}{2} - \frac{M_a \sin \omega t}{2}$$

$$I_{D4}(avg) = I_m (\frac{1}{2\pi} - \frac{M_a \cos \Phi}{8})$$

➤ Similarly, the rms current expression for the switches and diodes can be written as:

$$I_{s1}(RMS) = \sqrt{\frac{1}{2\pi} \int_0^\pi (iL^2 * Ds1) d\theta}$$

$$I_{D4}(Avg) = Im \sqrt{\frac{1}{8} - \frac{Ma \cos\Phi}{3\pi}}$$

$$I_{s1}(RMS) = Im \sqrt{\frac{1}{8} + \frac{Ma \cos\Phi}{3\pi}}$$

➤ The total conduction loss can be calculated as

$$P_{s1_cond} = \{V_{s1_drop} * I_{s1}(avg)\} + \{R_{s1} * I_{s1}(RMS)^2\}$$



$$P_{D4_cond} = \{V_{D4_drop} * I_{D4}(avg)\} + \{R_{D4} * I_{D4}(RMS)^2\}$$

• Total loss

$$P_{tot_cond} = 4 (P_{s1_cond} + P_{d4_cond})$$

The concept of Dead Time:

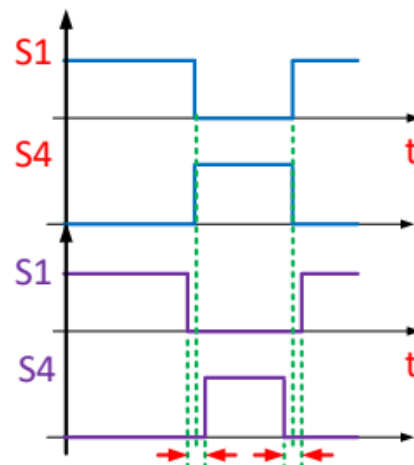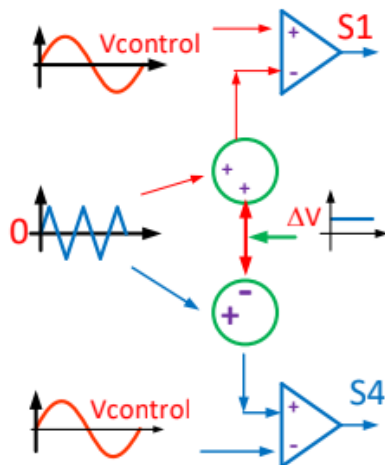- To avoid the simultaneous conduction of the switches of the same leg of the inverter a small amount of Dead Time is important.
- This can be achieved by shifting the carrier signal by a small dc value as shown in fig below:



➤