

# **POWER ELECTRONICS LAB**

## **Experiment-I**

### **STUDY OF BASIC TRANSISTOR CONVERTERS**

**Name:- SWARNENDU PAUL**

**Roll No.:- 19EE3FP18 Batch:- Monday**

---

#### **Part-A**

Simulate the **buck converter** in MATLAB/simulink using following parameters:


Input Voltage( $V_{in}$ ) = 110V, Capacitance  $C = 4\mu F$ , Load resistance  $R_L = 11.52\Omega$ , Switching Frequency = 50kHz. Choose MOSFET and diode resistance as  $1\mu\Omega$ , and diode voltage drop as 0 V (to simulate close to an ideal converter).

**I.** Select the value of  $L$  such that the converter operates in CCM for the given condition. Change duty ratio in steps of 0.1 starting from 0.1 to 0.9, and tabulate calculated and measured value of the output voltage. Also, plot a graph of voltage gain( $V_{out}/V_{in}$ ) Vs Duty Ratio(in x-axis) for CCM operation. Note: change  $L$  value if required, but make sure that the converter operates in CCM always for the entire duty ratio (limiting inductor value for CCM and DCM at 0.1 duty ratio).

**II.** Now select  $L$  such that the converter operates in DCM. For the duty ratio 0.5 compare the output voltage obtained in the CCM and DCM case.

III. For a given duty ratio(say 0.5) observe and save simulated waveforms for the following variables for both CCM and DCM case: current and voltage waveforms of MOSFET, inductor, diode, and output capacitor.

### Buck Converter circuit:

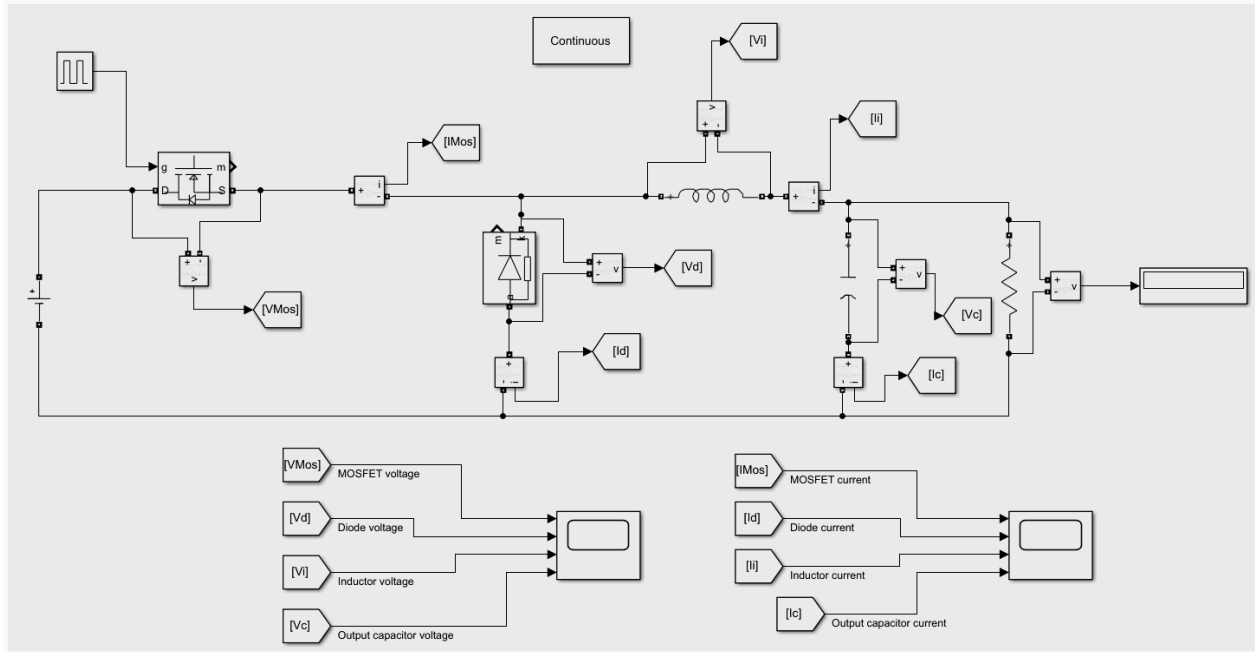

$$V_{in} = 110V, C = 4\mu F, R_L = 11.52\Omega, f_{sw} = 50KHz$$

I.

For the circuit to operate in CCM, we need

$$L \geq \frac{(1-D_{min}) \times R_{max}}{2 \times f_{sw}}$$


Here  $D_{min} = 0.1$   $R_{max} = 11.52\Omega$ ,  $f_{sw} = 50KHz$

Hence  $L \geq 103.68\mu H$

We have chosen  $L=110\mu H$  for this converter.

Duty Ratio	Calculated $V_{out}(V)$	Observed $V_{out}(V)$	Gain ( $V_{out}/V_{in}$ )
0.1	11	10.39	0.0945
0.2	22	21.15	0.1923
0.3	33	32.22	0.2929
0.4	44	43.49	0.3954
0.5	55	54.90	0.4991
0.6	66	66.32	0.6029
0.7	77	77.67	0.7061
0.8	88	88.74	0.8067
0.9	99	99.54	0.9049

Voltage Gain vs Duty Ratio plot:

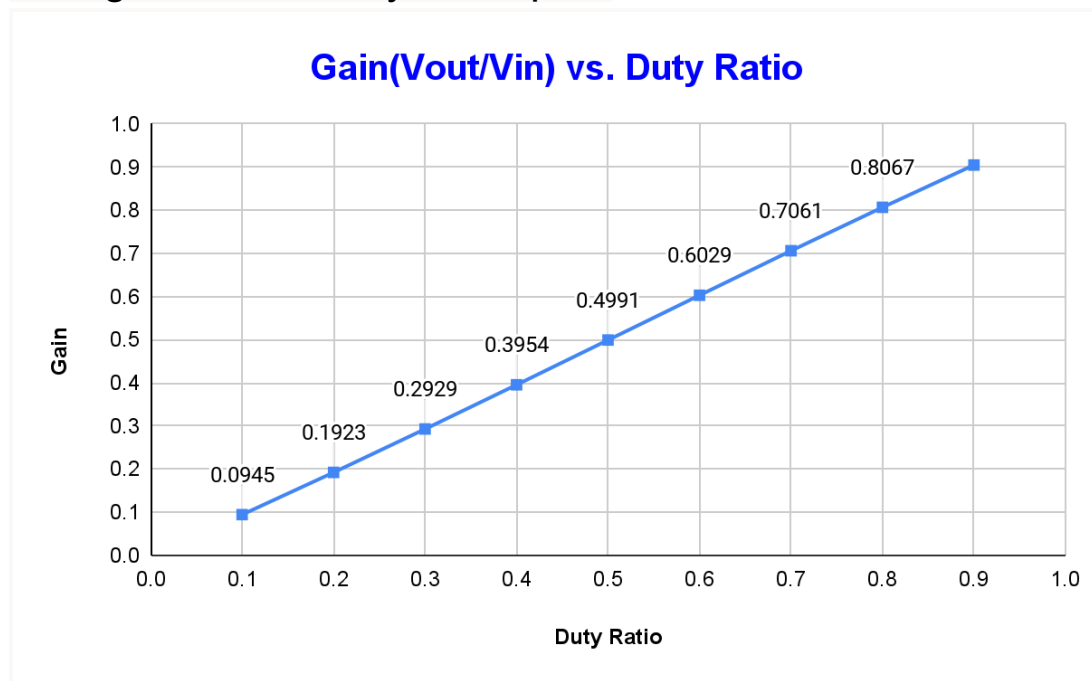

## II.

Now we need to operate the converter in DCM at duty ratio 0.5

$V_{in} = 110V$ ,  $C = 4\mu F$ ,  $R_L = 11.52\Omega$ ,  $f_{sw} = 50KHz$

For the circuit to operate in CCM, we need

$$L \leq \frac{(1-D_{max}) \times R_L}{2 \times f_{sw}}$$

Here  $D_{max} = 0.5$   $R_{max} = 11.52\Omega$ ,  $f_{sw} = 50KHz$

Hence,  $L \leq 57.6\mu H$

We have chosen  $L=50\mu H$  for this converter to operate in DCM.

### Result:

Output voltage = 57.35V (DCM) (Calculated at  $L=50\mu H$ )

Output voltage = 54.90V (CCM) (Calculated at  $L=110\mu H$ )  
(Calculated at  $L=110\mu H$ )

## III.


For duty ratio  $D=0.5$  now we will observe the current and voltage waveforms of MOSFET, Diode, Inductor and Output capacitor for both the CCM and DCM case.

Limiting value of  $L$  for which the converter operates in DCM at  $D=0.5$  is  $57.6\mu H$ .


So we have chosen  $L=30\mu H$  for DCM and  $L=90\mu H$  for CCM operation of the converter circuit.

## DCM current waveforms:


### MOSFET current

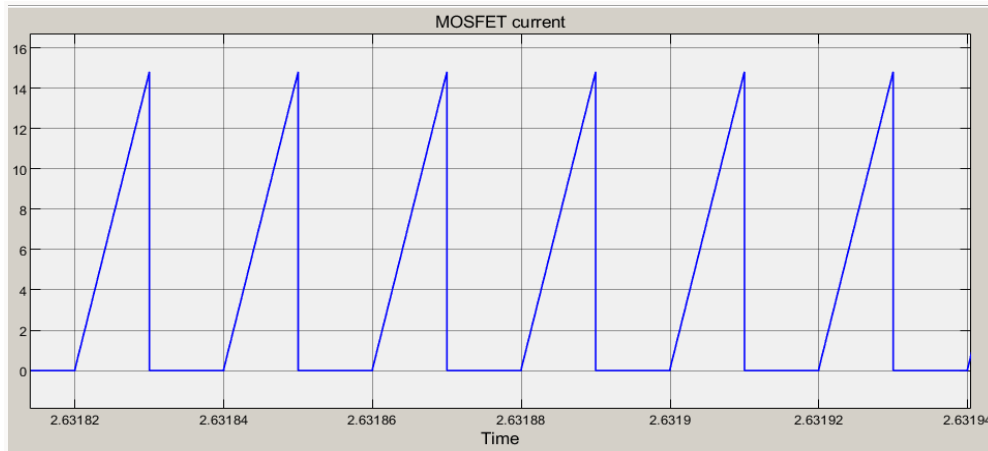


### Diode current

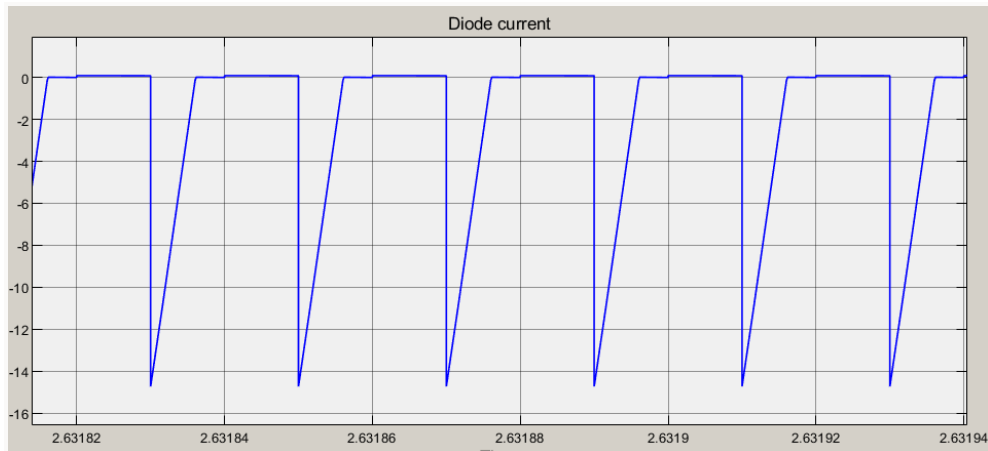


### Inductor current

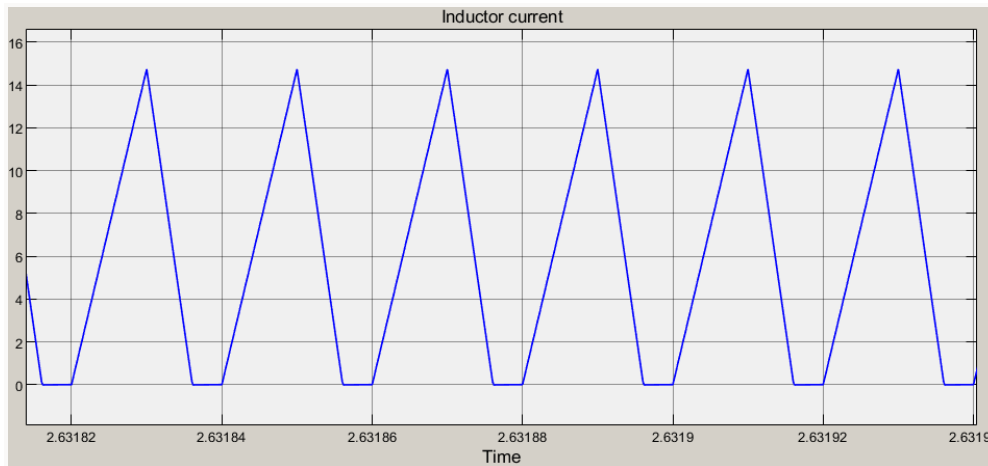


## Output Capacitor Current

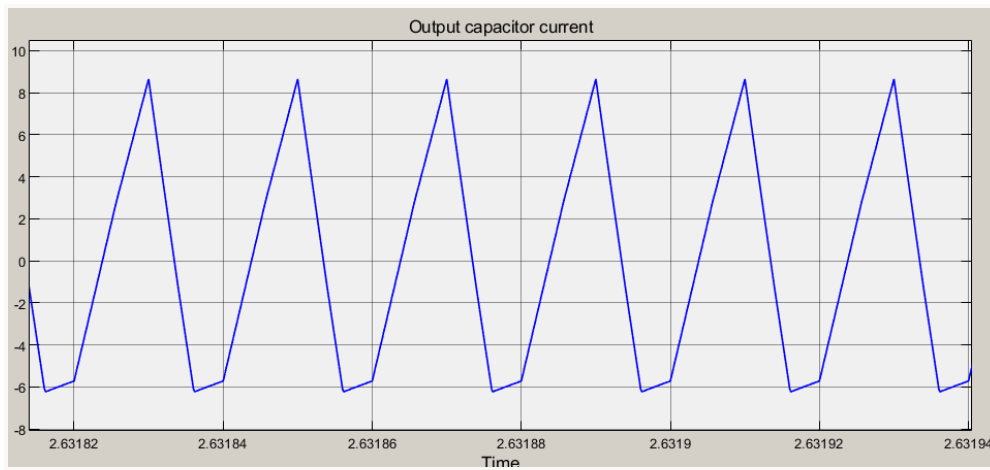


## DCM voltage waveforms: MOSFET voltage

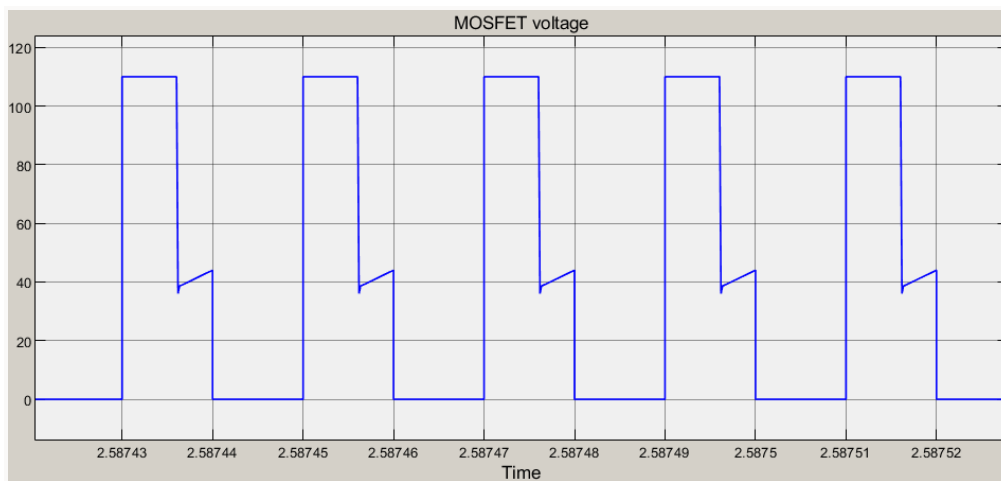


## Diode voltage

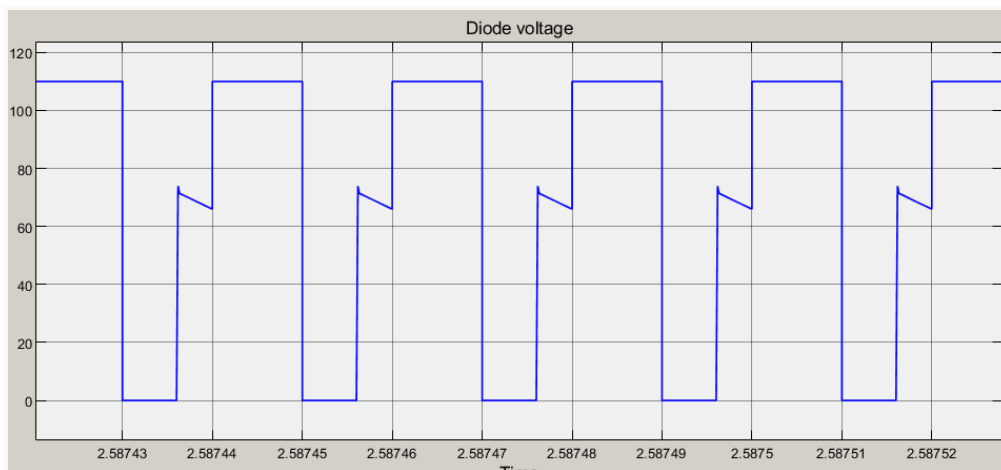

## Inductor Voltage

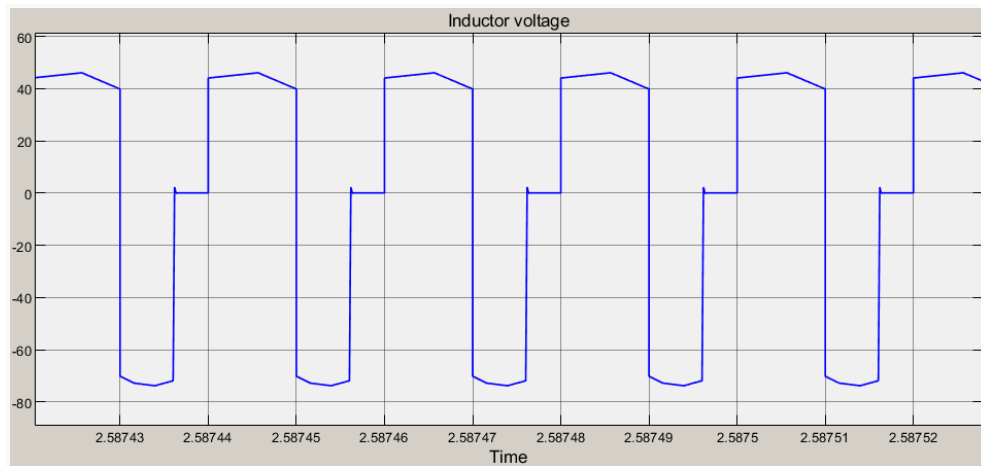


## Output capacitor voltage

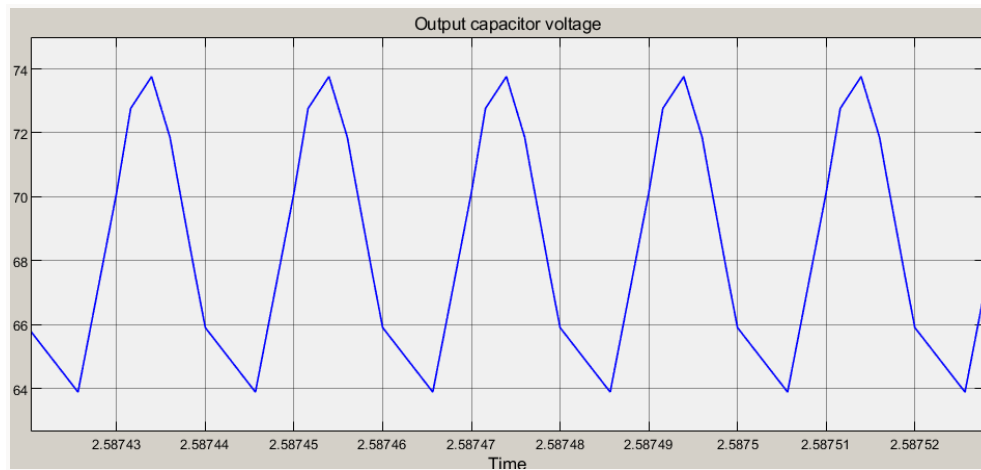


## CCM current waveforms:


### MOSFET Current

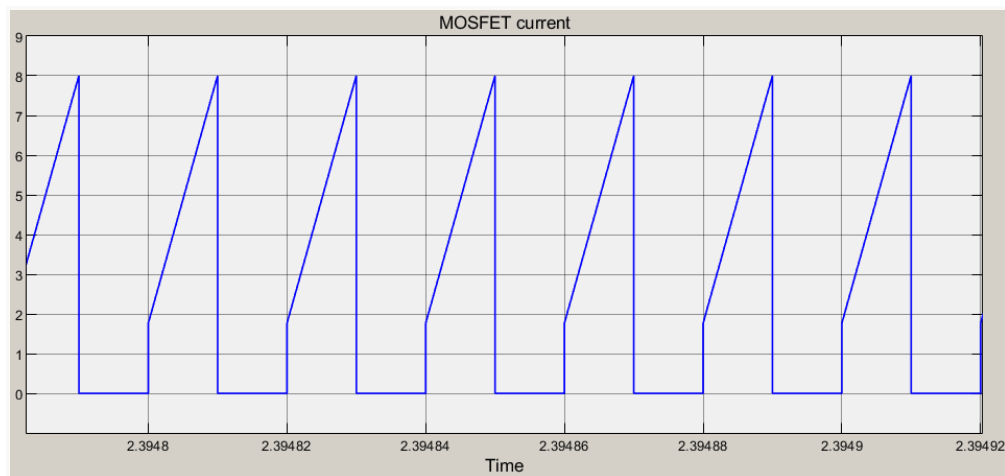


## Diode current

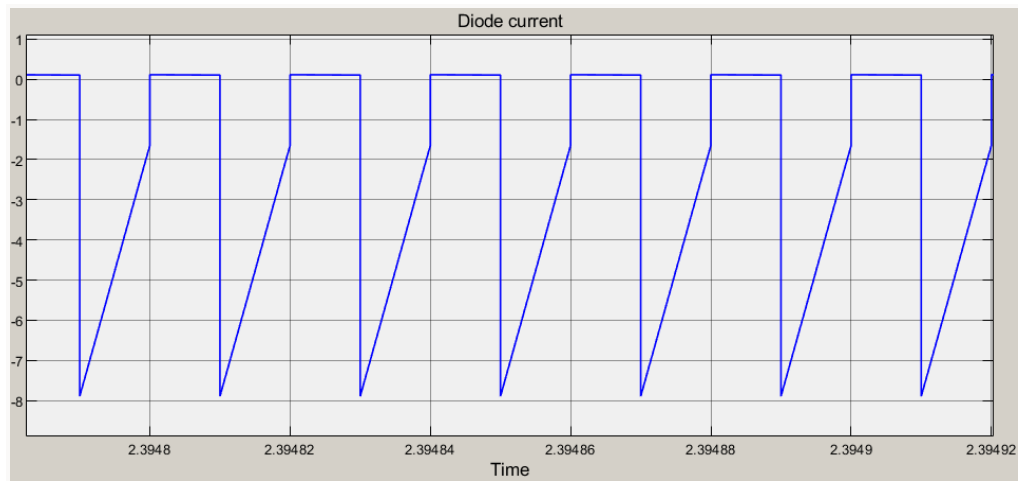

## Inductor current

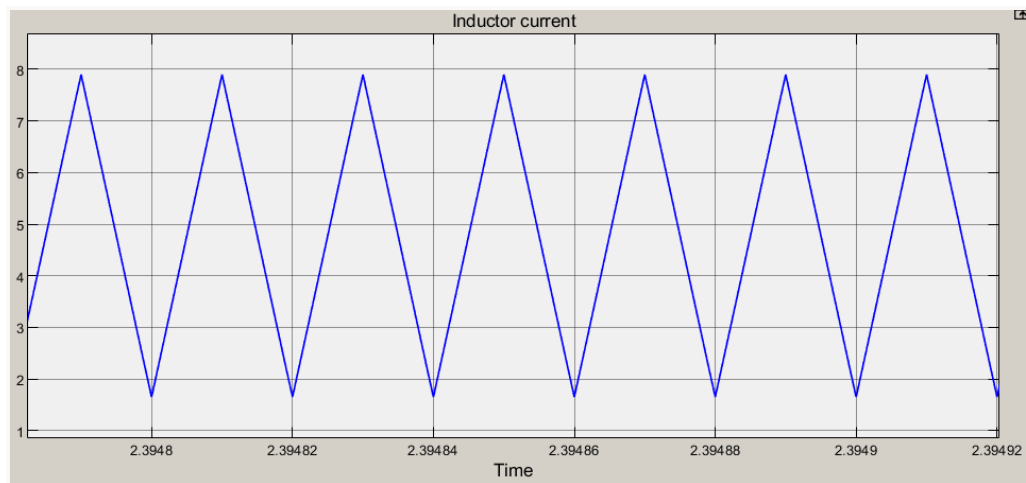


## Output capacitor current

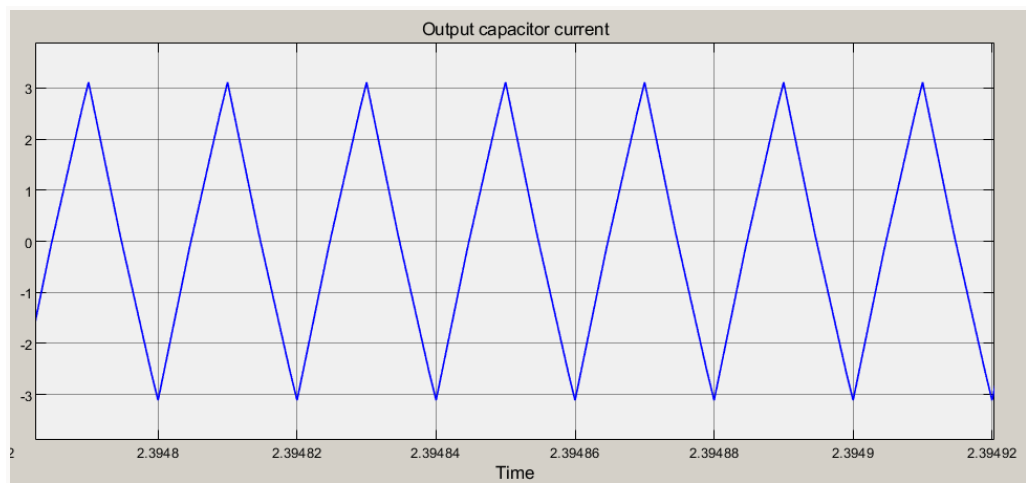




## CCM voltage waveforms:


### MOSFET voltage

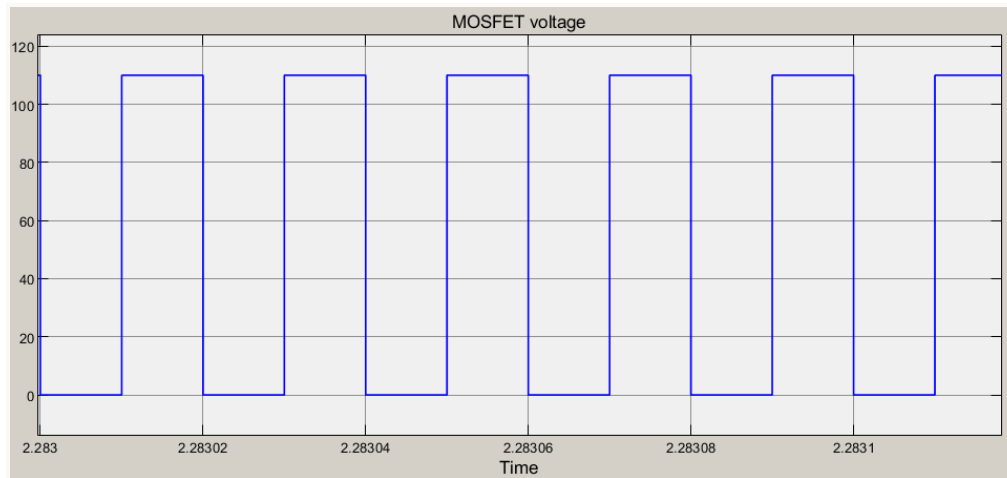


### Diode voltage

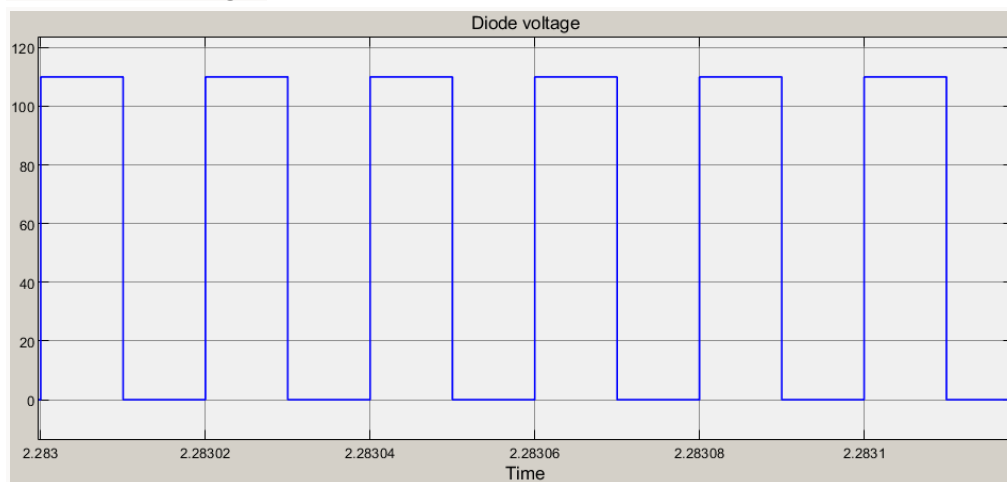

### Inductor voltage

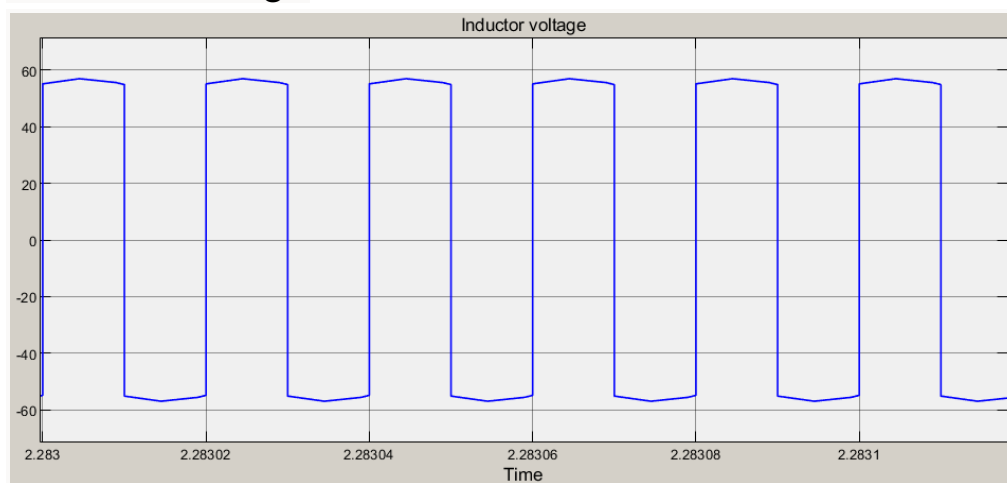

## Output capacitor voltage

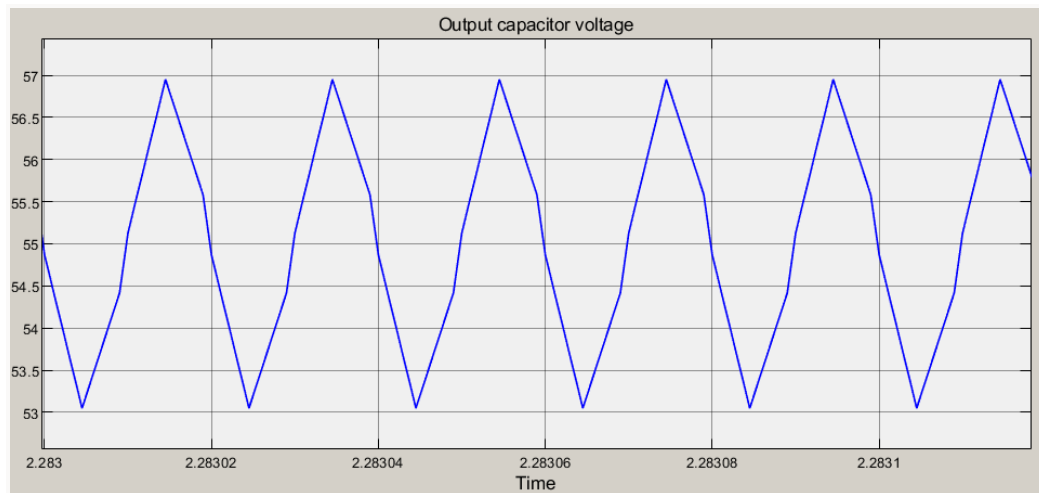


### Part-B

Simulate the **buck-boost converter** in MATLAB/Simulink using following parameters: Input Voltage( $V_{in}$ ) = 57V, Inductor  $L = 226\mu\text{H}$ , Capacitance  $C = 54\mu\text{F}$ , Load resistance  $R_{Load} = 11.52\Omega$ , Switching Frequency = 50kHz, Duty Cycle = 0.457. Choose MOSFET and diode resistance as  $1\mu\Omega$ , and diode voltage drop as 0. Select parasitic resistance of inductor  $R_L = 0\Omega$  in case(i) and  $R_L = 5\%$  of  $R_{Load}$  in case(ii). Vary Duty ratio from 0.1 to 0.9 in steps of 0.1

- I. Plot the voltage gain Vs duty ratio in case(i) and case(ii), and comment on the same.
- II. Keeping all other parameters the same, vary the switching frequency and check at what frequency the system will be on the verge of CCM and DCM conditions for case(i) and case(ii) for  $D=0.457$ ?
- III. For case (i) tabulate the steady-state input and output currents for various duty ratios.

## Buck-Boost converter circuit:

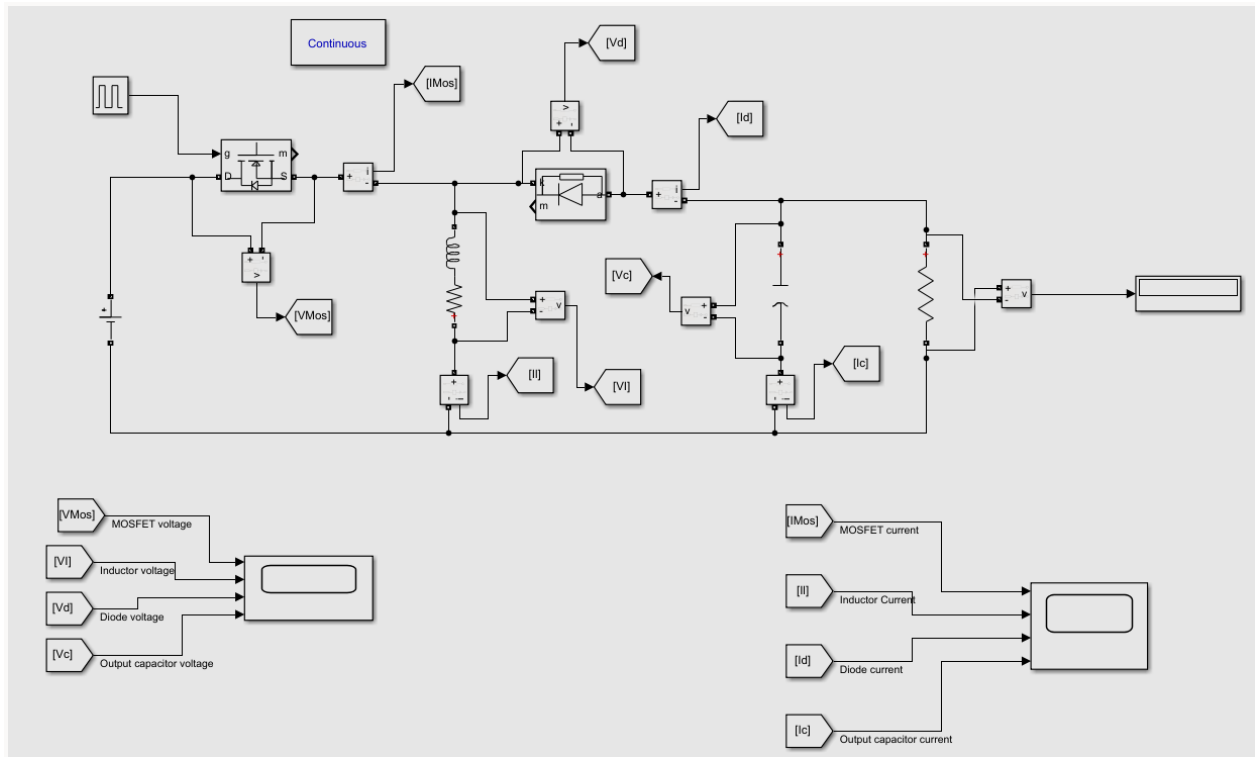

$V_{in} = 57V$ ,  $C = 54\mu F$ ,  $R_{Load} = 11.52\Omega$ ,  $f_{sw} = 50KHz$ ,  $L=226\mu H$

Polarity of Output voltage is always negative, the data shows the magnitude of output voltage.

I.

Case(i):


Parasitic resistance  $R_L = 0\Omega$

So, in CCM condition,  $gain(V_{out}/V_{in}) = \frac{D}{1-D}$

$V_{in} = 57V$ ,  $C = 54\mu F$ ,  $R_{Load} = 11.52\Omega$ ,  $f_{sw} = 50KHz$ ,  $L=226\mu H$

Duty Ratio	Calculated $V_{out}(V)$	Observed $V_{out}(V)$	Gain $(V_{out}/V_{in})$
0.1	6.33	6.34	0.1112
0.2	14.25	14.31	0.2511
0.3	24.43	24.59	0.4314
0.4	38.00	38.36	0.6730
0.5	57.00	57.45	1.0079
0.6	85.50	86.32	1.5144
0.7	133.00	134.49	2.3595
0.8	228.00	230.93	4.0514
0.9	513.00	520.43	9.1304

Voltage Gain vs Duty Ratio plot:

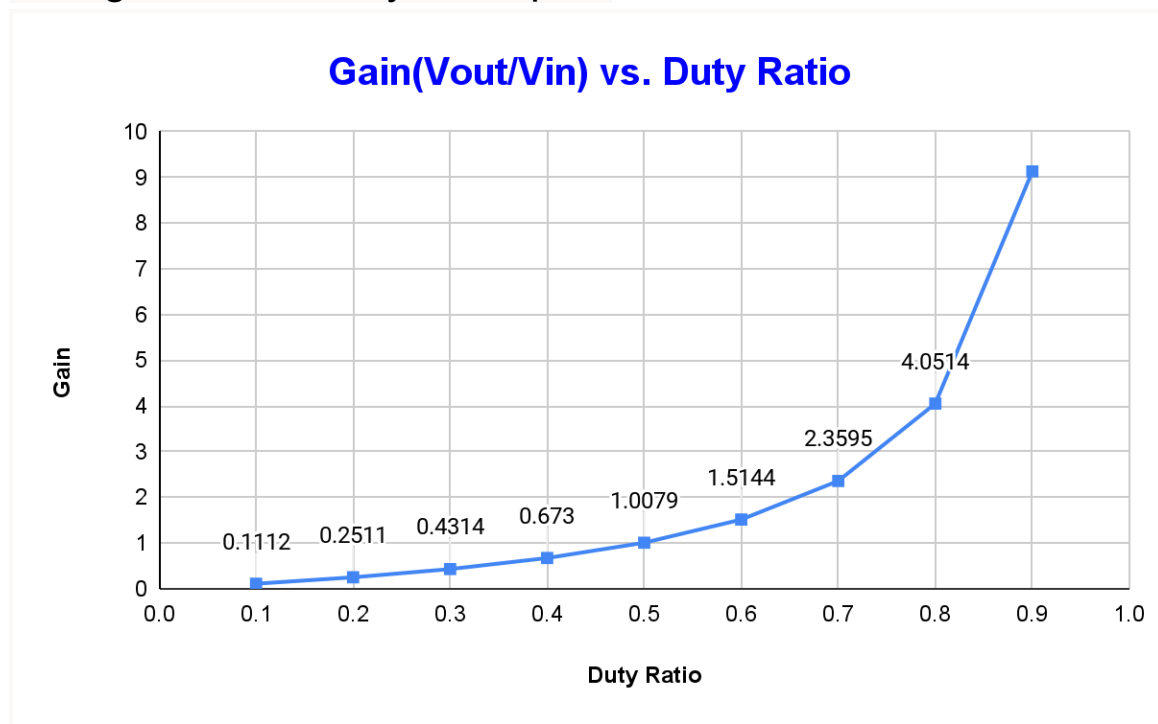

The plot strongly follows the formula  $Gain = \frac{D}{1-D}$  as there is no parasitic resistance in the inductor, the gain increases exponentially as we increase duty ratio.

Case(ii):


Parasitic resistance  $R_L = 5\%$  of  $R_{Load} = 0.576\Omega$

So, in CCM condition,  $gain(V_{out}/V_{in}) = \frac{D}{1-D + \frac{R_L}{R_{Load}(1-D)}}$

$V_{in} = 57V$ ,  $C = 54\mu F$ ,  $R_{Load} = 11.52\Omega$ ,  $f_{sw} = 50KHz$ ,  $L = 226\mu H$

Duty Ratio	Calculated $V_{out}(V)$	Observed $V_{out}(V)$	Gain ( $V_{out}/V_{in}$ )
0.1	5.97	5.96	0.1046
0.2	13.22	13.23	0.2321
0.3	22.17	22.22	0.3898
0.4	33.37	33.50	0.5877
0.5	47.50	47.77	0.8381
0.6	65.14	65.60	1.1509
0.7	88.67	86.21	1.5125
0.8	101.33	102.31	1.7949
0.9	85.50	86.49	1.5174

Voltage Gain vs Duty Ratio plot:

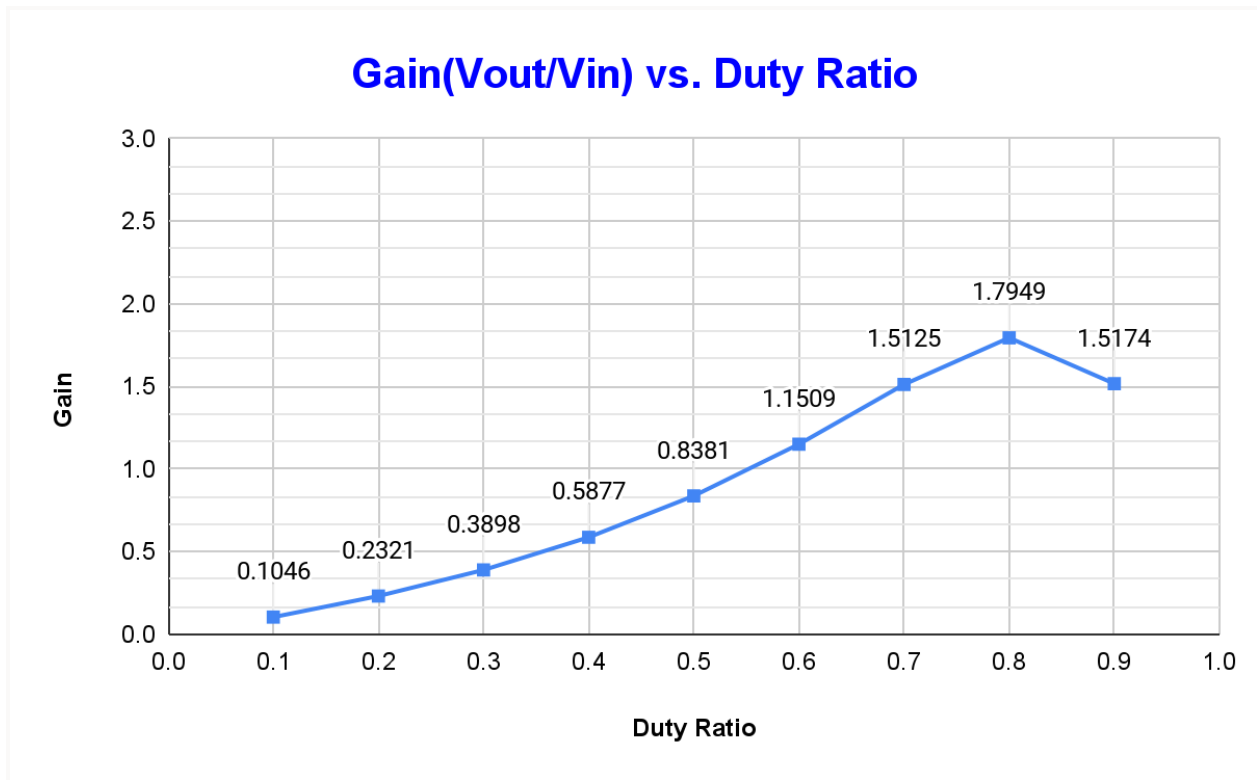

Due to parasitic resistance, power is dissipated through the inductor, so gain doesn't increase exponentially in this case. Also, for high duty ratio gain eventually decreases as inductor current is inversely proportional to  $(1-D)$  so it dissipates an increasing amount of power.

## II.

Case(i):  $V_{in} = 57V$ ,  $C = 54\mu F$ ,  $R_{Load} = 11.52\Omega$ ,  $L = 226\mu H$ ,  $R_L = 0\Omega$ ,  
Duty ratio( $D$ ) = 0.457

We know that,

When **buck-boost converter** operates in CCM,

$$Gain = \frac{D}{1-D} \text{ (without considering the sign of output voltage)}$$

And, when it operates in DCM,

$$Gain = \frac{V_{in} D^2 T_{sw}}{2LI_{out}}$$

So in the limiting region both the gains will be the same.

Putting  $I_{out} = \frac{V_{out}}{R_{Load}}$  and solving we get,

$$f_{sw} = \frac{1}{T_{sw}} = \frac{R_{Load}(1-D)^2}{2L}$$

So theoretically DCM to CCM transition happens at  $f_{sw}=7.515\text{KHz}$  when parasitic resistance of the inductor is 0.

We have already seen that at  $f_{sw}=50\text{KHz}$  the converter operates in CCM as the gain formula of  $\frac{D}{1-D}$  was the same as the observed gain.

Now we will vary the switching frequency from 5KHz to 10KHz to find the transition of DCM to CCM by observing the minimum current through the inductor in steady state. If it reaches 0, then the converter will operate in DCM.

$f_{sw}(\text{KHz})$	$I_{L,min}(\text{A})$	Mode	$f_{sw}(\text{KHz})$	$I_{L,min}(\text{A})$	Mode
5	-0.058(<0)	DCM	7.4	-0.008(<0)	DCM
6	-0.054(<0)	DCM	7.5	0.047	CCM
7	-0.049(<0)	DCM	7.6	0.1528	CCM
8	0.5528	CCM	7.8	0.2679	CCM
9	1.302	CCM			
10	2.059	CCM			
7.2	-0.042(<0)	DCM			

Hence, we observe that around 7.5KHz  $f_{sw}$  , the converter will transition from DCM to CCM.

Case(i):  $V_{in} = 57V$ ,  $C = 54\mu F$ ,  $R_{Load} = 11.52\Omega$ ,  $L=226\mu H$ ,  $R_L=0.576\Omega$ , Duty ratio(D) = 0.457

As observed before, this converter operates in CCM at 50KHz switching frequency.

We will vary the switching frequency from 5KHz to 10KHz to find the transition of DCM to CCM by observing the minimum current through the inductor in steady state. If it reaches 0, then the converter will operate in DCM.

$f_{sw}(KHz)$	$I_{L,min}(A)$	Mode	$f_{sw}(KHz)$	$I_{L,min}(A)$	Mode
5	-0.037(<0)	DCM	8.2	0.0771	CCM
6	-0.032(<0)	DCM	8.1	0.0100	CCM
7	-0.031(<0)	DCM			
8	-0.0087(<0)	DCM			
9	0.6599	CCM			
10	1.255	CCM			

So, from the table, we can conclude that around 8-8.1KHz switching frequency the converter transitions from DCM to CCM.



### III.

Case(i):  $V_{in} = 57V$ ,  $C = 54\mu F$ ,  $R_{Load} = 11.52\Omega$ ,  $f_{sw} = 50KHz$ ,  
 $L = 226\mu H$

Parasitic resistance  $R_L = 0\Omega$

(Average input and output current measurement)

Duty ratio(D)	Input current(A)	Output current(A)
0.1	0.2454	0.5498
0.2	0.5567	1.238
0.3	1.278	2.124
0.4	2.272	3.310
0.5	5.027	4.946
0.6	11.34	7.416
0.7	23.05	11.55
0.8	66.06	19.78
0.9	295.9	44.58

### Part-C

For following operating condition(i.e. Input Voltage( $V_{in}$ ) = 110V, Load voltage =48V, Inductance = 115 $\mu H$  Capacitance  $C = 50\mu F$ , Load resistance  $R_L = 11.52\Omega$ , Switching Frequency =50kHz, CCM and steady-state operation) compare the following between **buck** and **buck-boost converter**: voltage and current stress of switch and diode, inductor current ripple, output voltage ripple (save waveforms).

Given operating condition:

$V_{in} = 110V$ ,  $R_{Load} = 11.52\Omega$ ,  $L = 115\mu H$ ,  $C = 50\mu F$ ,  $f_{sw} = 50KHz$

$V_{out} = 48V$ , Hence,


$$D_{buck} = \frac{48}{110}$$

$$D_{buck-boost} = \frac{48}{158}$$


Both converters are operating in CCM condition.

MOSFET Switch voltage stress:

Buck converter- (Stress = 110V)

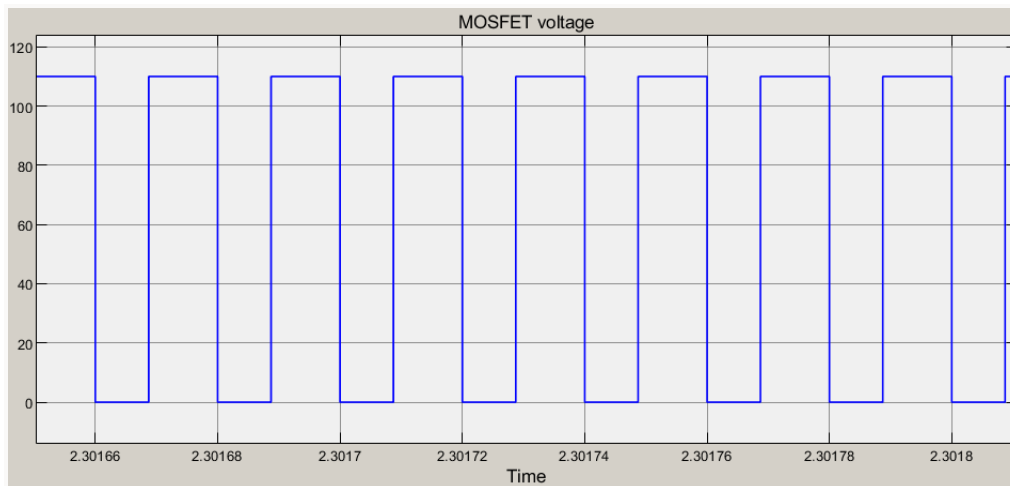


Buck-boost converter- (Stress = 158.4V)

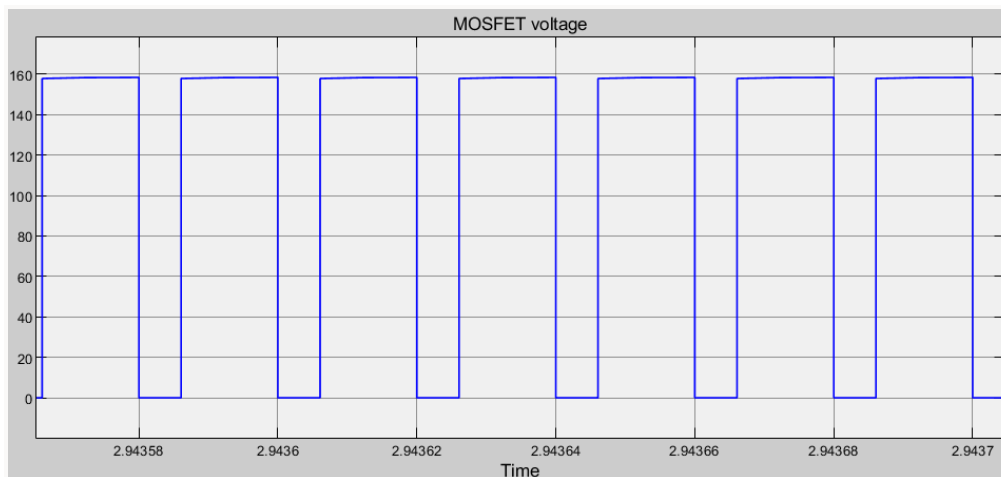


So a buck-boost converter switch has higher voltage stress than a buck converter in given operating condition.

## MOSFET Switch current stress:

Buck converter-  
Stress = 6.641A

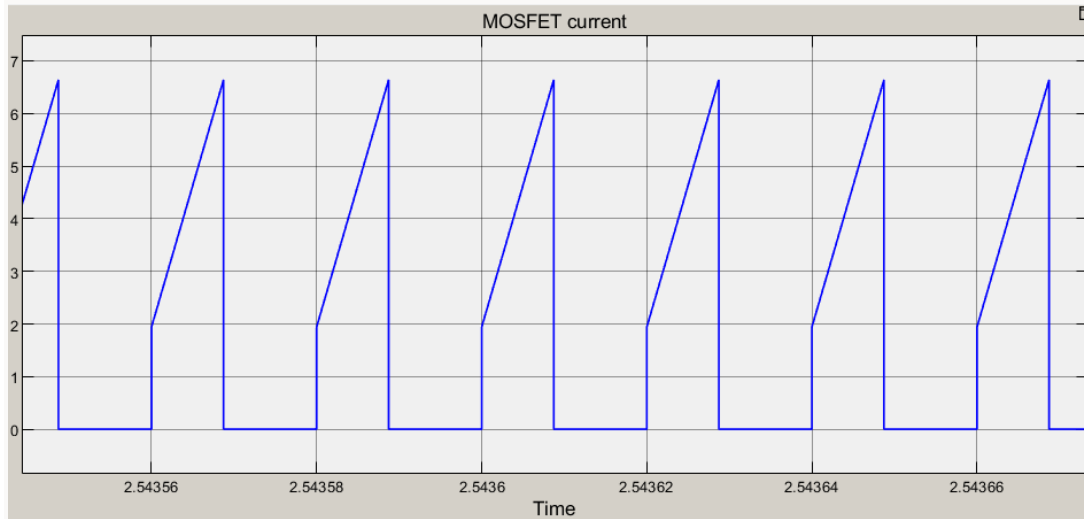

Buck-boost converter-  
Stress = 9.225A

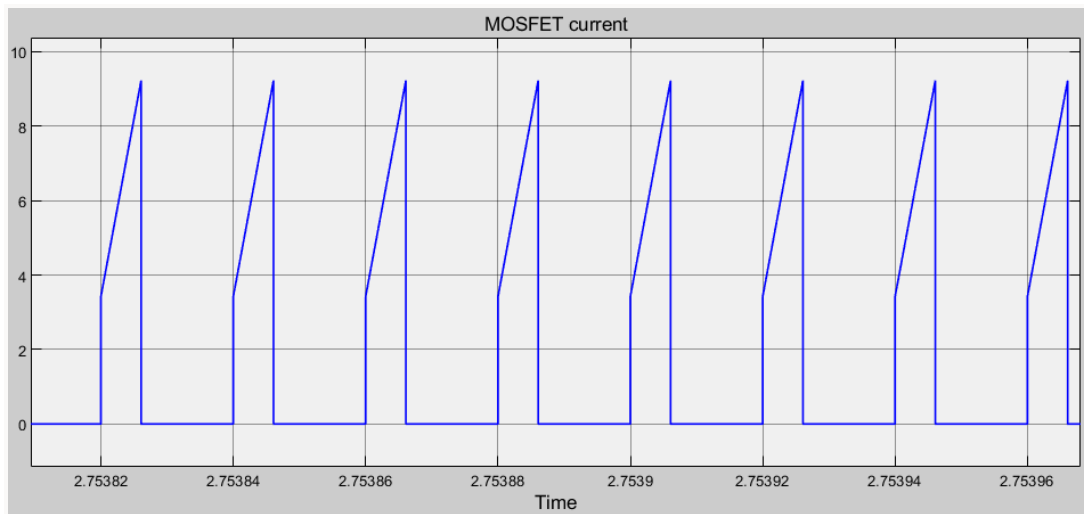


So a buck-boost converter switch has higher current stress than a buck converter in given operating condition.

## Diode voltage stress:


Buck converter-

Stress = 110V

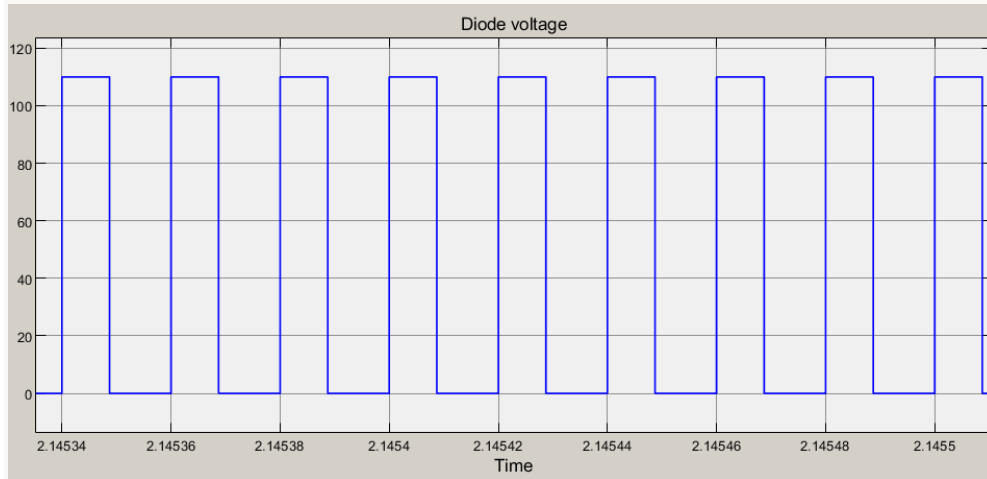

Buck-boost converter-

Stress = 158.4V

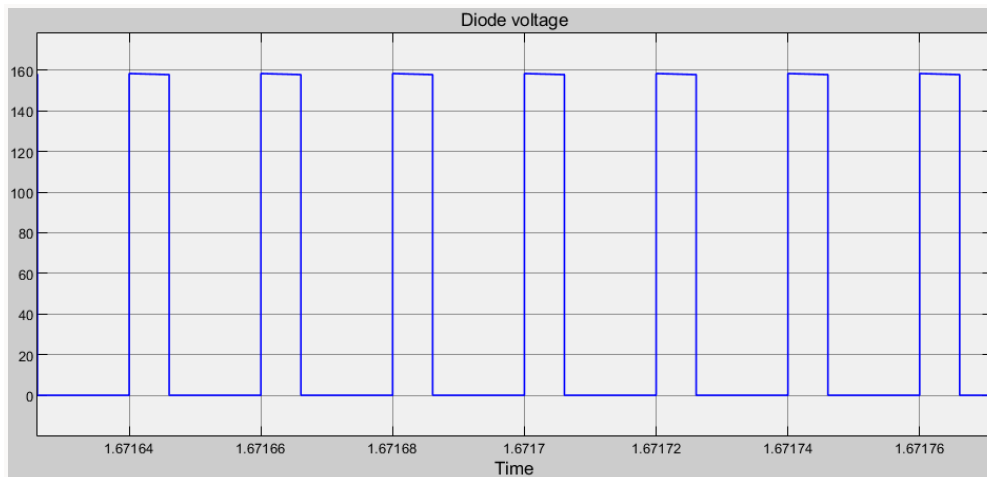


So a buck-boost converter diode has higher voltage stress than a buck converter in given operating condition.

## Diode Current Stress:


Buck converter-

Stress = 6.6483A

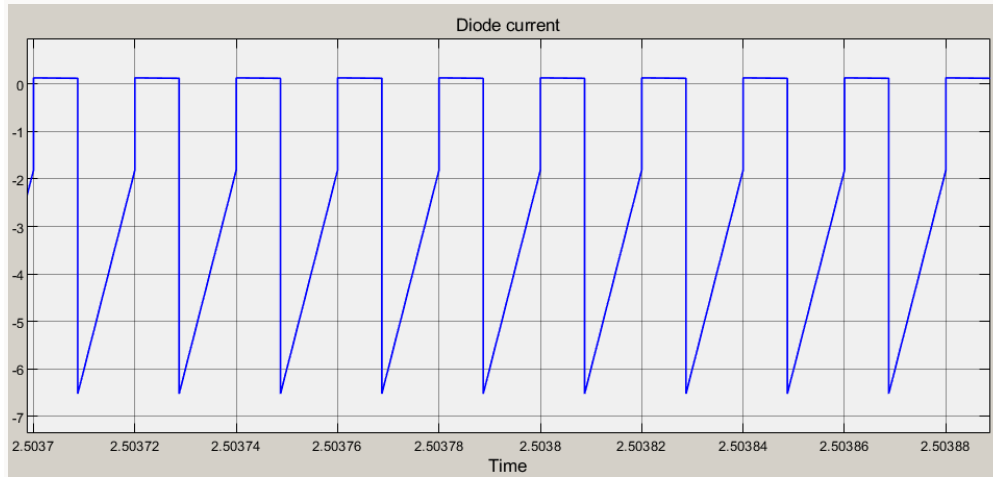

Buck-boost converter-


Stress = 9.2347A

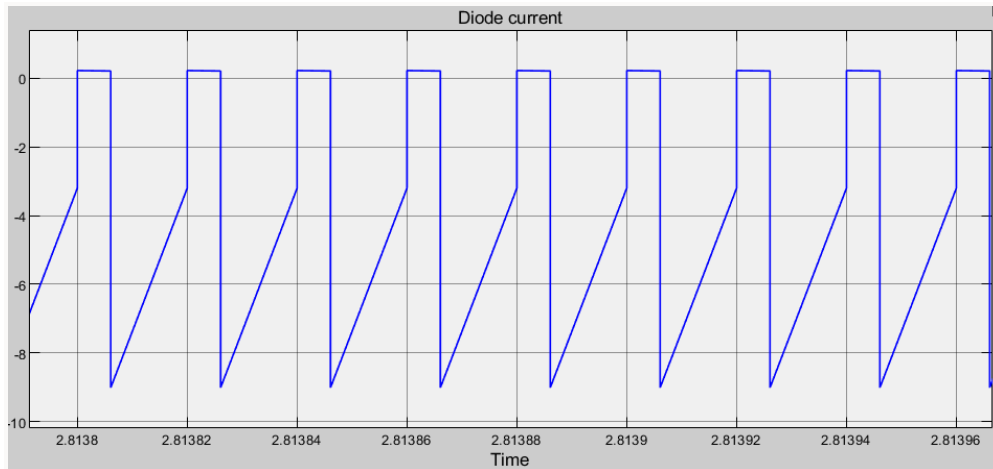


So a buck-boost converter diode has higher current stress than a buck converter in given operating condition.

Inductor current ripple:

Buck converter-  
Ripple = 4.706A

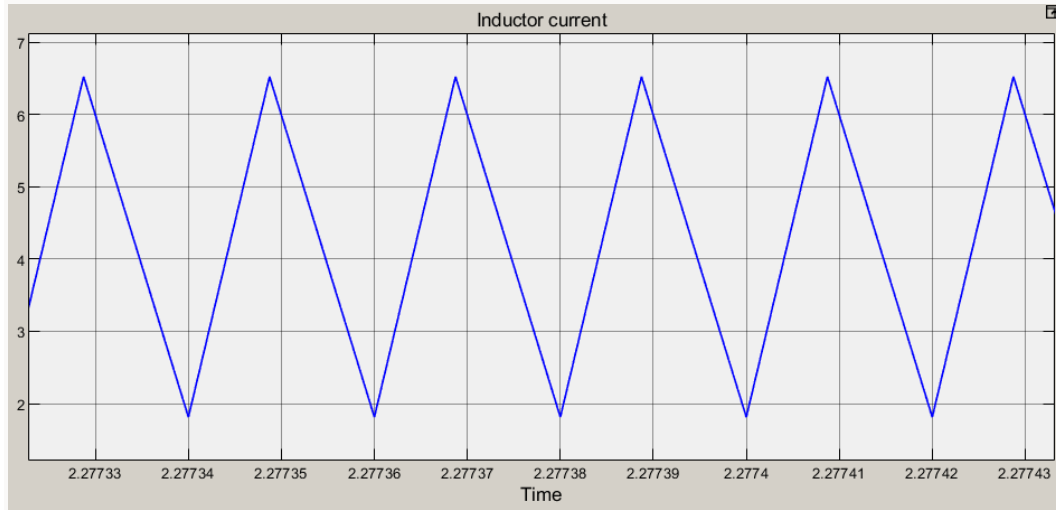

Buck-boost converter-  
Ripple = 5.812A

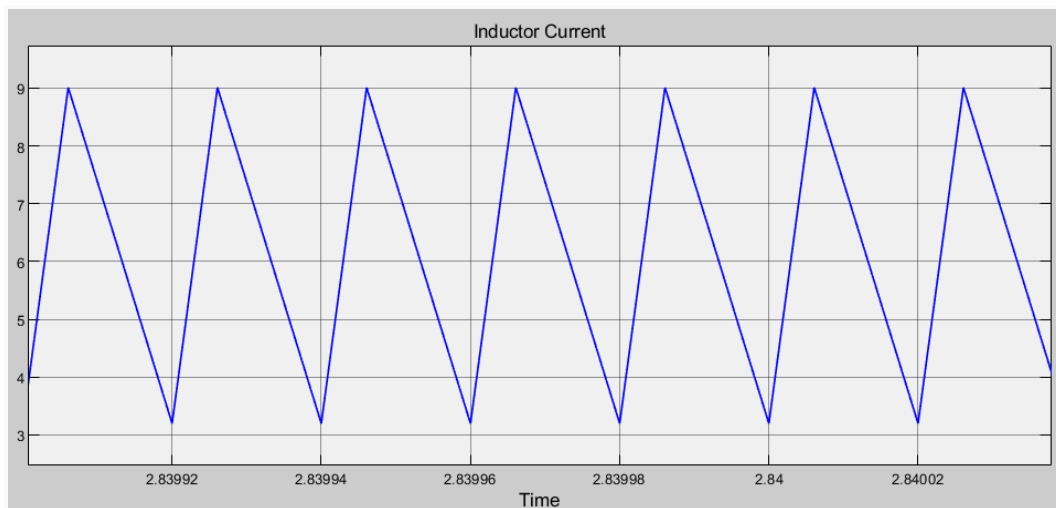


So, a buck-boost converter has higher inductor current ripple than buck converter in given operating condition.

Output voltage ripple:

Buck converter-


Ripple = 0.09286V

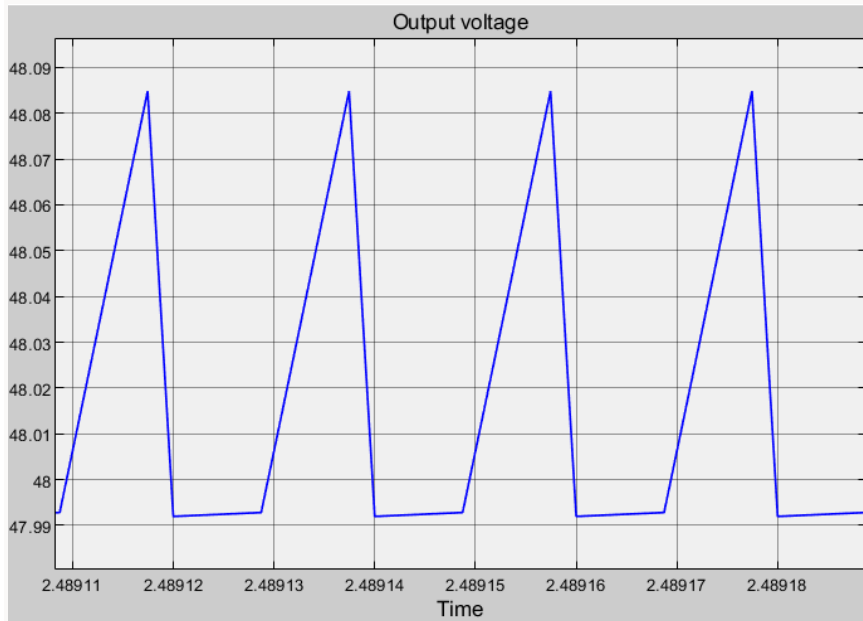

Buck-boost converter-

Polarity is opposite but only magnitude is considered here.

Ripple = 0.5343V

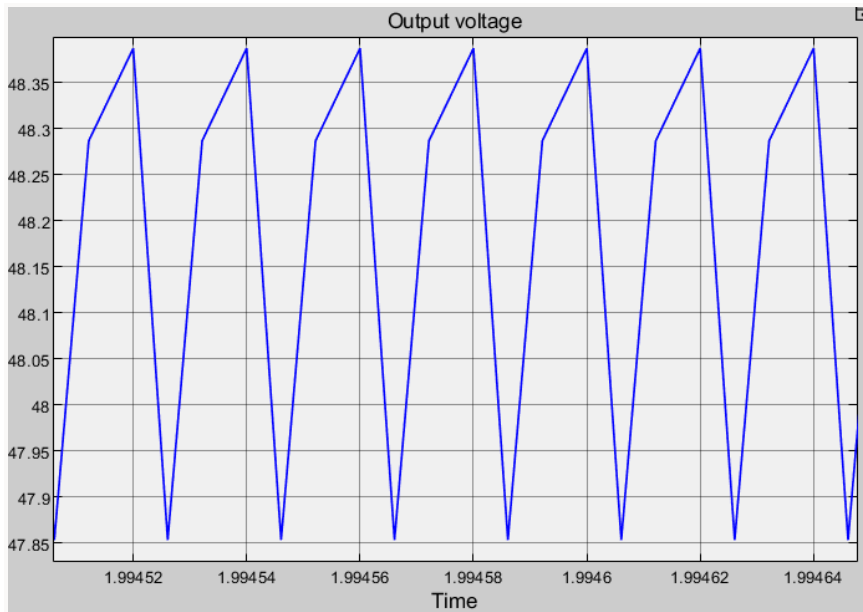

So, a buck-boost converter has higher output voltage ripple than buck converter in given operating condition.

## **Discussion:-**

- 1. For a given duty ratio and load, voltage gain is higher in DCM or CCM? Why?**
- 2. If all other parameters of a buck converter are kept the same, and only the switching frequency is varied, what will be its impact on converter performance?**

Keeping all other parameters the same, if we decrease the switching frequency, the inductor current ripple in the converter will increase, which also increases the output voltage ripple. Eventually the converter will move from CCM to DCM. After that, decreasing the switching frequency will increase gain of the converter but the output voltage ripple will also become much higher.

- 3. If all other parameters of a buck converter are kept the same, and only the load resistance is varied, what will be its impact on converter performance?**