



Question 11.14)

$$\text{given, } G_1(\text{machine}) = 50 \text{ MVA}$$

$$G_2(\text{machine}) = 100 \text{ MVA}$$

$$G(\text{system}) = 100 \text{ MVA}$$

$$H_1(\text{machine}) = 5 \text{ MJ/MVA}$$

$$H_2(\text{machine}) = 3 \text{ MJ/MVA}$$

$$n_1 = 4, n_2 = 3$$

so equivalent inertia for combined system
will be

$$\begin{aligned} H_{\text{eq}} &= n_1 \times \left(\frac{G_1(\text{machine})}{G(\text{system})} \right) H_1, \text{machine} \\ &\quad + n_2 \times \left(\frac{G_2(\text{machine})}{G(\text{system})} \right) \times H_2, \text{machine} \\ &= 4 \times \left(\frac{50}{100} \right) \times 5 + 3 \times \left(\frac{100}{100} \right) \times 3 \end{aligned}$$


$$H_{\text{eq}} = 19 \text{ MJ/MVA}$$




Date _____ / _____ / _____

Exercise 10


(Q) 10.1)

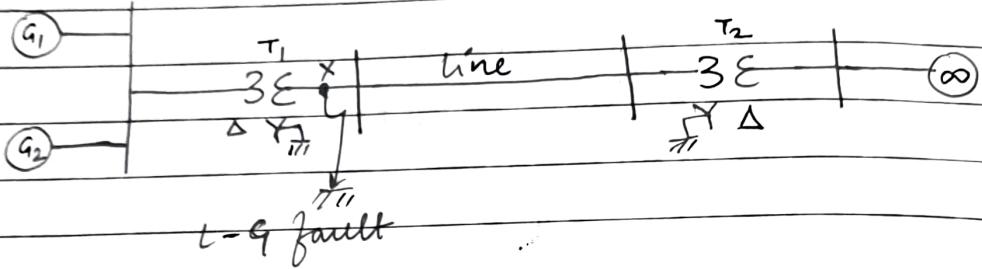


a) +ve sequence network -

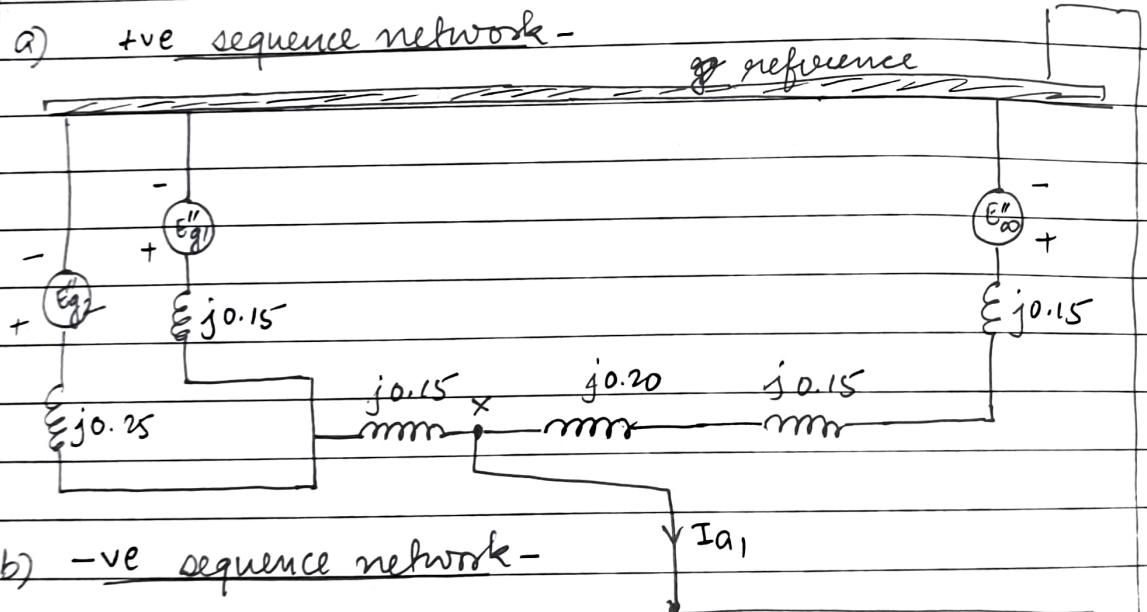

b) -ve sequence network -

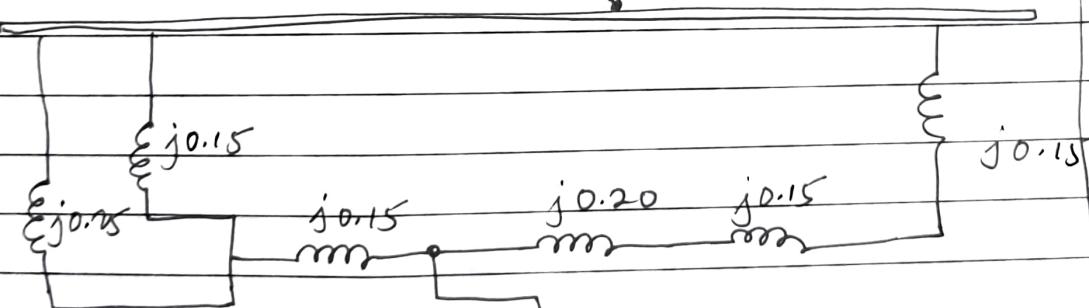

c) zero sequence network -

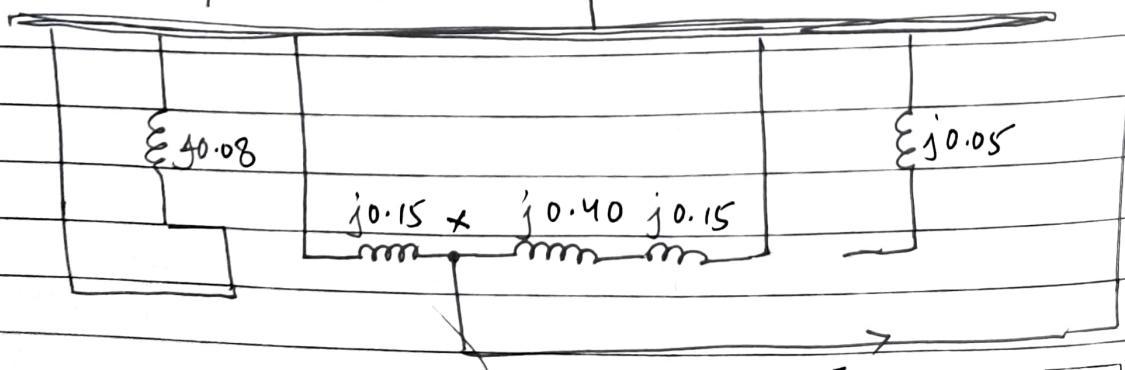



b) Both generators and infinite bus operate at 1 pu voltage

~~so, equivalent voltage across parallel branches~~

$$E_a = 1.0 \text{ pu}$$

let Z_1 = thevenin impedance of +ve sequence

$Z_2 = " "$ of -ve sequence

$Z_0 = " "$ of zero sequence

$$\text{so } Z_1 = \left[\left(j0.15 \parallel j0.25 \right) + j0.15 \right] \parallel \left[j0.20 + j0.15 + j0.15 \right]$$

$\approx 0.937j$ $0.2437j$ $j0.50$

$$= j0.163$$

$$Z_2 = Z_1 = j0.163$$


$$Z_0 = (j0.15) \parallel (j0.55) = j0.1178$$

$$I_{a1} = \frac{E_a}{Z_1 + Z_2 + Z_0} = -j2.253 = I_{ao}$$

$$\text{so fault current, } I_f = 3I_{ao} = \underline{\underline{-j6.759 \text{ pu}}}$$



Date ___ / ___ / ___

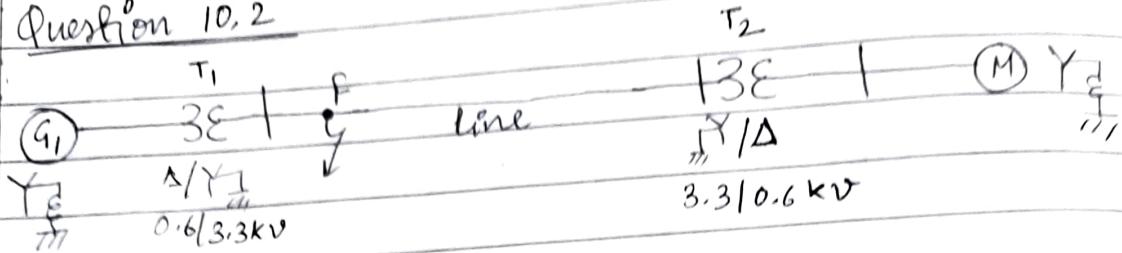Question 10.2

Double line to ground fault
To find fault current in phase C of G_1

Machines $\rightarrow 1.2 \text{ MVA}, 0.6 \text{ kV}, x_1 = x_2 = 0.1 \text{ pu}, x_{00} = 0.05 \text{ pu}$

$T_1, T_2 \rightarrow 1.2 \text{ MVA}, 0.05 \text{ pu}$ leakage reactance


Line $\rightarrow x_{L1} = x_{L2} = 0.2 \text{ pu}, x_{L0} = 0.40 \text{ pu}$
 $1.2 \text{ MVA}, 3.3 \text{ kV}$ base

$$x_n = 0.5 \text{ pu}$$

Ans)

+ve sequence network -

ground reference

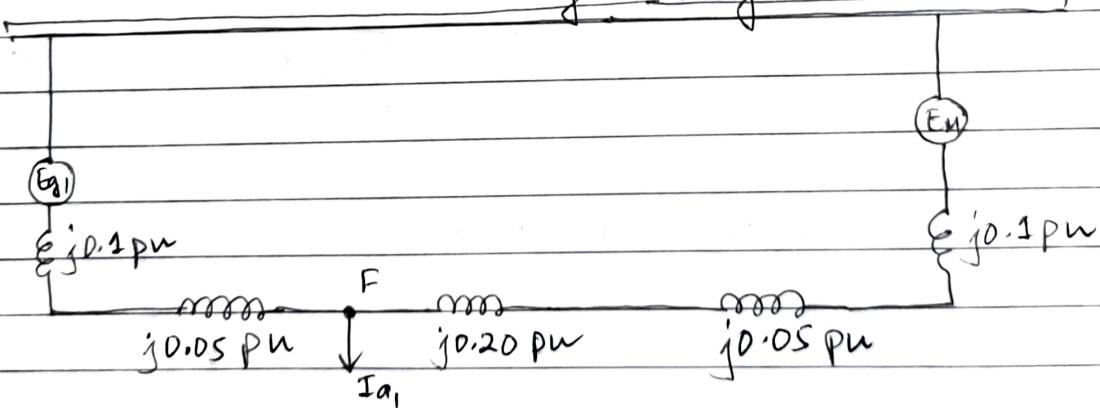


$$\begin{aligned} Z_1 &= \text{Thevenin equivalent reactance for +ve sequence} \\ &= (j0.1 + j0.05) || (j0.2 + j0.05 + j0.1) \text{ pu} \\ &= j0.105 \text{ pu} \end{aligned}$$

so $Z_1 = j0.105 \text{ pu} = Z_2$

Date _____

zero sequence network -

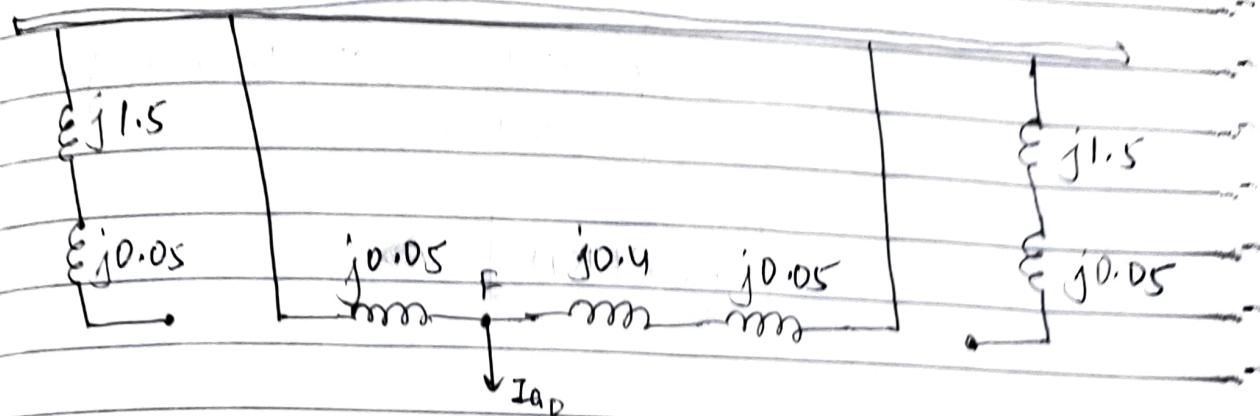

$$Z_0 = (j0.05) \parallel (j0.4 + j0.05)$$

$$Z_0 = j0.045$$

now, $I_{a1} = \frac{E_a}{Z_1 + \frac{Z_2 Z_0}{Z_2 + Z_0}} \quad (Z_b = 0)$

using the values of Z_1, Z_2 and Z_0 and $E_a = 1 \text{ pu}$

$$I_{a1} = -j7.32 \text{ pu}$$

$$I_{a2} = -\frac{(E_a - I_{a1} Z_1)}{Z_2} = j2.20 \text{ pu}$$

$$I_{a0} = -\frac{(E_a - I_{a1} Z_1)}{Z_0} = j5.142 \text{ pu}$$

now, $I_c = \frac{1}{3} [\beta I_{a1} + \beta^2 I_{a2} + I_{a0}]$

$$= \frac{1}{3} [(j-7.32) \angle 120^\circ + j2.20 \angle 240^\circ + j5.142]$$

$$I_c = 3.76 \angle 43^\circ \text{ pu}$$

P.T.D

no component of phase C current in I_1

$$= I_C \times \left(\frac{0.35}{0.35 + 0.15} \right) \times \left(\frac{1.2 \times 10^6}{0.6 \times 10^3} \right) A$$


$$= \boxed{5.264 \text{ KA}}$$

19EE10026


HARSH KUMAR JHA




Date _____

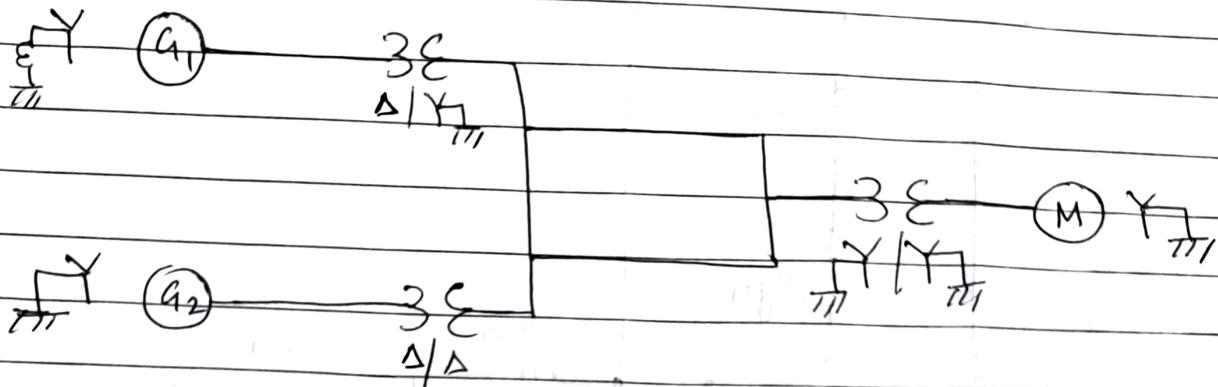Question 9.4)

• +ve sequence -

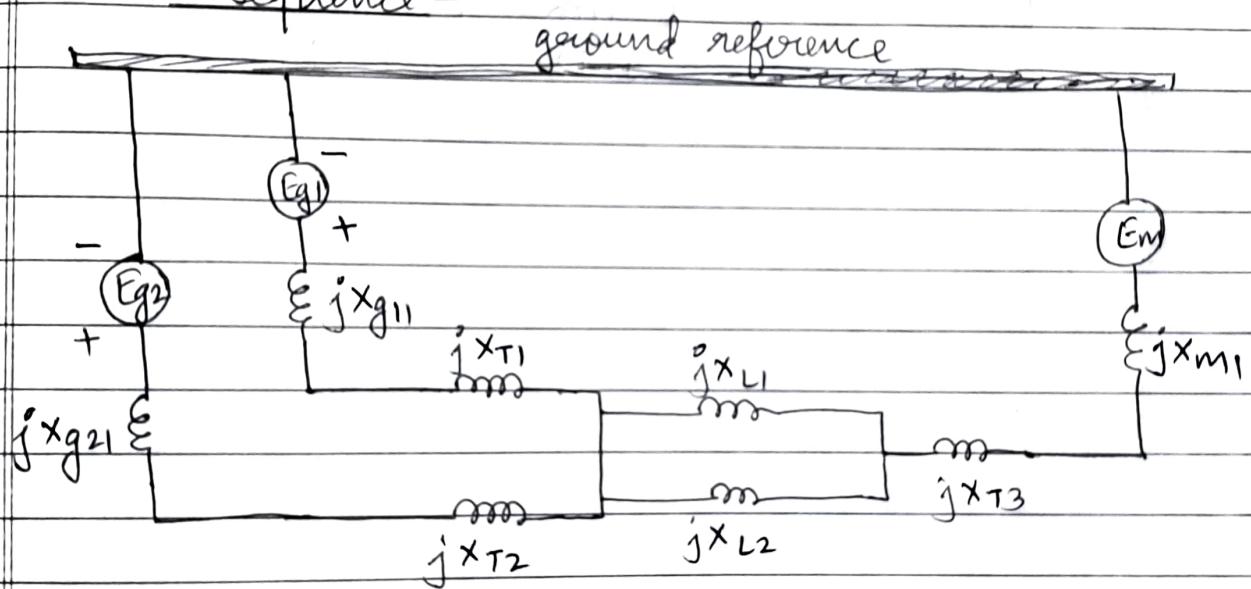


• -ve sequence -



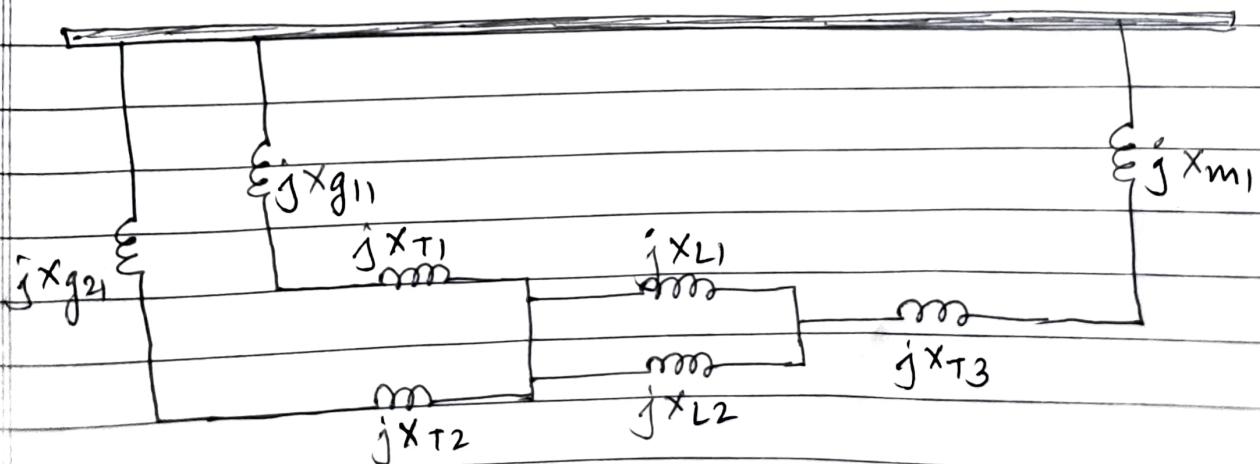





- zero sequence -

ground reference

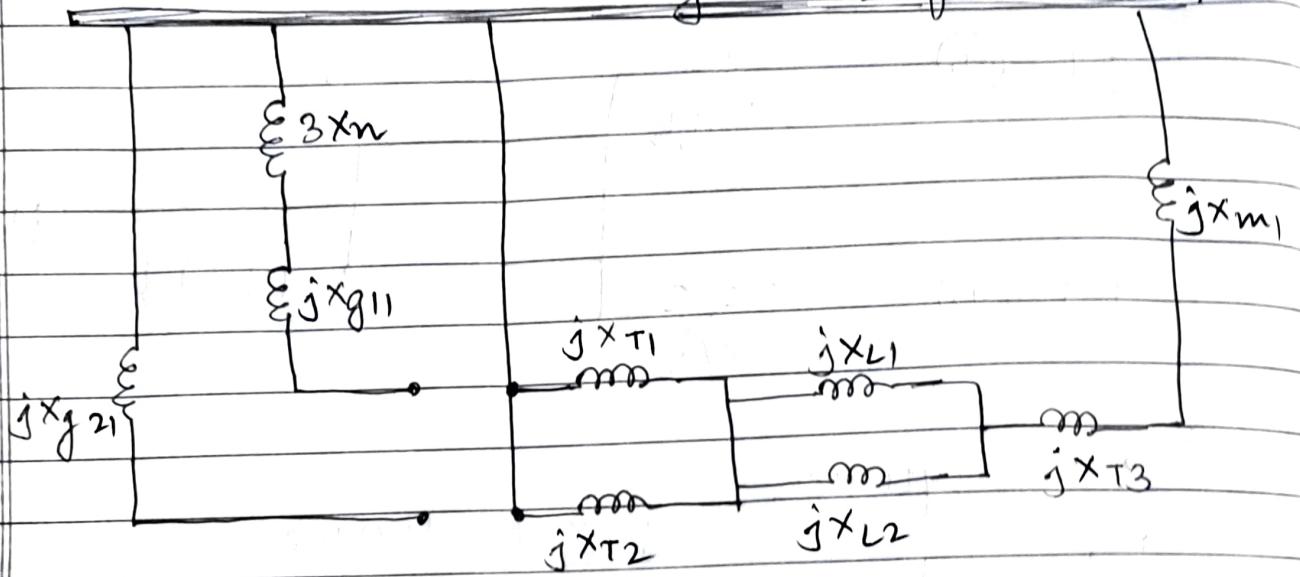

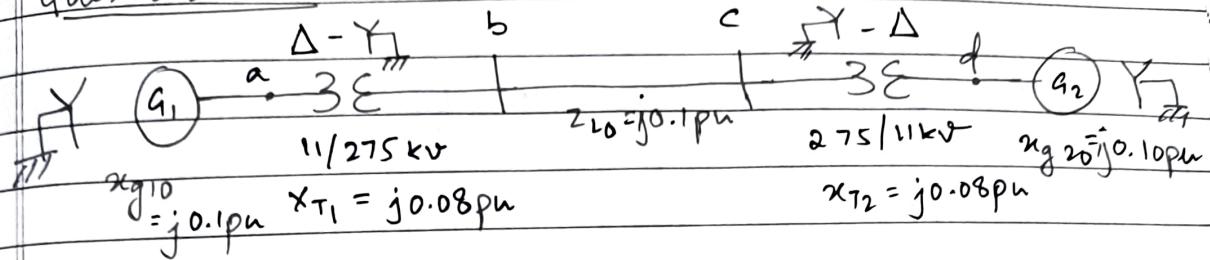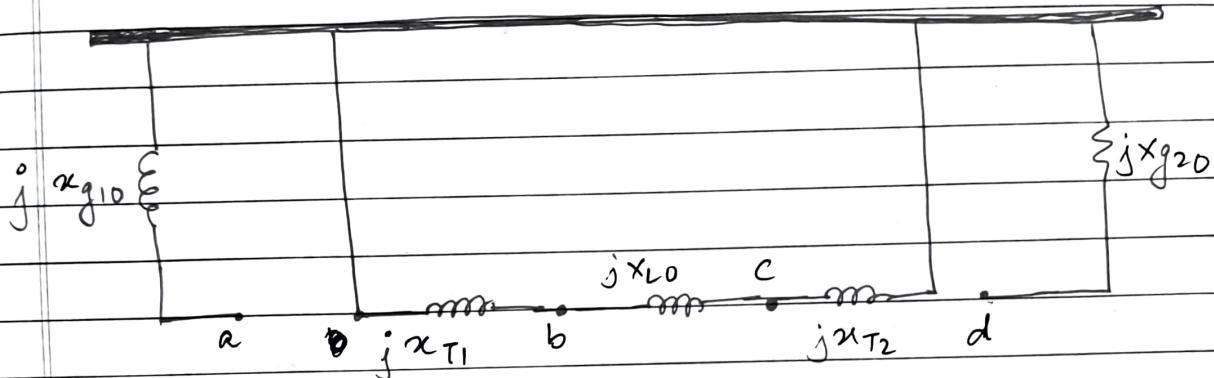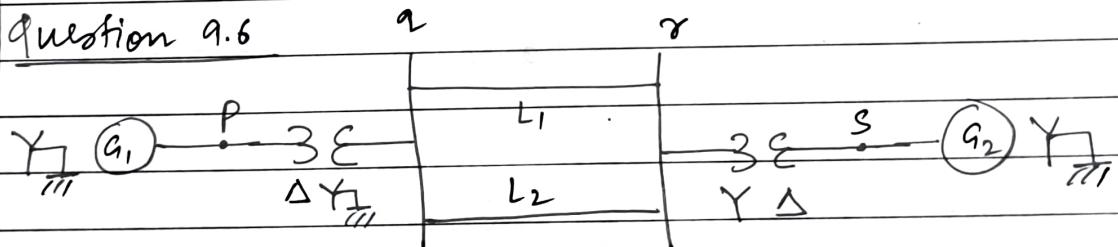
Question 9.5zero sequence network -Question 9.6zero sequence network -

ground

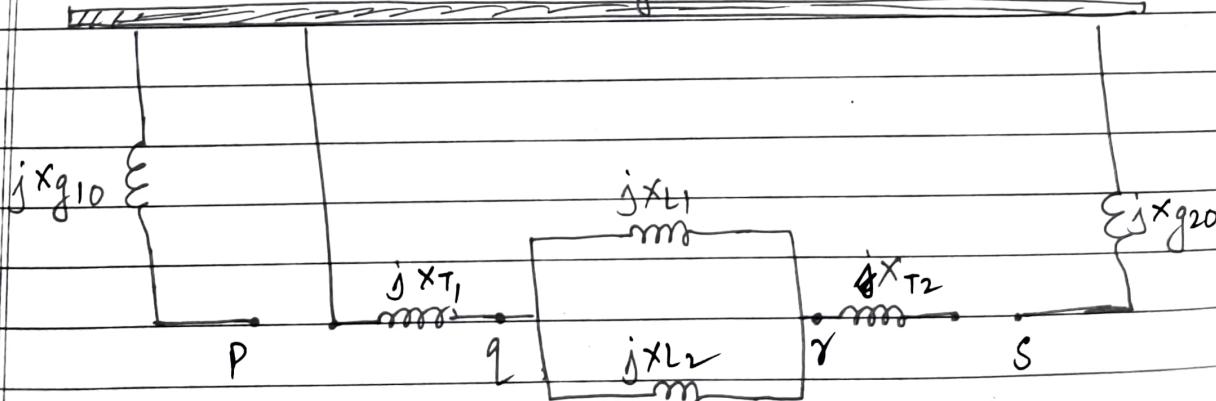



Date / /

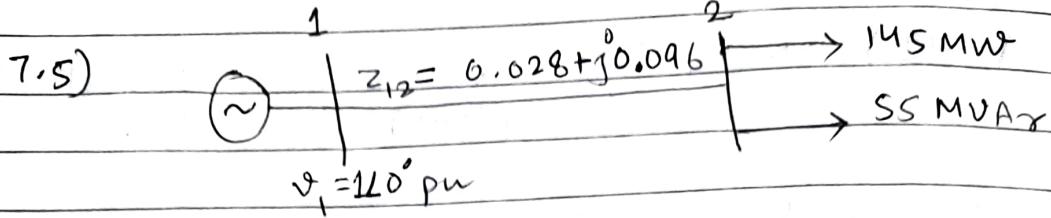

assuming base = 100 MVA

$$Y_{12} = \frac{1}{Z_{12}} = Y_{21} = 10 L - 73.74^\circ$$

$$Y_{10} = 0, Y_{20} = 0$$

$$Y_{11} = Y_{10} + Y_{12} = 10 L - 73.74^\circ$$

$$Y_{22} = Y_{20} + Y_{21} = 10 L - 73.74^\circ$$

$$Y_{12} = Y_{21} = -Y_{12} = 10 L 106.26^\circ$$

$$\text{now } Y_{bus} = \begin{bmatrix} 10 L - 73.74^\circ & 10 L 106.26^\circ \\ 10 L 106.26^\circ & 10 L - 73.74^\circ \end{bmatrix}$$

$$P_2 = \sum_{j=1}^2 |V_2| |V_j| |Y_{2j}| \cos(\theta_{2j} - \delta_2 + \delta_j)$$

$$\frac{\partial P_2}{\partial \delta_2} = \sum_{k=1}^2 |V_2| |V_k| |Y_{2k}| \sin(\theta_{2k} - \delta_2 + \delta_k) \\ = |V_2| |V_1| |Y_{21}| \sin(\theta_{21} - \delta_2 + \delta_1)$$

$$\frac{\partial P_2}{\partial |V_2|} = 2 |V_2| |V_1| |Y_{21}| \cos(\theta_{22}) + |V_1| |Y_{21}| \cos(\theta_{12} - \delta_2 + \delta_1)$$

$$\frac{\partial \theta_2}{\partial \delta_2} = |V_2| |V_1| |Y_{21}| \cos(\theta_{21} - \delta_2 + \delta_1)$$

$$\frac{\partial \theta_2}{\partial |V_2|} = - |V_1| |Y_{21}| \sin(\theta_{21} - \delta_2 + \delta_1) - 2 |V_2| |Y_{22}| \sin(\theta_{22})$$

(δ_1)

$$\text{slack voltage} = 1 \angle 0^\circ \text{ pu} = V_1$$

$$|V_2^{(0)}| = 1.0, \quad \delta_2^{(0)} = 0$$

$$S_2^{\text{sch}} = -\left(\frac{145 + j55}{100}\right) \text{ pu} = -1.45 - 0.55j \text{ pu}$$

$$P_2^{(0)} = 10 \cos(106.26^\circ - 0 + 0) + 10 \cos(-73.74^\circ) \\ = 0$$

$$\Rightarrow \Delta P^{(0)} = P^{\text{sch}} - P_2^{(0)} = -1.45 \text{ pu}$$

$$Q_2^{(0)} = -10 \sin(106.26^\circ) - 10 \sin(-73.74^\circ) = 0$$

$$\Rightarrow \Delta Q^{(0)} = -0.55 \text{ pu}$$

Jacobian elements -

$$J_1^{(0)} = \left(\frac{\partial P_2}{\partial \delta_2} \right)^{(0)} = 10 \sin(106.26^\circ) = 9.6$$

$$J_2^{(0)} = \left(\frac{\partial P_2}{\partial |V_2|} \right)^{(0)} = 2 \times 10 \cos(-73.74^\circ) + 10 \cos(106.26^\circ) \\ = 2.8$$

$$J_3^{(0)} = \left(\frac{\partial Q_2}{\partial \delta_2} \right)^{(0)} = 10 \cos(106.26^\circ) = -2.8$$

$$J_4^{(0)} = \left(\frac{\partial Q_2}{\partial |V_2|} \right)^{(0)} = 9.6$$

$$\therefore \begin{bmatrix} \Delta P_2^{(0)} \\ \Delta Q_2^{(0)} \end{bmatrix} = \begin{bmatrix} 9.6 & 2.8 \\ -2.8 & 9.6 \end{bmatrix} \begin{bmatrix} \Delta S_2^{(0)} \\ \Delta |V_2|^{(0)} \end{bmatrix}$$

$$\Rightarrow \begin{bmatrix} -1.45 \\ -0.55 \end{bmatrix} = \begin{bmatrix} 9.6 & 2.8 \\ -2.8 & 9.6 \end{bmatrix} \begin{bmatrix} \Delta S_2^{(0)} \\ \Delta |V_2|^{(0)} \end{bmatrix}$$



$$\Rightarrow \Delta \delta_2^{(0)} = -0.1238 \Rightarrow \delta_2^{(1)} = 0 - 0.1238 = -0.1238$$

$$\Delta |v_2|^{(0)} = -0.0934 \Rightarrow |v_2|^{(1)} = 1 - 0.0934 = 0.9066$$

now,

$$P_2^{(1)} = 0.9066 \times 10 \times \cos(106.26^\circ + 0.1238 \times 180/\pi) \\ = -1.29 \text{ pu}$$

$$Q_2^{(1)} = -0.9066 \times 10 \sin(106.26^\circ + 0.1238 \times 180/\pi) \\ = -0.433 \text{ pu}$$

$$\therefore \Delta P^{(1)} = -1.45 + 1.29 = -0.16 \text{ pu}$$

$$\Delta Q^{(1)} = -0.55 + 0.433 = -0.117 \text{ pu}$$


$$\begin{bmatrix} \Delta \delta_2^{(1)} \\ \Delta |v_2|^{(1)} \end{bmatrix} = J^{-1} \begin{bmatrix} -0.16 \\ -0.117 \end{bmatrix} = \begin{bmatrix} -0.012084 \\ -0.015712 \end{bmatrix}$$

$$\therefore \delta_2^{(2)} = -0.1238 - 0.012084 = -0.1359 \text{ pu}$$

$$v_2^{(2)} = 0.9066 - 0.015712 = 0.891 \text{ pu}$$

so voltage after 2 iteration = ~~0.891~~ 0.891 pu

δ at bus after 2 iteration = -0.1359 rad

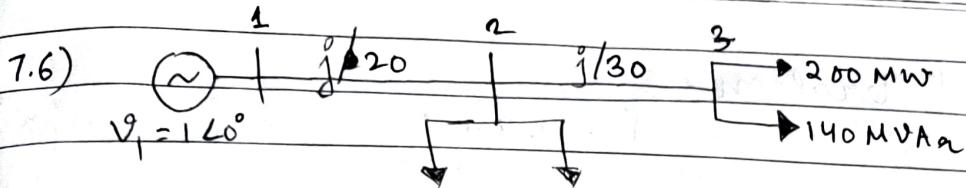

$$Y_{12} = 20 \text{ } \angle 20^\circ = -20 \text{ } \angle 20^\circ, \quad Y_{13} = 0, \quad Y_{23} = -30 \text{ } \angle 30^\circ$$

$$Y_{10} = Y_{20} = Y_{30} = 0$$

$$Y_{11} = Y_{10} + Y_{12} + Y_{13} = -20 \text{ } \angle 20^\circ$$

$$Y_{22} = Y_{20} + Y_{12} + Y_{23} = -50 \text{ } \angle 30^\circ$$

$$Y_{33} = Y_{30} + Y_{13} + Y_{23} = -20 \text{ } \angle 30^\circ$$

$$Y_{12} = Y_{21} = 20 \text{ } \angle 20^\circ, \quad Y_{23} = Y_{32} = 30 \text{ } \angle 30^\circ, \quad Y_{13} = Y_{31} = 0$$

a) GS method -

$$S_2^{\text{Sch}} = -\frac{j60 - 90}{100} = -0.9 - 0.6j \text{ pu} = P_2 + jQ_2$$

$$S_3^{\text{Sch}} = -\frac{200 - 140j}{100} = -2 - 1.4j = P_3 + jQ_3$$

$$\text{now, } v_2^{(P+1)} = \frac{1}{Y_{22}} \left[\frac{P_2 - jQ_2}{(v_2^{(P)})^*} - Y_{21} v_1 - Y_{23} v_3^{(P)} \right]$$

$$\text{and } v_3^{(P+1)} = \frac{1}{Y_{33}} \left[\frac{P_3 - jQ_3}{(v_3^{(P)})^*} - Y_{31} v_1 - Y_{32} v_2^{(P)} \right]$$

slack bus power \rightarrow

$$P_1 = \sum_{k=1}^3 |v_1| |v_k| |Y_{1k}| \cos(\theta_{1k} - \delta_1 + \delta_k)$$

$$Q_1 = -\sum_{k=1}^3 |v_1| |v_k| |Y_{1k}| \sin(\theta_{1k} - \delta_1 + \delta_k)$$

$$v_2^{(0)} = 1 + j0, \quad v_3^{(0)} = 1 + j0$$



Date _____ / _____ / _____

- - - 0,12

• 1st iteration-

$$v_2^{(1)} = \frac{1}{-50j} \left[\frac{-0.9 + 0.6j}{(v_2^{(0)})^*} - 20j - 30j \times v_3^{(0)} \right]$$

$$v_2^{(1)} = 0.988 L - 1.044^\circ$$

$$v_3^{(1)} = \frac{-1}{20j} \left[\frac{-2 + 1.4j}{1} - 0 - 30j v_2^{(0)} \right] = 1.433 L - 4^\circ$$

• 2nd iteration-

$$v_2^{(2)} = \frac{j}{50} \left[\frac{-0.9 + 0.6j}{0.988 L - 1.044^\circ} - 20j - 30j \times 1.433 L - 4^\circ \right]$$

$$= 1.247 L - 3.6^\circ$$

$$v_3^{(2)} = \frac{j}{20} \left[\frac{-2 + 1.4j}{1.433 L - 4^\circ} - 0 - 30j \times 0.988 L - 1.044^\circ \right]$$

$$= 1.433 L - 3.73^\circ$$

$$P_1 = |v_1|^2 |\gamma_{11}| \cos(\theta_{11} - \delta_1 + \phi_1) + |v_1| |v_2| |\gamma_{12}| \cos(\theta_{12} - \delta_1 + \phi_2) + |v_1| |v_3| |\gamma_{13}| \cos(\theta_{13} - \delta_1 + \phi_3)$$

$$\underline{P_1 = 1.566 \text{ pu}}$$

④ similarly, $\underline{\delta_1 = -4.89 \text{ pu}}$


$$\Rightarrow \boxed{S_1 = 1.566 \text{ pu} - j 4.89 \text{ pu} = (156.6 - j 489) \text{ MVA}}$$



Date _____ / _____ / _____

Q 6.11)

(i) series connection -

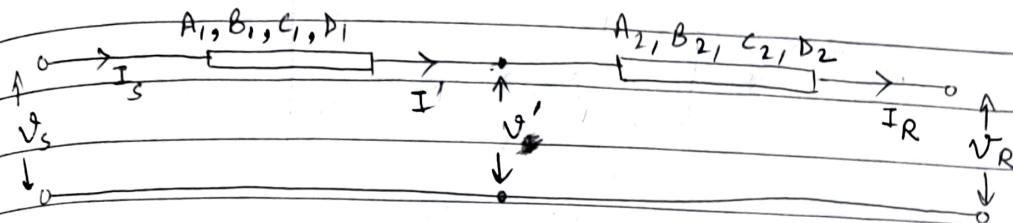

$$\begin{bmatrix} v_s \\ I_s \end{bmatrix} = \begin{bmatrix} A_1 & B_1 \\ C_1 & D_1 \end{bmatrix} \begin{bmatrix} v' \\ I' \end{bmatrix}$$

and $\begin{bmatrix} v' \\ I' \end{bmatrix} = \begin{bmatrix} A_2 & B_2 \\ C_2 & D_2 \end{bmatrix} \begin{bmatrix} v_R \\ I_R \end{bmatrix}$

$$\Rightarrow \begin{bmatrix} A_1 & B_1 \\ C_1 & D_1 \end{bmatrix}^{-1} \begin{bmatrix} v_s \\ I_s \end{bmatrix} = \begin{bmatrix} A_2 & B_2 \\ C_2 & D_2 \end{bmatrix} \begin{bmatrix} v_R \\ I_R \end{bmatrix}$$


$$\begin{aligned} n \begin{bmatrix} v_s \\ I_s \end{bmatrix} &= \begin{bmatrix} A_1 & B_1 \\ C_1 & D_1 \end{bmatrix} \begin{bmatrix} A_2 & B_2 \\ C_2 & D_2 \end{bmatrix} \begin{bmatrix} v_R \\ I_R \end{bmatrix} \\ &= \begin{bmatrix} A' & B' \\ C' & D' \end{bmatrix} \begin{bmatrix} v_R \\ I_R \end{bmatrix} \end{aligned}$$

$$\text{where } A' = A_1 A_2 + B_1 C_2, \quad B' = A_1 B_2 + B_1 D_2 \\ C' = A_2 C_1 + D_1 C_2, \quad D' = C_1 B_2 + D_1 D_2$$



Date / /

(ii) Parallel connection-

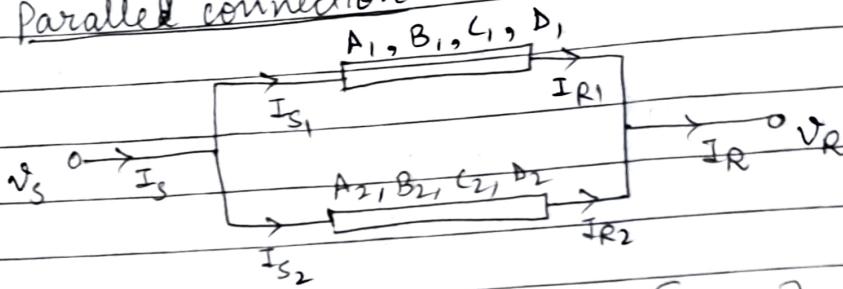

$$\begin{bmatrix} v_s \\ I_{S1} \end{bmatrix} = \begin{bmatrix} A_1 & B_1 \\ C_1 & D_1 \end{bmatrix} \begin{bmatrix} V_R \\ I_{R1} \end{bmatrix} \text{ and } \begin{bmatrix} v_s \\ I_{S2} \end{bmatrix} = \begin{bmatrix} A_2 & B_2 \\ C_2 & D_2 \end{bmatrix} \begin{bmatrix} V_R \\ I_{R2} \end{bmatrix}$$

$$\text{and } \begin{bmatrix} v_s \\ I_S \end{bmatrix} = \begin{bmatrix} A' & B' \\ C' & D' \end{bmatrix} \begin{bmatrix} V_R \\ I_R \end{bmatrix}$$

$$\text{and } I_S = I_{S1} + I_{S2}, \quad I_R = I_{R1} + I_{R2}$$

now, $v_s = A_1 V_R + B_1 I_{R1}$ and $v_s = A_2 V_R + B_2 I_{R2}$
 $I_{S1} = C_1 V_R + D_1 I_{R1}$ $I_{S2} = C_2 V_R + D_2 I_{R2}$

$$\Rightarrow \frac{v_s}{B_1} + \frac{v_s}{B_2} = V_R \left(\frac{A_1}{B_1} + \frac{A_2}{B_2} \right) + I_{R1} + I_{R2}$$

$$\Rightarrow v_s \left(\frac{B_1 + B_2}{B_1 B_2} \right) = V_R \left(\frac{A_1 B_2 + A_2 B_1}{B_1 B_2} \right) + I_R$$

or $v_s = \frac{(A_1 B_2 + A_2 B_1)}{B_1 + B_2} V_R + \frac{B_1 B_2}{B_1 + B_2} I_R$

and $I_S = I_{S1} + I_{S2} = V_R (C_1 + C_2) + I_R (D_1 + D_2)$

or $A' = \frac{A_1 B_2 + A_2 B_1}{B_1 + B_2}$ $B' = \frac{B_1 B_2}{B_1 + B_2}$

$C' = C_1 + C_2$

$D' = D_1 + D_2$

Date _____

Q 6.12) $\nu_R = 30 L^0 \text{ kV}$, $P_f = 0.8 \text{ lag}$, $P = 10 \text{ MW}$

(given)

let current in parallel lines be I_1 and I_2

now, $|I_R| = \frac{10 \text{ MW}}{\nu_R \times P_f} = \frac{10 \times 10^6}{30 \times 10^3 \times 0.8} = 416.67 \text{ A}$

~~and so~~ $I_R = 416.67 L - 36.87^\circ$
 $= I_1 + I_2$ ————— (1)

and $\nu_R + I_1 (5.5 + j13.5) = \nu_R + I_2 (6 + j11)$

$\Rightarrow I_1 = I_2 (6 + j11) = 0.87 L - 8.28^\circ \times I_2$
 $(5.5 + j13.5)$

from (1), $416.67 L - 36.87^\circ = I_2 [1 + 0.87 L - 8.28^\circ]$

$\Rightarrow I_2 = 224.42 L - 33.89^\circ \text{ A}$
 $I_1 = 192 L - 40.33^\circ \text{ A}$


$\Rightarrow P_2 = 30 I_2 \cos \phi = 5585 \text{ kW}$

$P_1 = 10 \text{ MW} - P_2 = 4415 \text{ kW}$

$(\text{kVA})_2 = 30 L^0 \times I_2 = 6732 L 33.89^\circ \text{ kVA}$

$(\text{kVA})_1 = 30 L^0 \times I_1 = 5787 L 40.33^\circ \text{ kVA}$

5.3)

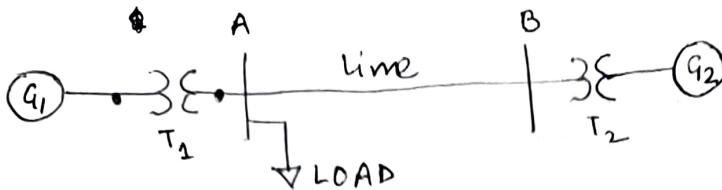

G_1 : 90 MVA, 20 kV, $x_{g1} = 0.09 \text{ pu}$

G_2 : 90 MVA, 18 kV, $x_{g2} = 0.09 \text{ pu}$

T_1 : 80 MVA, 20/200 kV, $x_{T_1} = 0.16 \text{ pu}$

T_2 : 80 MVA, 200/20 kV, $x_{T_2} = 0.20 \text{ pu}$

Line: 200 kV, $x_{\text{line}} = 120 \Omega$

Load: 200 kV, $S = (48 + j64) \text{ MVA}$

Base: 100 MVA, 20 kV

$$\text{Ans) } (MVA)_B = 100$$

Base kV for generator = 20 kV
 G_1 and G_2

Now, for $G_1 \rightarrow$

$$x_{g1(\text{new})} = 0.09 \times \frac{(MVA)_{B,\text{new}}}{(MVA)_{B,\text{old}}} \times \frac{(kV)_{B,\text{old}}^2}{(kV)_{B,\text{new}}^2}$$

$$= 0.09 \times \frac{100}{90} \times \frac{20^2}{20^2}$$

$$\boxed{x_{g1(\text{new})} = 0.1 \text{ pu}}$$

for $G_2 \rightarrow$

$$x_{g2(\text{new})} = 0.09 \times \frac{100}{90} \times \frac{18^2}{20^2}$$

$$\boxed{x_{g2(\text{new})} = 0.081 \text{ pu}}$$

$$\text{For } T_1 \rightarrow \\ x_{T_1, \text{new}} = 0.16 \times \frac{100}{80} \times \frac{20^2}{20^2}$$

$$x_{T_1, \text{new}} = 0.2 \text{ pu}$$

$$\text{For } T_2 \rightarrow \\ x_{T_2, \text{new}} = 0.20 \times \frac{100}{80} \times \frac{20^2}{20^2}$$

$$\Rightarrow x_{T_2, \text{new}} = 0.25 \text{ pu}$$

For line \rightarrow

$$(KV)_{B, \text{line}} = 20 \times \frac{200}{20} KV = 200 KV$$

$$Z_{B, \text{line}} = \frac{(KV)_{B, \text{line}}^2}{(MVA)_B} = \frac{200^2}{100} = 400 \Omega$$

$$\text{so } x_{\text{line}} = \frac{120}{400} \text{ pu} = 0.3 \text{ pu} = x_{\text{line}}$$

The load is given as $S = (48 + j64) \text{ MVA}$


Assuming series combination of resistance and inductance in load,

$$Z_{\text{load}} = \frac{(200)^2}{48 + j64} = 300 - 400j \Omega$$


$$\text{so, } Z_{\text{load, pu}} = \frac{Z_{\text{load}}}{Z_{B, \text{line}}} = \frac{300 - j400}{400} \\ = (0.75 - j1) \text{ pu}$$

$$\text{so } R_{\text{series}} = 0.75 \text{ pu} \\ X_{\text{series}} = j1 \text{ pu}$$

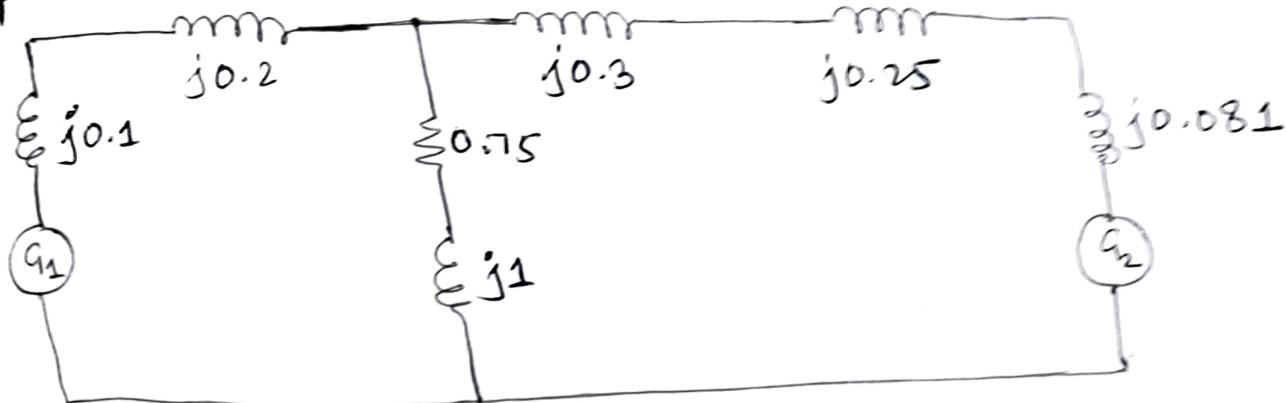~~Reactance~~
~~Impedance~~ diagram will be \rightarrow



Q.12)

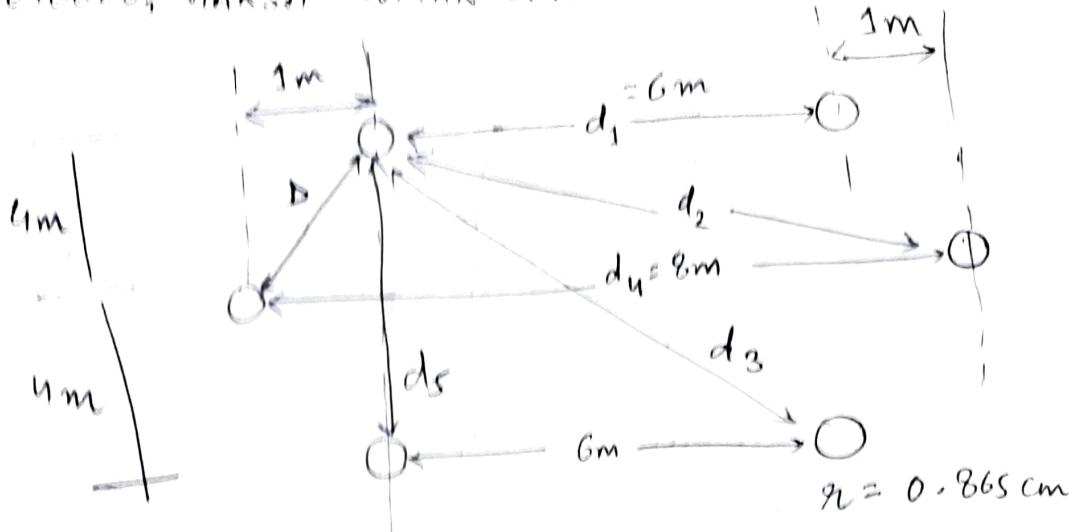

now, capacitance to neutral, $C_{AN} = \frac{0.0242}{\log\left(\frac{D_{eq}}{D_s}\right)}$ $\mu F/km$

now, $d_1 = 6m$ (given)

$$d_2 = \sqrt{4^2 + 7^2} = 8.062m$$

$$d_3 = \sqrt{8^2 + 6^2} = 10m$$

$d_4 = 8m$ (given)

$$D = \sqrt{4^2 + 1^2} = 4.123m$$

$$\text{now, } D_{eq} = D^{1/3} \cdot d_2^{1/3} \cdot d_3^{1/6} \cdot d_4^{1/6} = 6.129m$$

$$\text{and } D_b = r_L^{1/2} \cdot d_3^{1/3} \cdot d_4^{1/6} = 0.283m$$

$$\text{now } C_{AN} = \frac{0.0242}{\log\left(\frac{6.129}{0.283}\right)} \mu F/km = 0.0181 \mu F/km$$

$$\text{so capacitive admittance to neutral} = \frac{1}{2\pi f C_{AN}} \text{ S/km} = \boxed{5.686 \times 10^{-6} \text{ S/km}}$$


now, charging current, $|I_{ang}| = 2\pi f C_{av} \times |V_{LN}|$

$$= 2\pi \times 50 \times 0.0181 \times \frac{13^2}{\sqrt{3}} \times 10^{-3}$$
$$= 0.433 \text{ Amp/km}$$

so charging current per conductor = $\frac{0.433}{2} \text{ Amp/km}$

$$= 0.2166 \text{ Amp/km}$$

3.9)

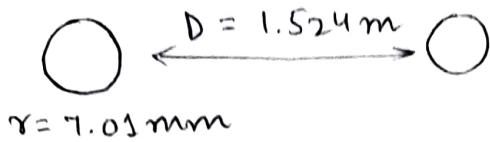

$$\text{line-to-line capacitance, } C_{12} = \frac{0.0121}{\log\left(\frac{D}{r}\right)} \text{ MF/km}$$

$$\Rightarrow C_{12} = \frac{0.0121}{\log\left(\frac{1.524}{7.01 \times 10^{-3}}\right)} \text{ MF/km}$$

- so total line-to-line capacitance

$$= \frac{0.0121}{\log\left(\frac{1.524}{7.01 \times 10^{-3}}\right)} \times 32.16 \text{ } \mu\text{F}$$

$$\boxed{= 0.166 \mu\text{F}}$$

$$\begin{aligned} \text{• line-to-line admittance} &= j2\pi f \times C_{\text{L-L}} \\ &= j6.27 \times 10^{-5} \text{ mho} \\ &\quad (\text{given } f = 60 \text{ Hz}) \end{aligned}$$

$$\begin{aligned} \text{• reactive power} &= V^2 \times (\text{admittance}) \\ &= (20 \times 1000)^2 \times 6.27 \times 10^{-5} \text{ VA}_\text{R} \\ &= \boxed{25.08 \text{ kVA}_\text{R}} \end{aligned}$$


3.11) from 3.9

line-to-line capacitance = $0.166 \mu\text{F}$

and length of conductor, $L = 32.16 \text{ km}$

$$\text{so charge per length, } \lambda = \frac{C}{L} = \frac{0.166 \times 10^{-6}}{32.16 \times 1000} \bullet$$

$$= 103.233 \times 10^{-9} \text{ C/m}$$

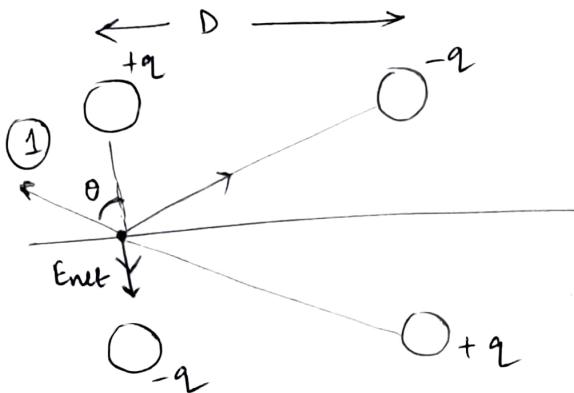

(i) Surface electric field at conductor ①, E_1

E_1 won't have much effect from other charges.

$$\text{so } E_1 = \frac{\lambda}{2\pi\epsilon_0 r} = \boxed{2.66 \text{ kV/cm}}$$

(using $r = 7.01 \text{ mm}$)

(ii) directly under the conductor on ground,


$$E_{net} = \frac{2\lambda}{2\pi\epsilon_0 \times h} - \frac{2\lambda}{2\pi\epsilon_0 \sqrt{h^2+d^2}} \times \left(\frac{h}{\sqrt{h^2+d^2}} \right)$$

$$= \frac{2\lambda h}{2\pi\epsilon_0} \left(\frac{1}{h^2} - \frac{1}{h^2+d^2} \right)$$

$$= \boxed{0.0483 \text{ kV/m}}$$

HARSH KUMAR JHA

2.2)

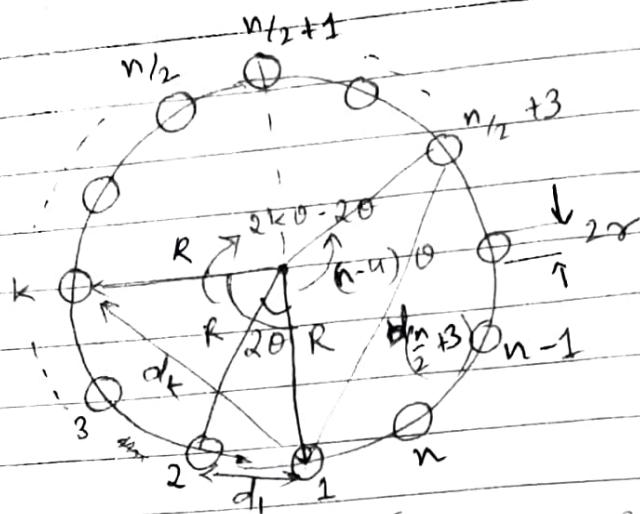

now, $20 \times n = 360^\circ$ (n = no. of subconductors)
 $\Rightarrow n\theta = 180^\circ$

and $d^2 = 2R^2(1 - \cos(2\theta))$
 $\Rightarrow d = R \sin\theta$

see the figure for semiconductor labelling
 and d_k value.

$$\Rightarrow d_k = 2R \sin[(k-1)\theta]$$

for $k = \frac{n}{2} + 3$, $d_{\frac{n}{2}+3} = 2R \sin\left(\left(\frac{n}{2}+2\right)\theta\right)$

and from figure, $d_{\frac{n}{2}+3} = 2R \sin\left(\left(\frac{n-4}{2}\right)\theta\right)$

and $\left(\frac{n}{2}+2\right)\theta + \left(\frac{n-4}{2}\right)\theta = n\theta = 180^\circ$


or $\sin\left(\left(\frac{n-4}{2}\right)\theta\right) = \sin\left(\frac{n+4}{2}\theta\right)$

\therefore we can ~~not~~ generalise the expression
 of d_k for all distances.

$$GMR = \left\{ r^1 \cdot \prod_{k=2}^n \alpha R \sin((k-1)\theta) \right\}^{1/n}$$

$$= \left\{ r^1 \cdot (\alpha R)^{n-1} \cdot \prod_{k=2}^n \sin((k-1)\theta) \right\}^{1/n}$$


$$GMR = \left\{ r^1 \cdot (\alpha R)^{n-1} \cdot \prod_{k=1}^{n-1} \sin(k\theta) \right\}^{1/n}$$

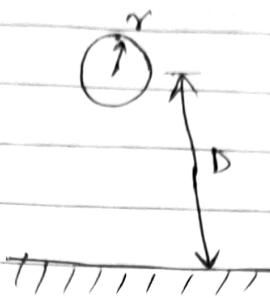2.11)

We need to consider charge imaging here.
so, distance between conductor and its image = $2D$

$$\begin{aligned} \text{so } L &= 0.4605 \left[\log\left(\frac{1}{r'}\right) \cdot \log\left(\frac{1}{2D}\right) \right] \\ &= 0.4605 \left[\log\left(\frac{100 \times 2}{e^{-1/4} \times 1.956}\right) \cdot \log\left(\frac{1}{2 \times 6.705}\right) \right] \end{aligned}$$

$$L = 1.493 \text{ mH/km}$$

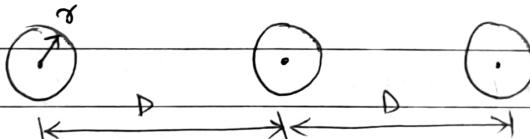2.12)

$$r = 1.25 \text{ cm}, \quad D = 3 \text{ m} \quad (\text{given})$$

~~$L_a = 0.4605$~~

$$L_a = 2 \times 10^{-7} \left[\ln\left(\frac{1}{r'}\right) + \ln\sqrt{D \times 2D} + j\sqrt{3} \ln \sqrt{\frac{D}{2D}} \right] \text{ H/m}$$

$$\Rightarrow L_a = (1.22 - j0.12) \text{ mH/km}$$

$$L_B = 2 \times 10^{-7} \left[\ln\left(\frac{1}{r'}\right) + \ln\sqrt{D \times D} + j\sqrt{3} \ln \sqrt{\frac{D}{D}} \right] \text{ H/m}$$


$$\Rightarrow L_B = 1.14 \text{ mH/km}$$

$$L_C = 2 \times 10^{-7} \left[\ln\left(\frac{1}{r'}\right) + \ln\sqrt{D \times 2D} + j\sqrt{3} \ln \sqrt{\frac{2D}{D}} \right] \text{ H/m}$$

$$\Rightarrow L_C = (1.22 + j0.12) \text{ mH/km}$$

Date _____


1.1) load duration curve -

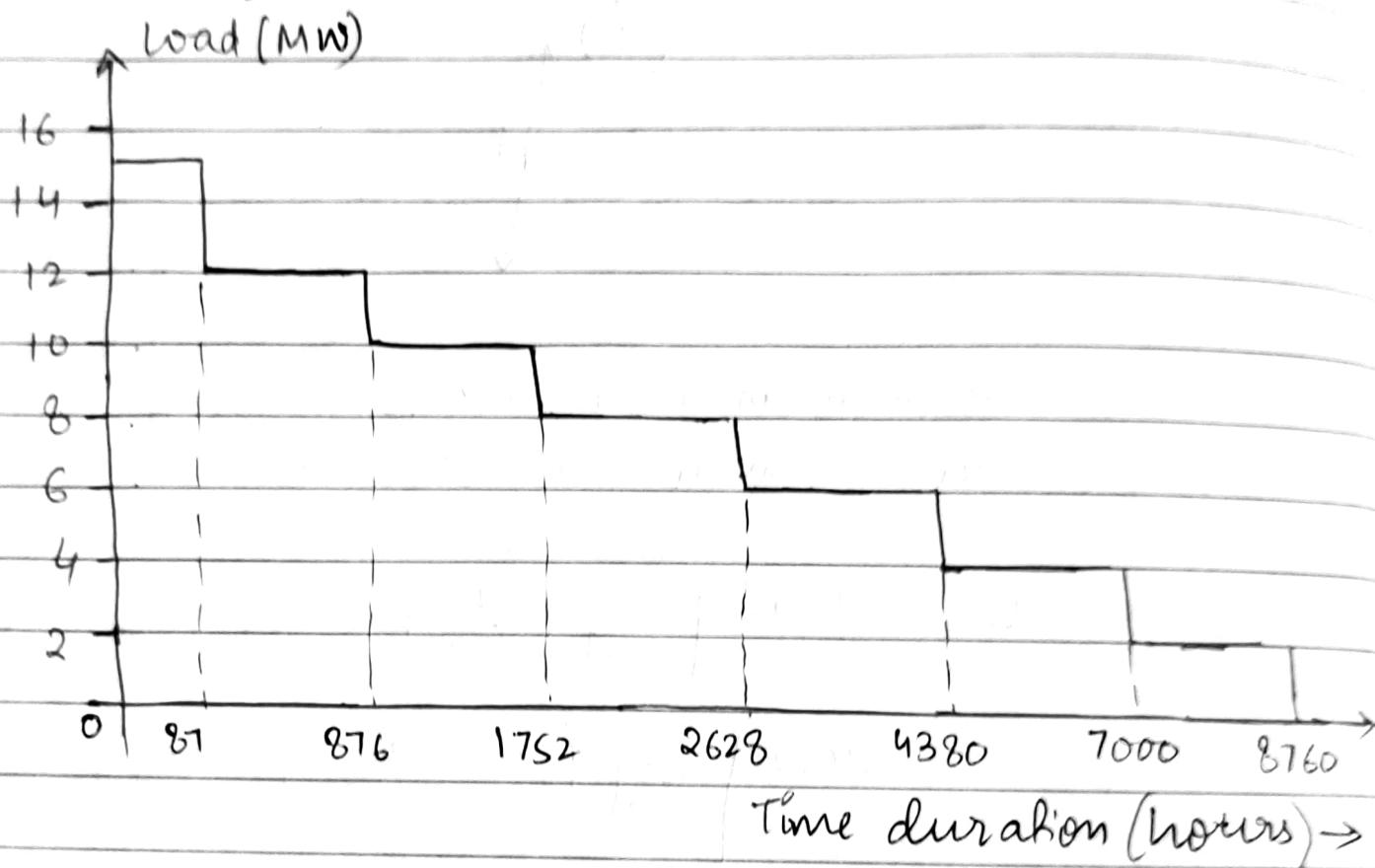

$$\text{Average load} = \frac{\text{Units generated}}{\text{Time}}$$
$$= 5.827 \text{ MW}$$

$$\text{no load factor} = \frac{\text{Average load}}{\text{Max load}}$$
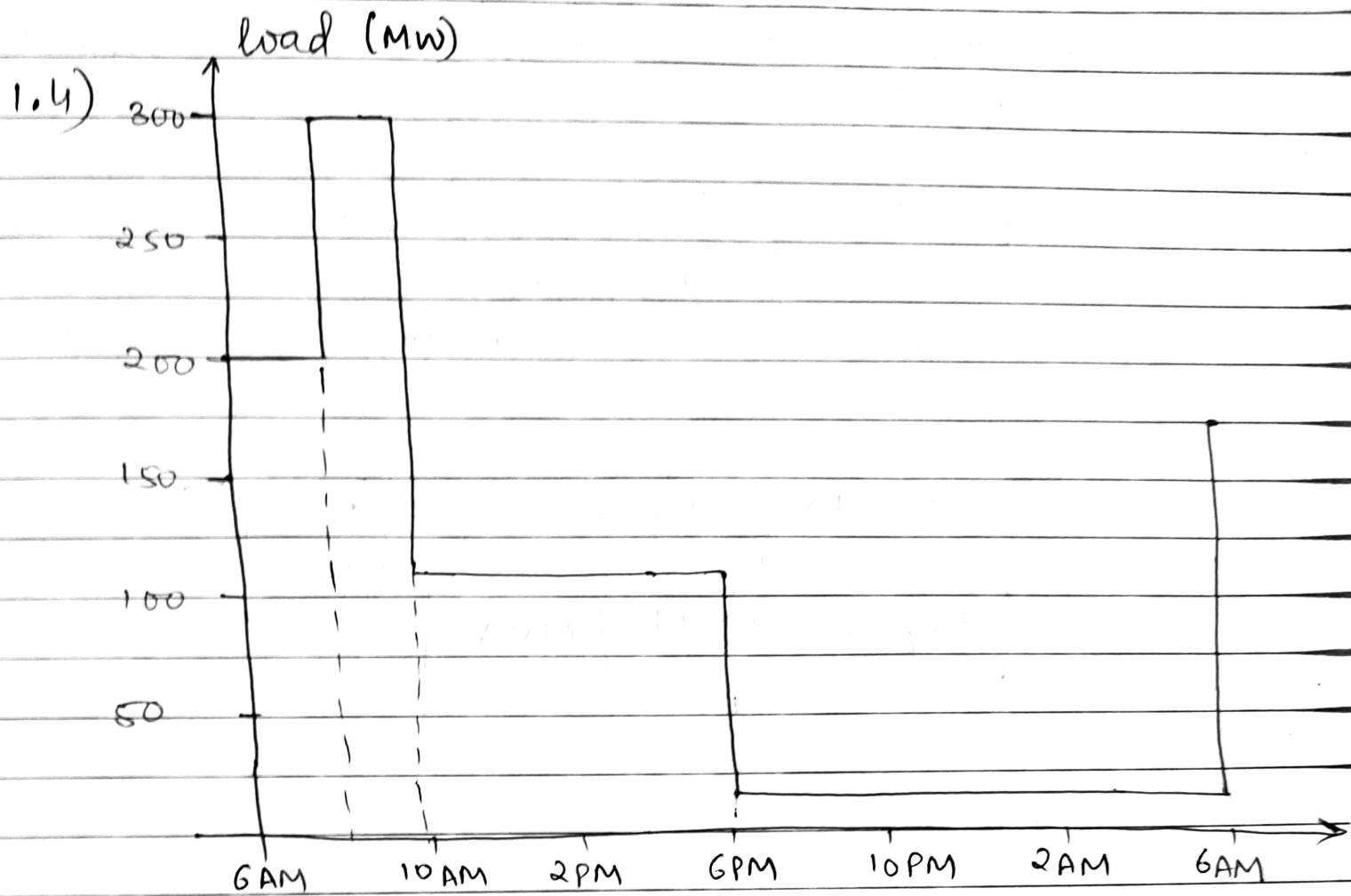
$$= \frac{5.827}{15} = \underline{\underline{0.389}}$$



- daily energy produced = $(200 \times 2 + 300 \times 2 + 120 \times 8 + 20 \times 12)$
 $= 2200 \text{ MWhr}$

- load factor = $\frac{(2200)}{24} / 300 = 0.3055$

• Diversity factor = 

$$\frac{200 + 300 + 150}{300}$$

$$= \frac{100 + 150 + 50 + 70}{300}$$

$$= \underline{\underline{1.067}}$$