

19EE10039
Manasi Uniyal

3/4/2022

11.14

$$G_1 = 50 \text{ MVA}$$

$G_2 = 100 \text{ MVA}$ 2 machine.

$G' = 150 \text{ MVA}$ - system

$$H_1 = 5 \text{ MJ/MVA}$$


$H_2 = 3 \text{ MJ/MVA}$ 3 machine.

$$n_1 = 4, n_2 = 3.$$


$$H_{eq} = n_1 \left(\frac{G_1}{G} \right) H_1 + n_2 \left(\frac{G_2}{G} \right) H_2.$$

$$\underline{H_{eq}} = 19 \text{ MJ/MVA}$$

10.1

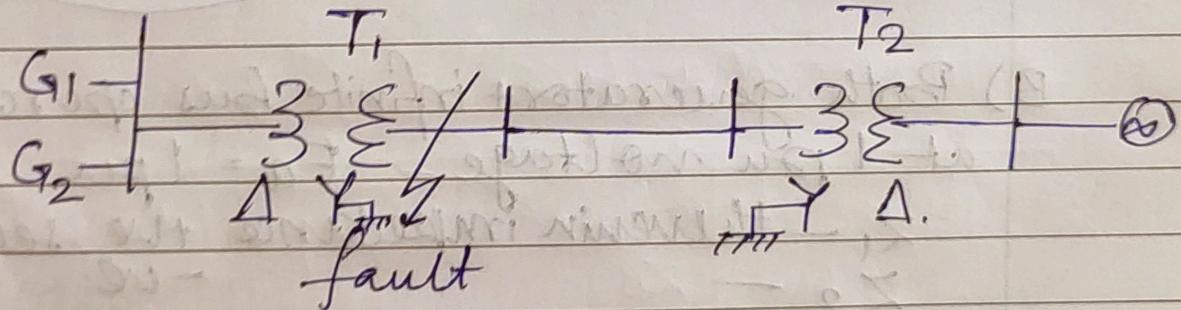


a) +ve sequence network.

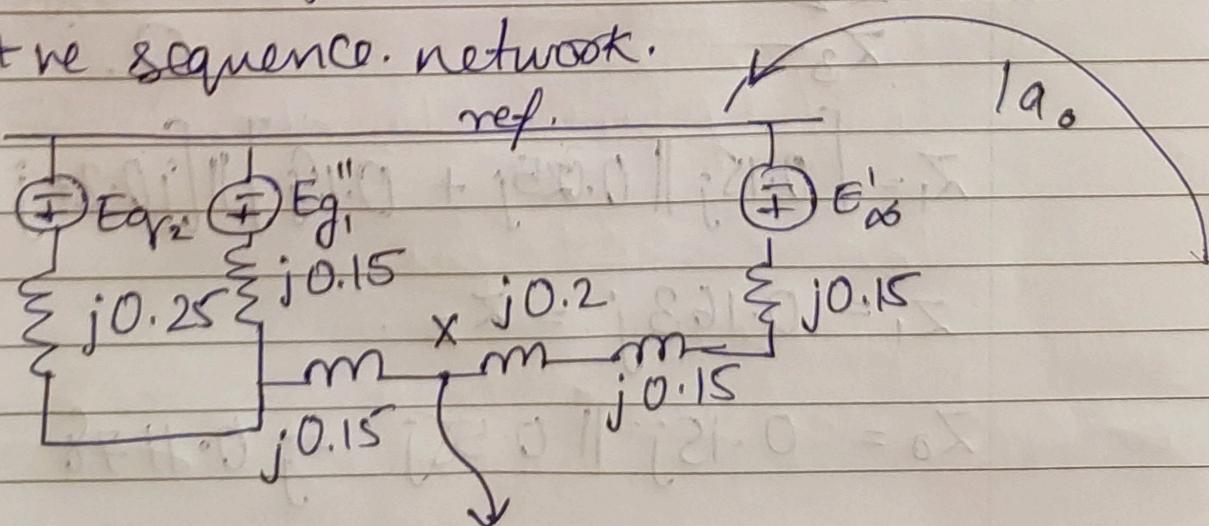


b)

-ve sequence network.

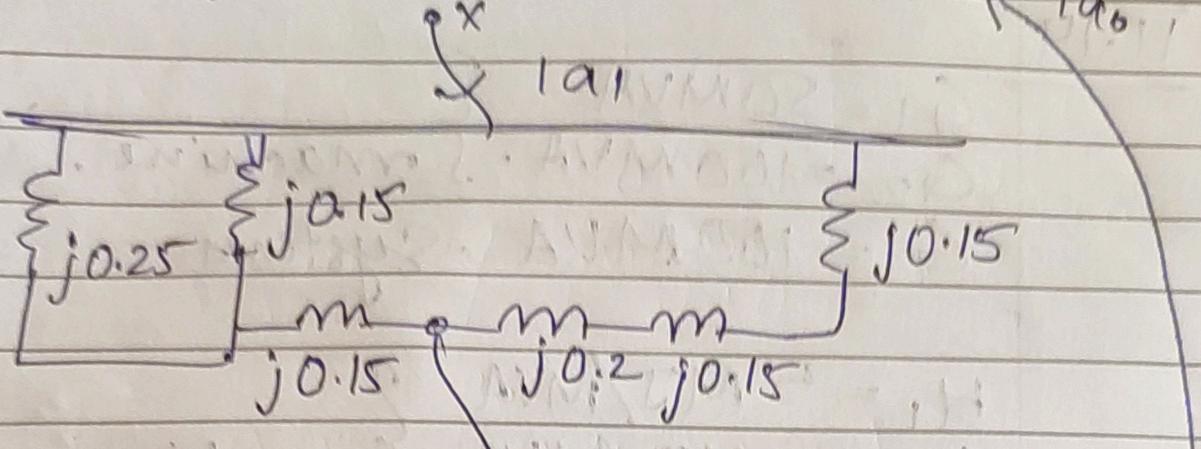

c) Osequence network

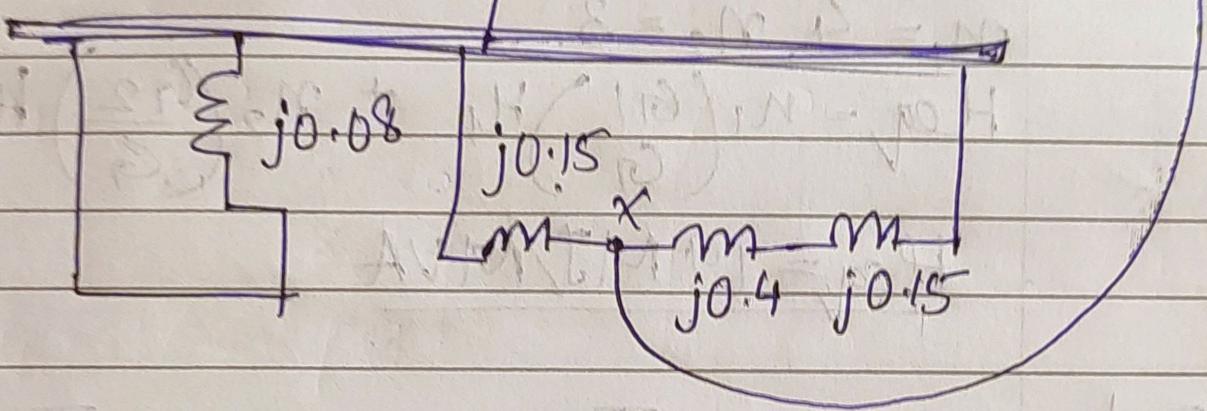

B) Both generators + infinite bus operate at 1 pu voltage $E_a = 1 \text{ pu}$

Z_1 - thevenin impedance +ve sequence

Z_2 -

Z_3 -

$$Z_1 = [0.15j \parallel 0.25j + 0.15j] \parallel [j0.2 + j0.15 + j0.15]$$


$$Z_1 = 0.163j = Z_2$$

$$Z_0 = 0.15j \parallel 0.55j = j0.1178$$

$$I_{a_1} = \frac{E_a}{Z_1 + Z_2 + Z_0} = -j2.253 = I_{a_0}$$

So fault current $I_f = 3I_{a_0} = -j6.759 \text{ pu}$.

10.2

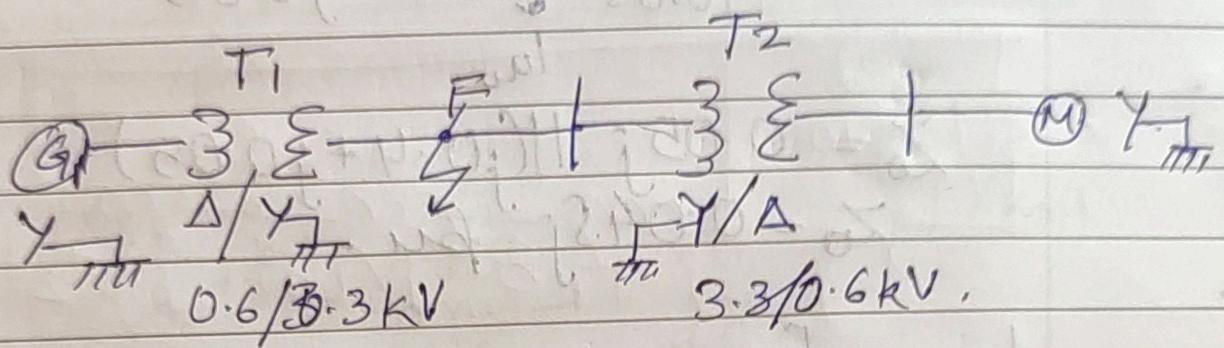

$$\chi_1 = \chi_2 = 0.1 \text{ pu} \quad \chi_0 = 0.05 \text{ pu}$$

$$T_1 \rightarrow 1.2 \text{ MVA} \quad T_2 \rightarrow 0.05 \text{ pu}$$


$$\chi_{L1} = \chi_{L2} = 0.2 \text{ pu}$$

$$\chi_{L0} = 0.4 \text{ pu}$$

$$\chi_h = 0.5 \text{ pu}$$

the sequence.


ref.

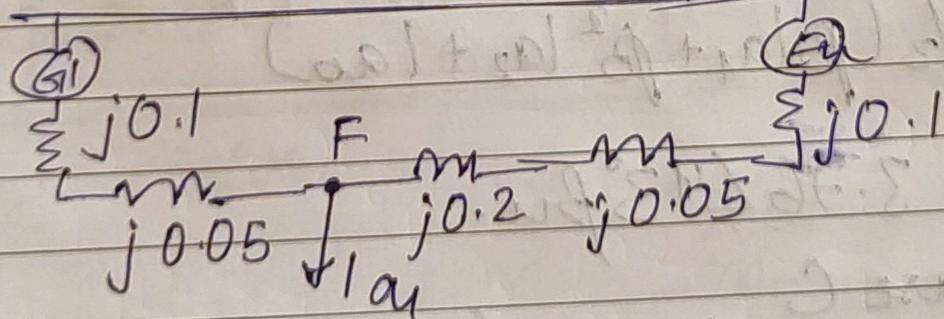

$$\chi_1 = (0.1j + 0.05j) \parallel (0.2j + 0.05j + 0.1j)$$

$$\chi_1 = 0.105j \text{ pu} = \chi_2$$

Osequence

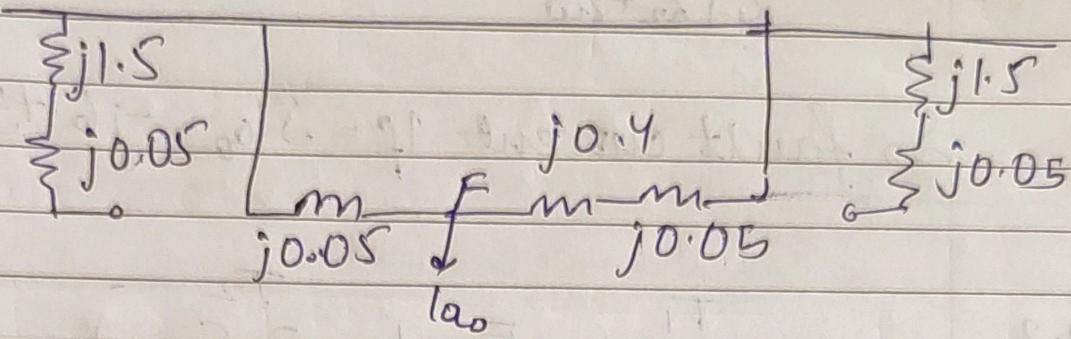

$$Z_0 = 0.05j \parallel (j0.4 + j0.05)$$

$$Z_0 = 0.045j \text{ pu.}$$

$$I_{a1} = \frac{E_a}{Z_1 + Z_0} \quad Z_f = 0 \text{ pu}$$

$$I_{a1} = -j7.32 \text{ pu.}$$


$$I_{a2} = -\frac{(E_a - I_{a1}Z_1)}{Z_2} = j2.2 \text{ pu.}$$

$$I_{a0} = -\frac{(E_a - I_{a1}Z_1)}{Z_0} = j5.142 \text{ pu.}$$

$$I_C = \frac{1}{3} (\beta I_{a1} + \beta^2 I_{a2} + I_{a0})$$


$$I_C = 3.76 \angle 43^\circ \text{ pu.}$$

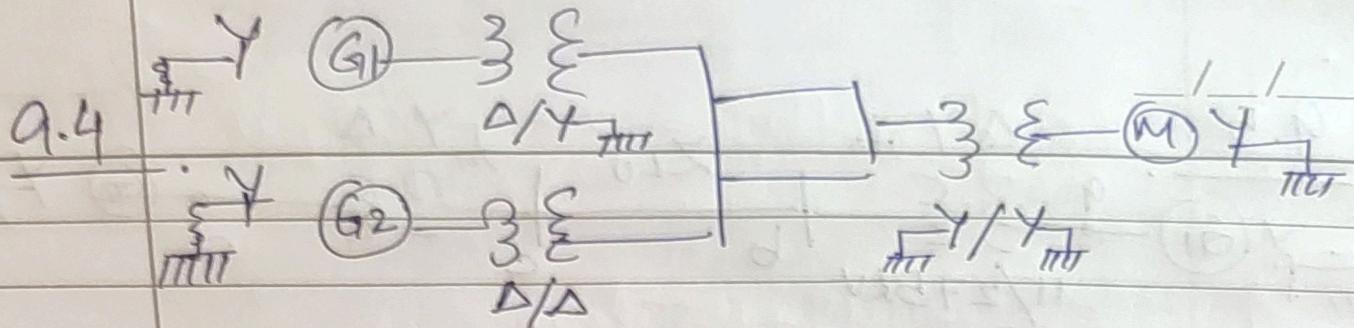comp. of phase C
in $G_1 = I_C \left(\frac{0.85}{0.5} \right) \left(\frac{1.2 \times 10^6}{0.6 \times 10^3} \right) = 5.264 \text{ kA}$




+ve sequence.

ref.

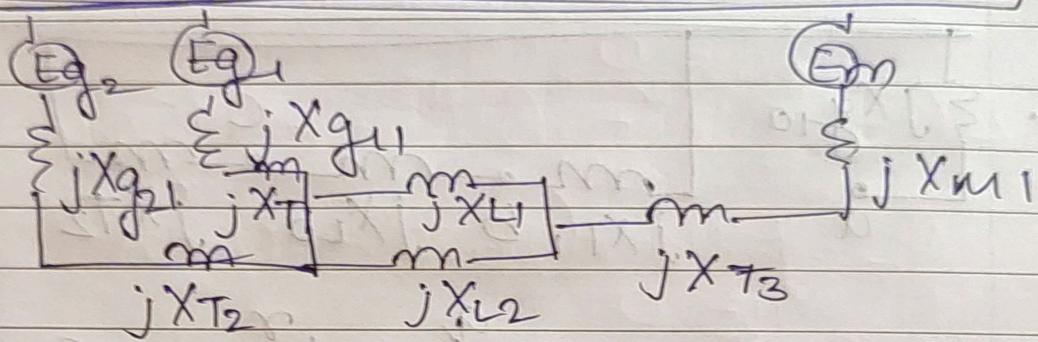


+ve sequence.

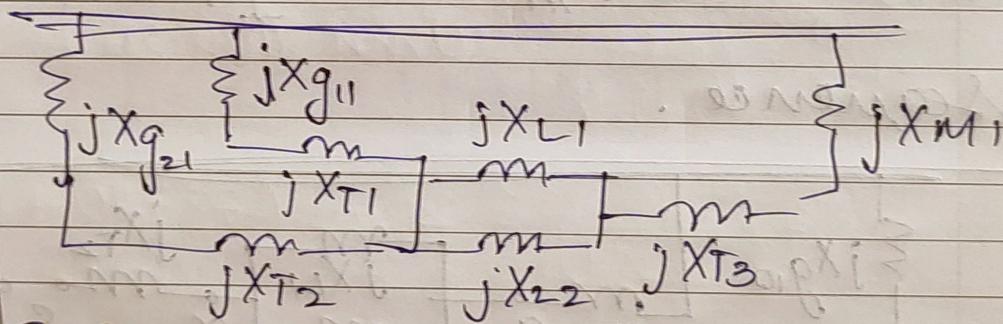


Zero sequence.


ref.

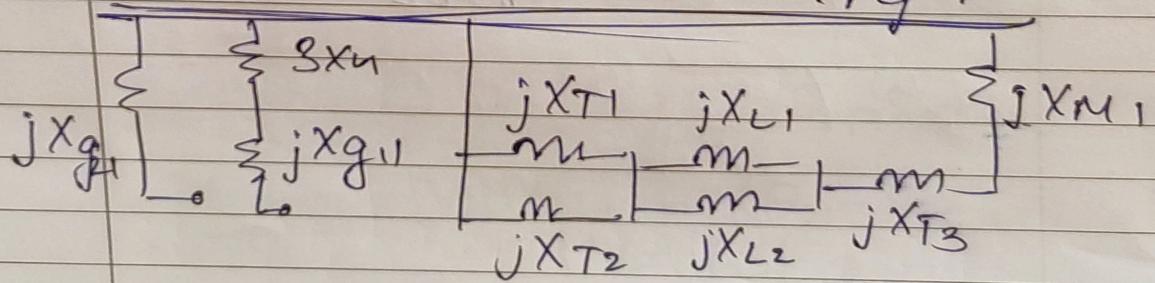


9.5

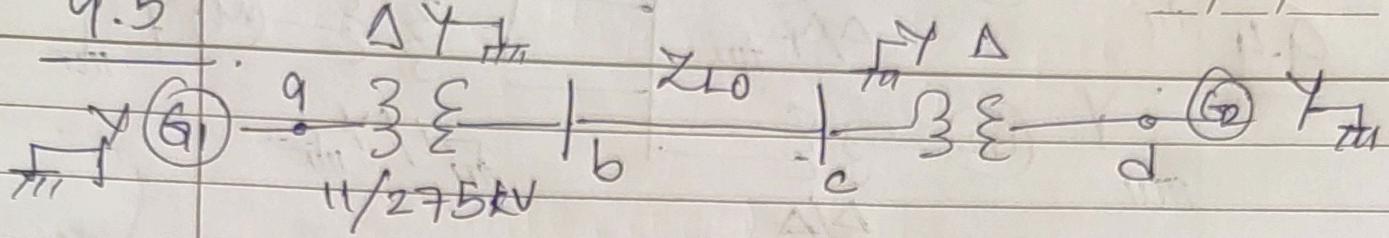


Zero sequence.

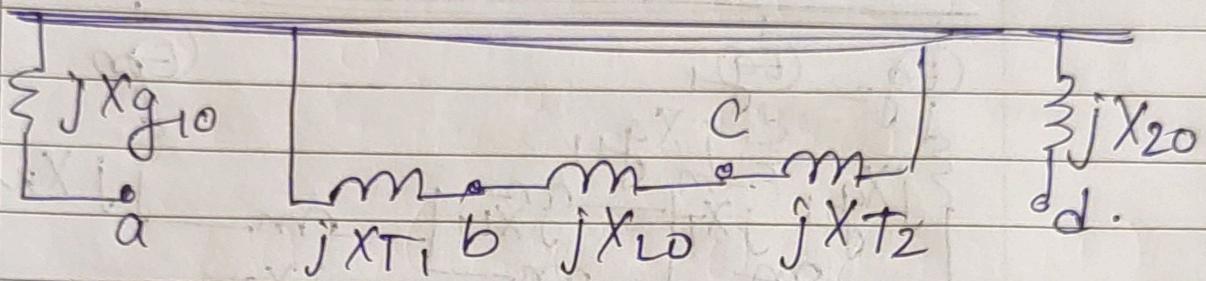


9.6

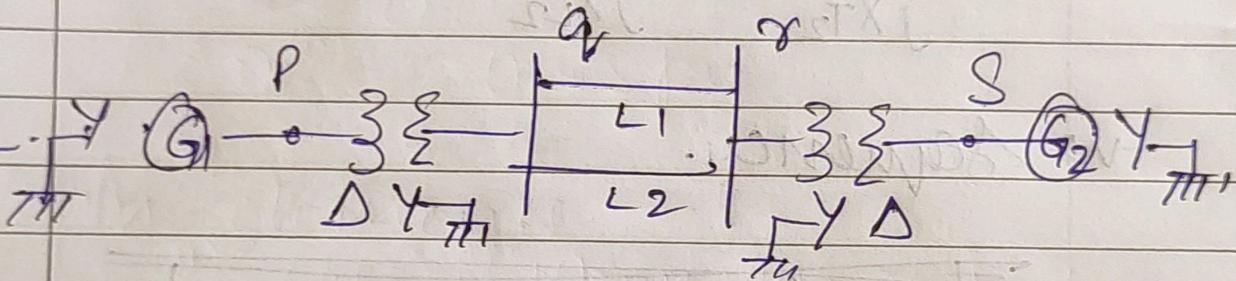

Zero sequence.

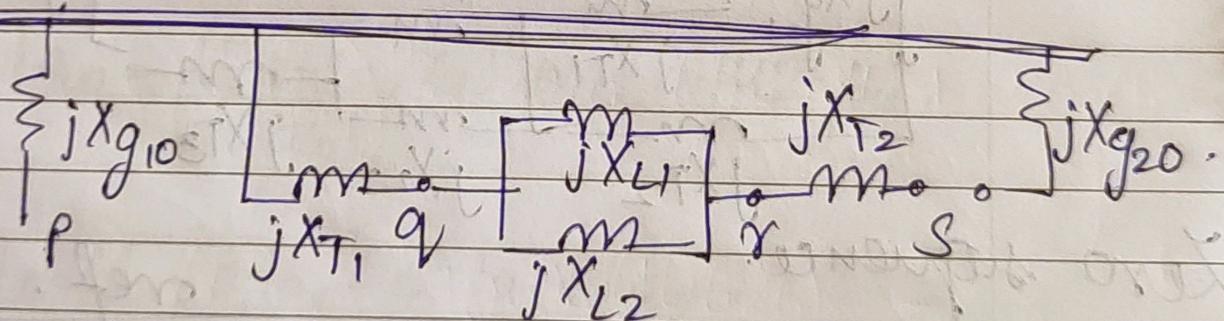

7.5

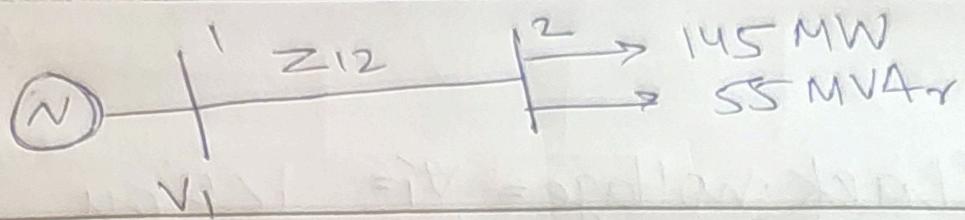

Base = 100 MVA

$$Y_{12} = \frac{1}{Z_{12}} = Y_{21} = 10 \angle -73.74^\circ$$

$$Y_{10} = Y_{20} = 0.$$

$$Y_{11} = Y_{10} + Y_{12} = Y_{12}$$

$$Y_{22} = Y_{20} + Y_{21} = Y_{21} = Y_{12}.$$

$$Y_{12} = Y_{21} = -Y_{12} = 10 \angle 106.26^\circ$$

$$Y_{bus} = \begin{bmatrix} 10 \angle -73.74^\circ & 10 \angle 106.26^\circ \\ 10 \angle 106.26^\circ & 10 \angle -73.74^\circ \end{bmatrix}$$

$$P_2 = \sum_{j=1}^2 |V_2| |Y_j| |V_2| \cos(\theta_{2j} - \delta_2 + \delta_j)$$

$$\begin{aligned} \frac{\partial P_2}{\partial \delta_2} &= \sum_{k=1, k \neq 2}^2 |V_2| |V_k| |Y_{2k}| \sin(\theta_{2k} - \delta_2 + \delta_k) \\ &= |V_2| |V_1| |Y_{21}| \sin(\theta_{21} - \delta_2 + \delta_1) \end{aligned}$$

$$\frac{\partial P_2}{\partial V_2} = 2 |V_2| |Y_{22}| \cos \theta_{22} + |V_1| |Y_{21}| \cos (\theta_{21} - \delta_2 + \delta_1)$$

$$\frac{\partial Q_2}{\partial \delta_2} = |V_1| |V_2| |Y_{21}| \cos(\theta_{21} - \delta_2 + \delta_1)$$

$$\frac{\partial \theta_2}{\partial V_2} = -|V_1| |Y_{21}| \sin(\theta_{21} - \delta_2 + \delta_1) - 2 |V_2| |Y_{22}| \sin(\theta_{22})$$

Slack voltage = $V_1 = 1 \angle 0^\circ$ pu.

$$|V_2| = 1 \quad S_2^{(0)} = 0$$

$$S_2^{(0)} = -(145 + j55) \text{ pu}$$

$$P_2^{(0)} = 10 \cos(106.26^\circ) + 10 \cos(-73.74^\circ)$$

$$\Delta P^{(0)} = P_2^{(0)} - P_2^{(0)} = 0 \quad -1.45 \text{ pu}$$

$$Q_2^{(0)} = -10 \sin(106.26^\circ) - 10 \sin(-73.74^\circ)$$

$$\Delta Q^{(0)} = -0.55 \text{ pu}$$

Jacobian elements :-

$$J_1^{(0)} = \left(\frac{\partial P_2}{\partial S_2} \right)^{(0)} = 10 \sin(106.26^\circ) = 9.6$$

$$J_2^{(0)} = \left(\frac{\partial P_2}{\partial |V_2|} \right)^{(0)} = 20 \cos(-73.74^\circ) + 10 \cos(106.26^\circ) = 2.8$$

$$J_3^{(0)} = \left(\frac{\partial Q_2}{\partial S_2} \right)^{(0)} = 10 \cos(106.26^\circ) = -2.8$$

$$J_4^{(0)} = \left(\frac{\partial Q_2}{\partial |V_2|} \right)^{(0)} = 9.6$$

$$\begin{bmatrix} \Delta P_2^{(0)} \\ \Delta Q_2^{(0)} \end{bmatrix} = \begin{bmatrix} 9.6 & 2.8 \\ -2.8 & 9.6 \end{bmatrix} \begin{bmatrix} \Delta S_2^{(0)} \\ \Delta V_2^{(0)} \end{bmatrix}$$

$$\begin{bmatrix} -1.45 \\ -0.55 \end{bmatrix} = \begin{bmatrix} 9.6 & 2.8 \\ -2.8 & 9.6 \end{bmatrix} \begin{bmatrix} \Delta S_2^{(0)} \\ \Delta V_2^{(0)} \end{bmatrix}$$

$$\begin{array}{l|l} \Delta S_2^{(0)} = -0.1238 & S_2^{(0)} = -0.1238 \\ \Delta V_2^{(0)} = -0.0934 & |V_2|^{(0)} = 0.9066 \end{array}$$

$$P_2^{(0)} = 0.9066 \times 10 \cos\left(406.26 + 0.1238 \times \frac{180}{\pi}\right) \\ = -1.29 \text{ pu.}$$

$$Q_2^{(0)} = -0.9066 \times 10 \sin\left(406.26 + 0.1238 \times \frac{180}{\pi}\right) \\ = -0.433 \text{ pu.}$$


$$\Delta P^{(0)} = -1.45 + 1.29 = -0.16 \text{ pu.} \\ \Delta Q^{(0)} = -0.55 + 0.433 = -0.117 \text{ pu}$$

$$\begin{bmatrix} \Delta S_2^{(1)} \\ \Delta V_2^{(1)} \end{bmatrix} = J^{-1} \begin{bmatrix} -0.16 \\ -0.117 \end{bmatrix} = \begin{bmatrix} -0.012084 \\ -0.015712 \end{bmatrix}$$

$$\delta_2^{(1)} = -0.1238 - 0.012084 = -0.1359 \text{ rad.} \\ |V_2|^{(1)} = 0.891 \text{ pu.}$$

So, voltage after 2 iteration = 0.891 pu
 S at bus after 2 iter. = -0.1359 rad.

7.6

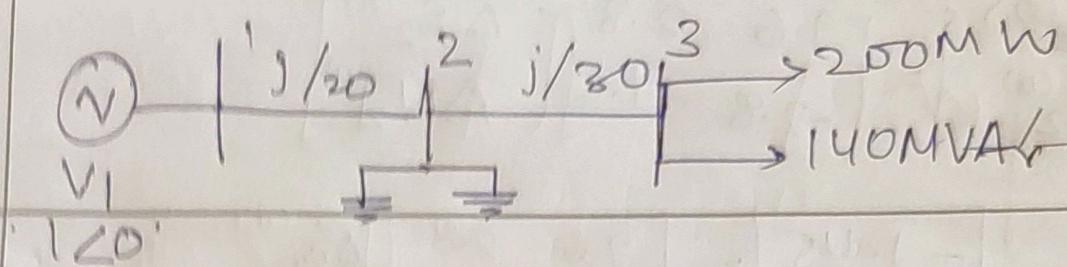

$$Y_{12} = 20j = -20j$$

$$Y_{13} = 0 = Y_{10} = Y_{20} = Y_{30}$$

$$Y_{23} = -30j$$

$$Y_{11} = Y_{10} + Y_{12} + Y_{13} = -20j$$

$$Y_{22} = Y_{20} + Y_{21} + Y_{23} = -50j$$

$$Y_{33} = \underline{Y_{30}} = -20j$$

$$Y_{12} = Y_{21} = 20j$$

$$Y_{23} = Y_{32} = 30j$$

$$Y_{13} = Y_{31} = 0.$$

(a) GS Method: —

$$S_2^{\text{sen}} = -60j - 90 = P_2 + jQ_2.$$

$$S_3^{\text{sen}} = -2 - 1.4j$$

$$V_2^{P+1} = \frac{1}{Y_{22}} \left[\frac{P_2 - jQ_2}{V_2^P} - Y_{21}V_1 - Y_{23}V_3^P \right]$$

$$V_3^{P+1} = \frac{1}{Y_{33}} \left[\frac{P_3 - jQ_3}{V_3^P} - Y_{31}V_1 - Y_{32}V_2^P \right]$$

Slack bus power:—

$$P_1 = \sum_{k=1}^8 |V_1| |V_k| |Y_{1k}| \cos(\theta_{1k} - \delta_1 + \delta_k),$$

$$Q_1 = - \sum_{k=1}^3 |V_1| |V_k| |Y_{1k}| \sin(\theta_{1k} - \delta_1 + \delta_k)$$

$$V_2^{(0)} = 1 \quad V_3^{(0)} = 1$$

1st iteration:—

$$V_2^1 = \frac{1}{-50j} \left[\frac{-0.9 + 0.6j}{V_2^{(0)}} - 20j - 30j V_3^0 \right].$$

$$V_2^1 = 0.988 \angle 1.044^\circ$$

$$V_3^1 = \frac{1}{-20j} \left[-2 + 1.4j - 30j V_2^0 \right] = 1.433 \angle 4^\circ$$

2nd iteration:—

$$V_2^2 = \frac{j}{50} \left[\frac{-0.9 + 0.6j}{0.988 \angle 1.044} - 20j - 30j (1.433 \angle 4) \right]$$
$$= 1.247 \angle -3.6^\circ$$


$$V_3^2 = \frac{j}{20} \left[\frac{-2 + 1.4j}{1.433 \angle 4} - 30j (0.988 \angle 1.044) \right]$$
$$= 1.433 \angle -3.73^\circ$$

$$P_1 = |V_1|^2 |Y_{11}| \cos(\theta_{11} - \delta_1 + \delta_1) + |V_1| |V_2| |Y_{12}| \cos(\theta_{12} - \delta_1 + \delta_2)$$
$$+ |V_1| |V_3| |Y_{13}| \cos(\theta_{13} - \delta_1 + \delta_3)$$

$$\begin{aligned} P_1 &= 1.586 \text{ pu.} \\ Q_1 &= -4.89 \text{ pu.} \end{aligned} \quad \left\{ \begin{array}{l} S_1 = (1.586 - j4.89) \text{ pu.} \\ = 158.6 - j489 \text{ MVA} \end{array} \right.$$

6.11

(i) Series.

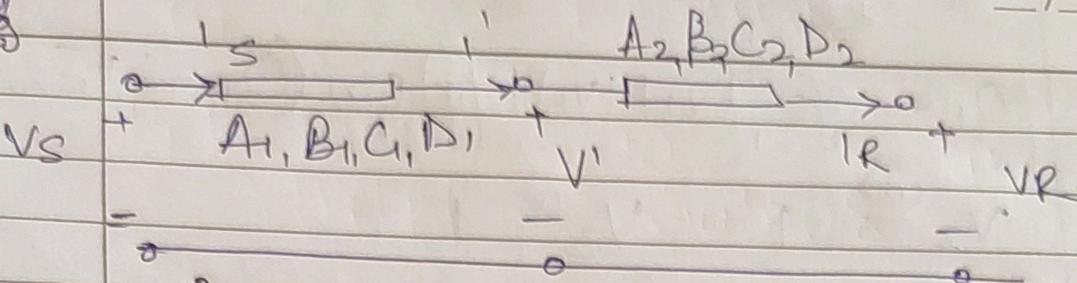

$$\begin{bmatrix} V_s \\ I_s \end{bmatrix} = \begin{bmatrix} A_1 & B_1 \\ C_1 & D_1 \end{bmatrix} \begin{bmatrix} V_I \\ I' \end{bmatrix}$$

$$\begin{bmatrix} V' \\ I' \end{bmatrix} = \begin{bmatrix} A_2 & B_2 \\ C_2 & D_2 \end{bmatrix} \begin{bmatrix} V_R \\ I_R \end{bmatrix}$$

$$\begin{bmatrix} A_1 & B_1 \\ C_1 & D_1 \end{bmatrix} \begin{bmatrix} V_s \\ I_s \end{bmatrix} = \begin{bmatrix} A_2 & B_2 \\ C_2 & D_2 \end{bmatrix} \begin{bmatrix} V_R \\ I_R \end{bmatrix}$$

$$\begin{bmatrix} V_s \\ I_s \end{bmatrix} = \begin{bmatrix} A_1 & B_1 \\ C_1 & D_1 \end{bmatrix} \begin{bmatrix} A_2 & B_2 \\ C_2 & D_2 \end{bmatrix} \begin{bmatrix} V_R \\ I_R \end{bmatrix}$$

$$\begin{bmatrix} A' & B' \\ C' & D' \end{bmatrix}$$


$$A' = A_1 A_2 + B_1 C_2$$

$$B' = A_1 B_2 + B_1 D_2$$

$$C' = A_2 C_1 + D_1 C_2$$

$$D' = C_1 B_2 + D_1 D_2$$

(ii) Parallel.

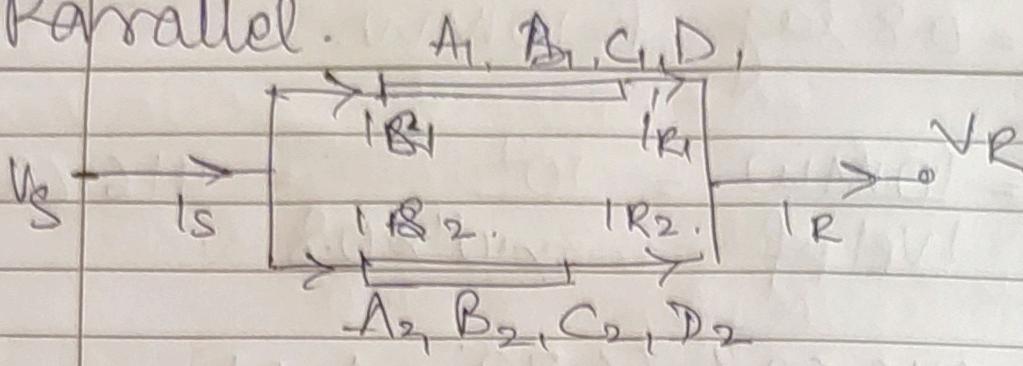

$$\left[\frac{V_S}{I_{S1}} \right] = \begin{bmatrix} A_1 & B_1 \\ C_1 & D_1 \end{bmatrix} \left[\frac{V_R}{I_{R1}} \right]$$

$$\left[\frac{V_S}{I_{S2}} \right] = \begin{bmatrix} A_2 & B_2 \\ C_2 & D_2 \end{bmatrix} \left[\frac{V_R}{I_{R2}} \right]$$

$$\left[\frac{V_S}{I_S} \right] = \begin{bmatrix} A' & B' \\ C' & D' \end{bmatrix} \left[\frac{V_R}{I_R} \right]$$

$$I_S = I_{S1} + I_{S2}$$

$$I_R = I_{R1} + I_{R2}$$

$$V_S = A_2 V_R + B_2 I_{R2}$$

$$V_S = A_1 V_R + B_1 I_{R1}$$

$$I_{S2} = C_2 V_R + D_2 I_{R2}$$

$$I_{S1} = C_1 V_R + D_1 I_{R1}$$

$$\frac{V_S}{B_1} + \frac{V_S}{B_2} = V_R \left(\frac{A_1 + A_2}{B_1 + B_2} \right) + \frac{I_{R1} + I_{R2}}{I_R}$$

$$V_S = V_R \left(\frac{A_1 B_2 + A_2 B_1}{B_1 + B_2} \right) + \left(\frac{B_1 B_2}{B_1 + B_2} \right) I_R$$

$$I_S = V_R (C_1 + C_2) + I_R (D_1 + D_2)$$

$$A' = \frac{A_1 B_2 + A_2 B_1}{B_1 + B_2}$$

$$B' = \frac{B_1 B_2}{B_1 + B_2}$$

$$C' = C_1 + C_2$$

$$D' = D_1 + D_2$$

6.12

$$V_R = 30 \angle 0^\circ \text{ KV}$$
$$\text{pf} = 0.8 \text{ lag} \quad P = 10 \text{ MW.}$$

$$|I_R| = \frac{10 \text{ MW}}{|V_R| \text{ pf}} = \frac{10^7}{3 \times 10^4 \times 0.8} = 416.67 \text{ A.}$$

$$I_R = 416.67 \angle -36.87^\circ = I_1 + I_2$$

$$V_R + I_1 (5.5 + 13.5j) = V_R + I_2 (6 + 11j)$$

$$I_2 = I_2 \frac{(6 + 11j)}{(5.5 + 13.5j)} = I_2 (0.87 \angle -8.28^\circ)$$

$$416.67 \angle -36.87^\circ = I_2 (1 + 0.87 \angle -8.28^\circ)$$

$$I_2 = 224.42 \angle -33.89^\circ \text{ A}$$


$$I_1 = 192 \angle -40.33^\circ \text{ A.}$$

$$P_2 = 30 I_2 \cos \phi = 5585 \text{ kW}$$

$$P_1 = 10 \text{ MW} - P_2 = 4415 \text{ kW}$$

$$(KVA)_2 = 30 \angle 0^\circ \times I_2 = 6732 \angle 33.89^\circ \text{ KVA}$$
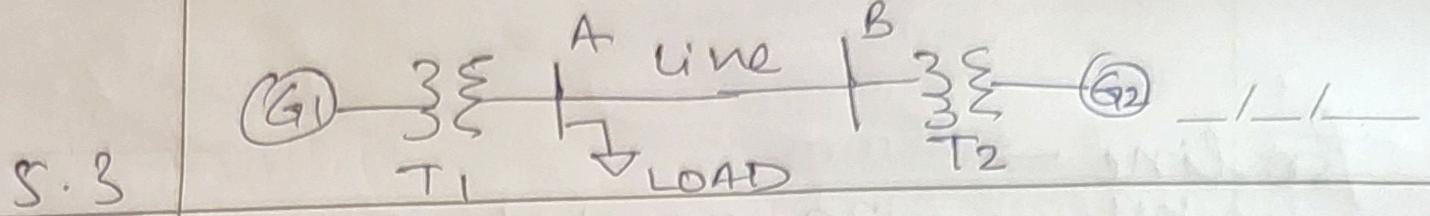
$$(KVA)_1 = 30 \angle 0^\circ \times I_1 = 5787 \angle 40.33^\circ \text{ KVA}$$



S. 3

$$(MVA)_B = 100$$

Base kV for Generator = 20 kV
G1 and G2

for G1 →

$$x_{g1} = 0.09 \frac{MVA_{B\ new}}{MVA_{B\ old}} \frac{kV_{B\ old}^2}{kV_{B\ new}^2}$$

$$= 0.09 \times \frac{100}{90} \times \left(\frac{20}{20}\right)^2$$

$$x_{g1\ new} = 0.1 \text{ pu.}$$

for G2 →

$$x_{g2\ new} = 0.09 \times \frac{100}{90} \times \left(\frac{18}{20}\right)^2$$

$$= 0.081 \text{ pu.}$$

for T1 →

$$x_{T1\ new} = 0.06 \times \frac{100}{80} \times \left(\frac{20}{20}\right)^2$$

$$= 0.2 \text{ pu.}$$

for T2 →

$$x_{T2\ new} = 0.06 \times \frac{100}{80} \times \left(\frac{20}{20}\right)^2$$

$$= 0.25 \text{ pu.}$$

for line →

$$kV_{B\text{line}} = 20 \times \frac{200}{20} \text{ kV} = 200 \text{ kV}$$

$$Z_{B\text{line}} = \frac{kV^2}{MVA_B} = \frac{200^2}{100} = 400 \Omega$$

$$X_{line} = \frac{120}{400} \text{ pu} = 0.3 \text{ pu} = X_{line}$$

$$S = 48 + 64j \text{ MVA}$$

(a)


$$Z_{load} = \frac{200^2}{48+64j} = 300 - 400j \Omega$$


$$Z_{load\text{ pu}} = \frac{Z_{load}}{Z_{B\text{line}}} = \frac{300 - 400j}{400} \\ = (0.75 - j) \text{ pu}$$

$$R_{series} = 0.75 \text{ pu}$$

$$X_{series} = j \text{ pu}$$

Impedance diagram: —

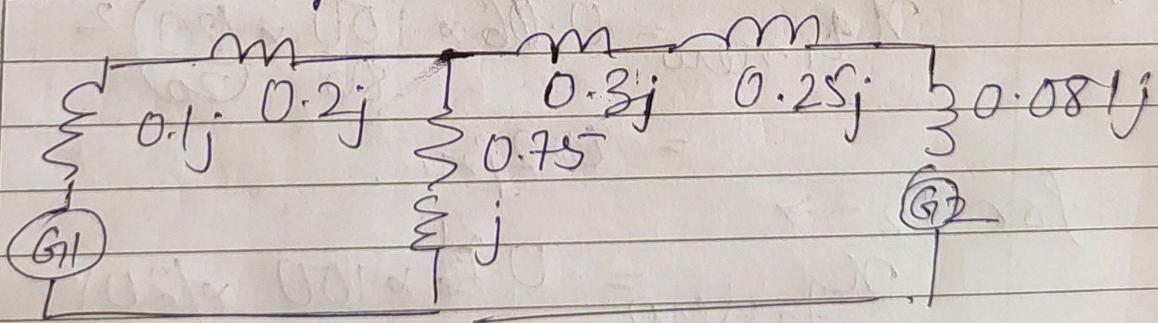

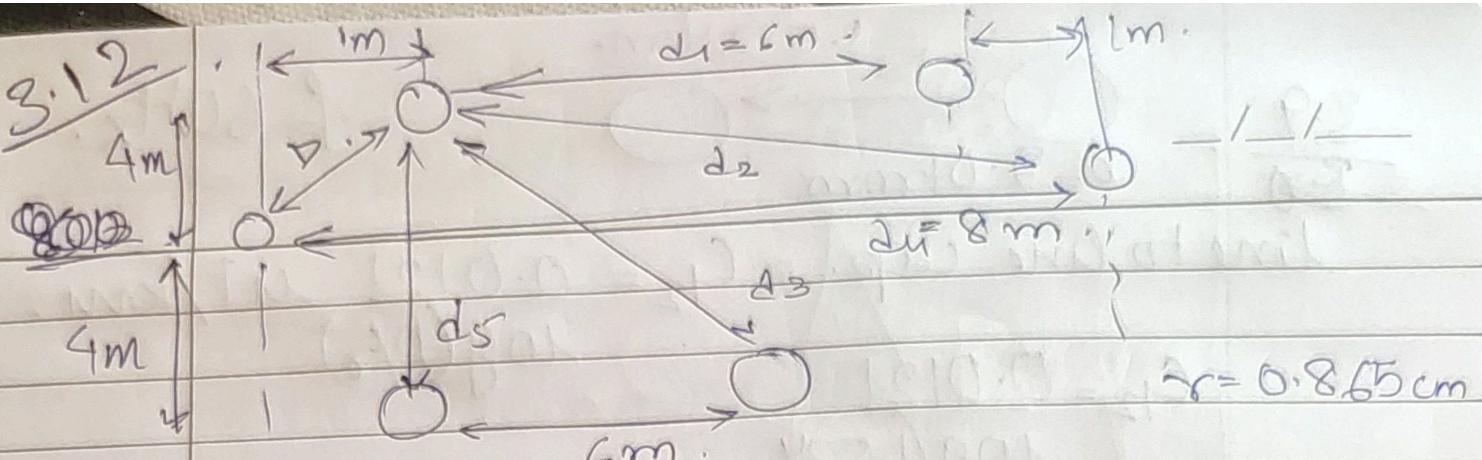

$$\text{capacitance } C_{\text{avg}} = \frac{0.0242}{\log \left(\frac{D_{\text{ear}}}{D_3} \right)} \text{ uF/km}$$

$$d_1 = 6m$$

$$d_2 = \sqrt{4^2 + 7^2} = 8.062 \text{ m.}$$

$$d_3 = 10m$$

$$du = 8m$$

$$D_S = \gamma^{42} d_3^{43} dy^{46} = 0.283 \text{ m.}$$


$$C_{avg} = \frac{0.0242}{wg \left(\frac{6.129}{0.283} \right)} = 0.0181 \text{ mT/km.}$$

$$\text{capacitive admittance to neutral} = 2\pi f C_{\text{air}} = \text{mho/km} = 5.686 \times 10^6 \text{ mho/km}$$

$$\text{changing current, } I_{\text{carg}} = 2\pi f C_{\text{air}} (V_{LN}) \\ = 0.433 \text{ A/km.}$$

Chargeney current
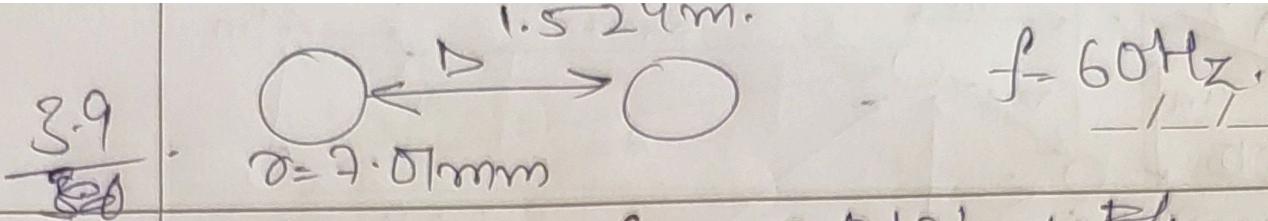
$$\text{per conductor} = \frac{0.433}{2} = 0.2166 \text{ A/km.}$$



line to line cap. $C_{12} = \frac{0.0121}{\log(D/d)} \mu\text{F/km}$.

$$C_{12} = 0.0121$$

$$\log\left(\frac{1.524}{2.01 \times 10^{-3}}\right)$$

total line = $C_{12} \times 32.16 \text{ MF}$

to line caps. = 0.166 MF .

line to line = $j 2\pi f C_{11}$

admittance = $j 6.27 \times 10^{-5} \text{ mho.}$


reactive power = $V^2 \times \text{admittance}$
 $= (2 \times 10^4)^2 \times 6.27 \times 10^{-5}$
 $= 25.08 \text{ kVAr.}$

3.11 from 3.9

line to line Cap. = 0.166 MF

length of Cap. = 32.16 km.

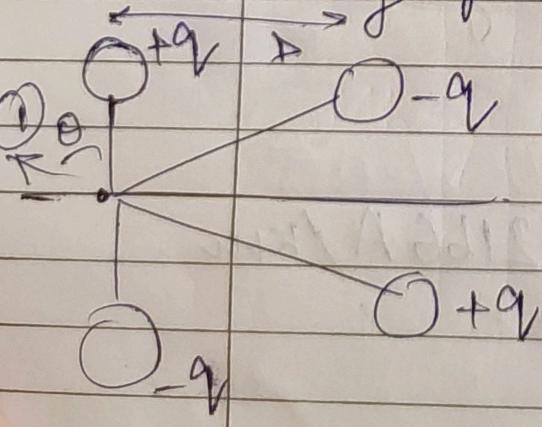change per length = $\lambda = \frac{C}{L} = 103.23 \times 10^{-9} \text{ C/m}$



(i) Surface electric field at ①


$$E_1 = \frac{\lambda}{2\pi\epsilon_0 h} = 2.66 \text{ kV/cm}$$

(ii) $E_{\text{net}} = \frac{2\lambda}{2\pi\epsilon_0 h} - \frac{2\lambda}{2\pi\epsilon_0 \sqrt{h^2+d^2}} \left(\frac{h}{\sqrt{h^2+d^2}} \right)$

$$= \frac{2\lambda h}{2\pi\epsilon_0} \left(\frac{1}{h^2} - \frac{1}{h^2+d^2} \right)$$

$$= 0.0483 \text{ kV/m}$$

2.2

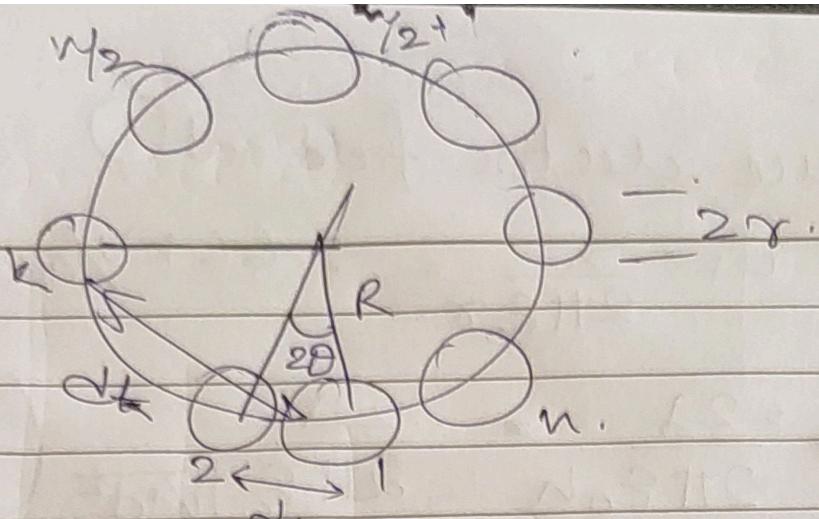

$$2\theta_m = 360^\circ$$

$$n\theta = 180^\circ$$

$$d^2 = 2R^2(1 - \cos 2\theta)$$

$$d = R \sin \theta$$

$$d_k = 2R \sin(k-1)\theta$$

$$k = \frac{n}{2} + 3$$

$$d_{n/2+3} = 2R \sin\left(\frac{n}{2} + 2\right) \theta.$$

$$d_{n/2+3} = 2R \sin\left(\frac{n-4}{2}\right) \theta.$$


$$\left(\frac{n}{2} + 2\right)\theta + \left(\frac{n-4}{2}\right)\theta = n\theta = 180^\circ$$

$$GMR = \left\{ \gamma' \prod_{k=2}^n 2R \sin(k-1)\theta \right\}^{1/n}$$

$$= \left\{ \gamma' (2R)^{n-1} \prod_{k=2}^n \sin(k-1)\theta \right\}^{1/n}$$

$$GMR = \left\{ \gamma' (2R)^{n-1} \prod_{k=1}^{n-1} \sin k\theta \right\}^{1/n}$$

2.11

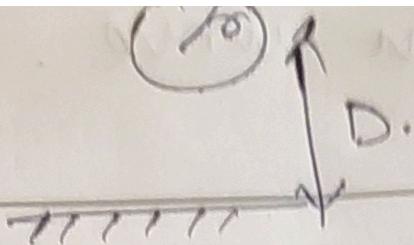


$$L = 0.4605 (\log Y_0 + \log Y_{2D})$$

$$= 0.4605 \left(\log \frac{2D}{e^{-Y_0} \cdot 1.956} \log \frac{1}{206708} \right)$$

$$L = 1.493 \text{ mH/km.}$$

2.12

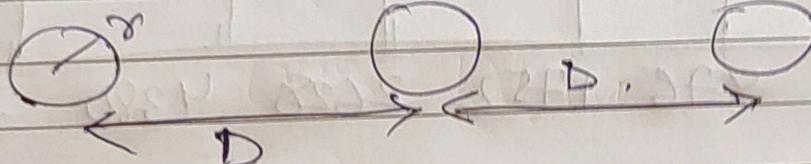

$\gamma = 1.25 \text{ cm}$

$D = 3 \text{ cm}$

$$L_a = 2 \times 10^{-7} \left(\ln \frac{1}{\gamma'} + \ln \sqrt{3} D^2 + \sqrt{3} j \ln \sqrt{Y_2} \right) \text{ H/m.}$$

$$L_a = (1.22 - 0.12j) \text{ mH/km.}$$


$$L_B = 2 \times 10^{-7} \left(\ln \frac{1}{\gamma'} + \ln D + \sqrt{3} j \ln (1) \right) \text{ H/m.}$$

$$L_B = 1.14 \text{ mH/km.}$$

$$L_C = 2 \times 10^{-7} \left(\ln Y_0 + \ln \sqrt{2} D^2 + \sqrt{3} j \ln \sqrt{2} \right) \text{ H/m.}$$


$$L_C = (1.22 + 0.12j) \text{ mH/km.}$$

load duration curve
load (MW)

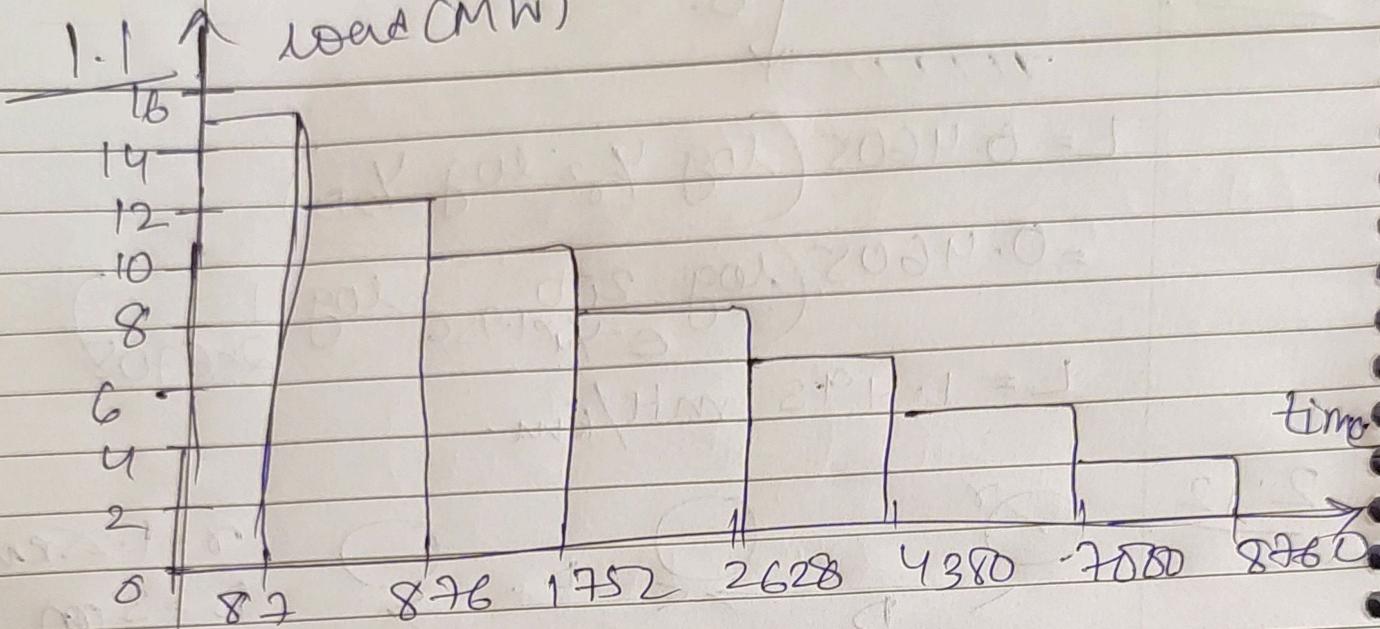

$$\text{avg load} = \frac{\text{Units generated}}{\text{time}} = 5.827 \text{ MW}$$
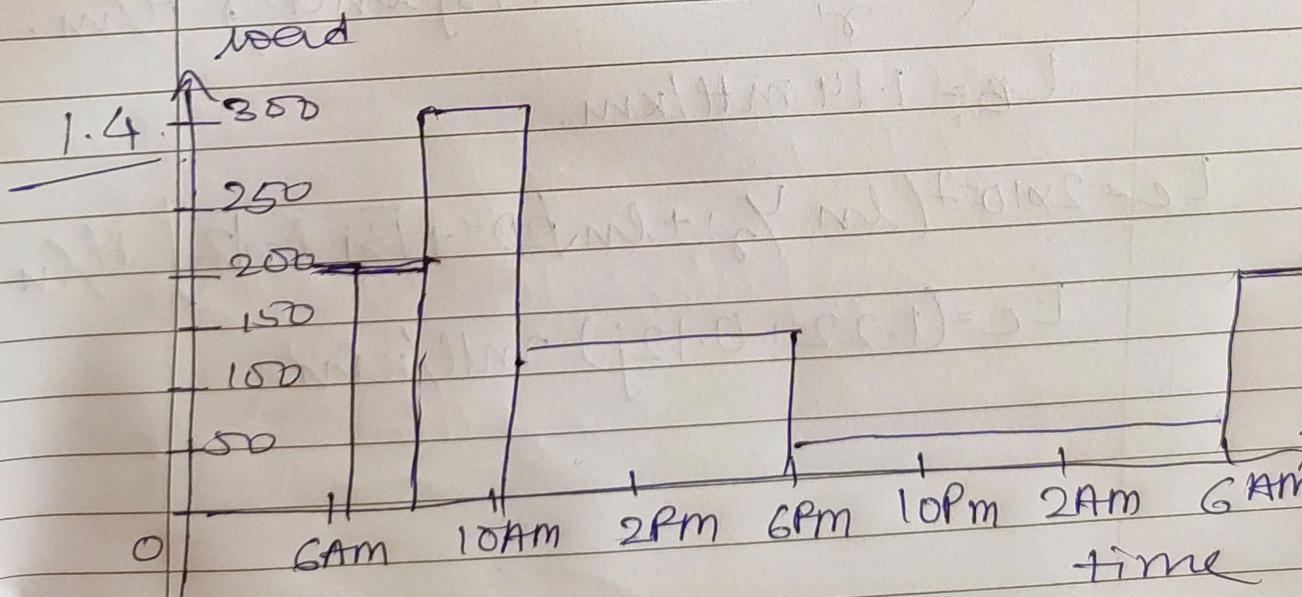
$$\text{load factor} = \frac{\text{avg load}}{\text{max load}} = 0.389$$



Daily Energy produced = 2200 MWhr.

$$\text{load factor} = \frac{2200}{24 \times 300} = 0.3055$$

$$\text{diversity factor} = \frac{100 + 150 + 50 + 20}{300} \\ = 1.067.$$