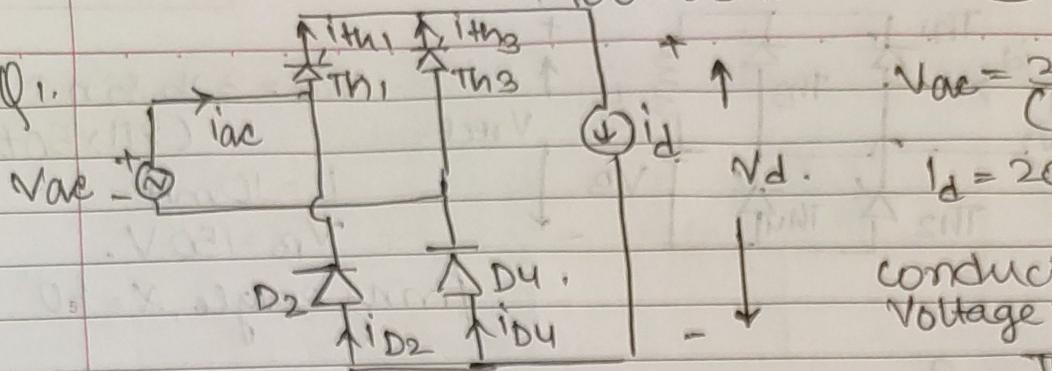


# Test PE Mansi Uniyal

Date \_\_\_\_\_ Page \_\_\_\_\_ A.

Q1.



$$V_{ac} = \frac{325}{\sqrt{2}} \sin(2\pi \times 50t)$$

$$I_d = 20A.$$

conduction

$$\text{voltage } I = 1V$$

D2

conduction

$$\text{voltage } I = 1V.$$

D4

$$|Th_1 \text{ waveform}| = 45^\circ$$

wrt  $V_{ac}$

$$|Th_3 \text{ waveform}| = 225^\circ$$

wrt  $V_{ac}$

conduction





$$|Th_1| = 2V$$


Th1

conduction

$$|Th_3| = 2V.$$

Th3

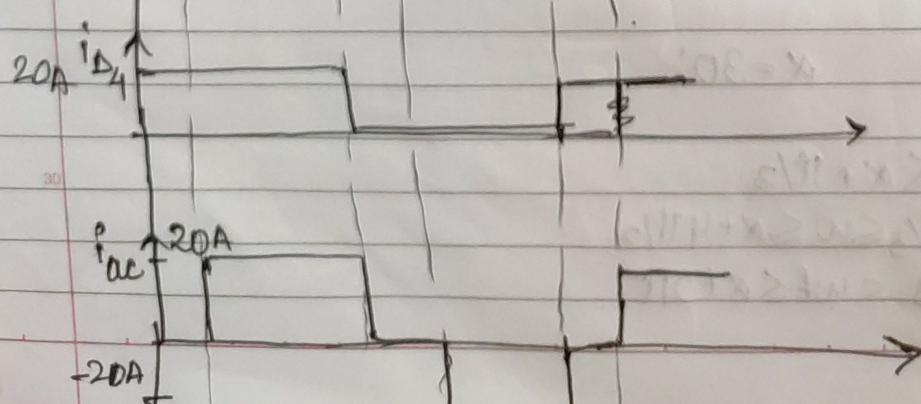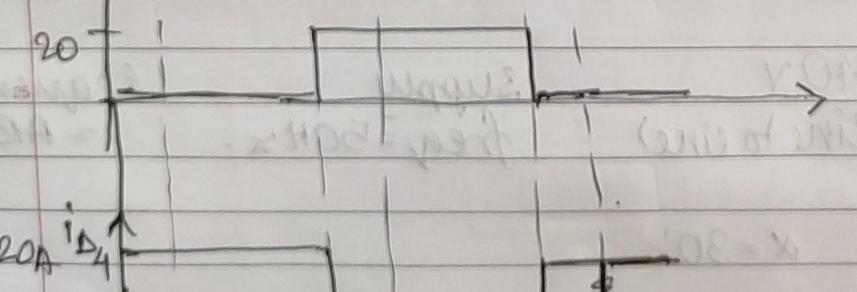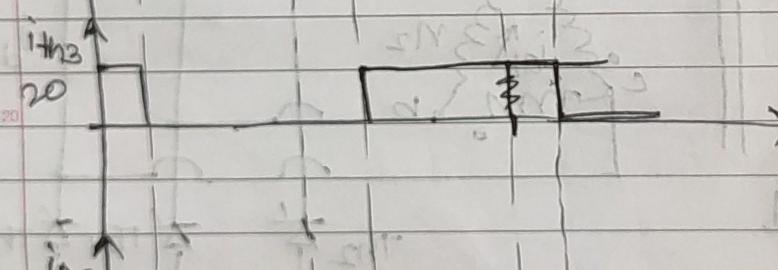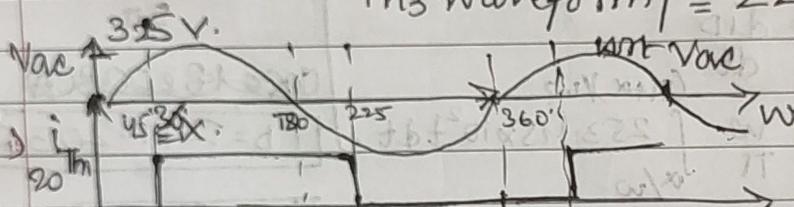


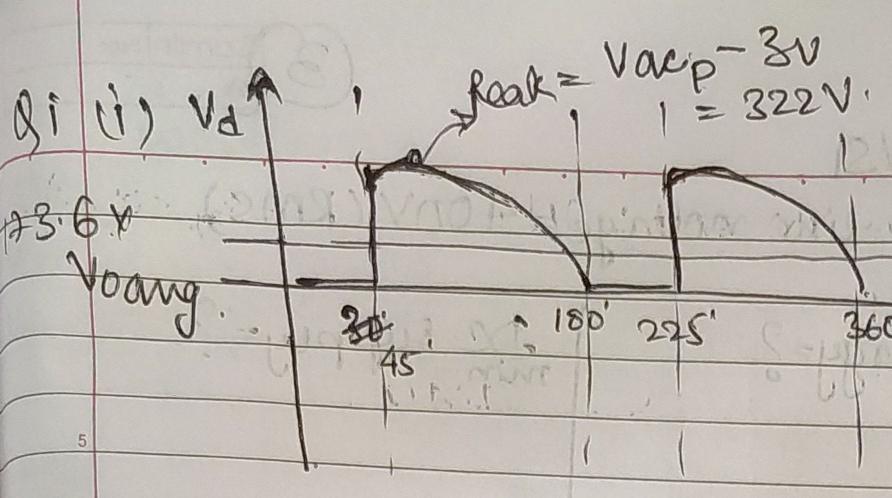

(ii)  $V_{TH_1} = ?$  }  
 $V_{D_2} = ?$  } turnoff.


when  $V_{TH_1}$  stops conducting

$$V_{TH_1} = 323V.$$

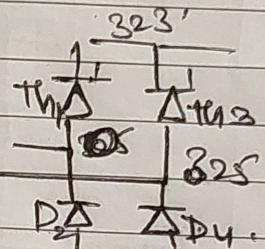

When  $D_2$  stops conducting.

$$V_{D_2} = 322V$$

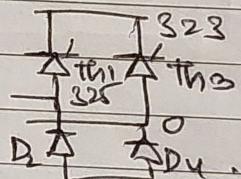

(iii) displacement factor  $\alpha_A = ?$  for operating angle  $\theta = 45^\circ$

$\frac{V_{AC}}{V_{DC}}$

$$= \cos 45^\circ$$

$$= \cos (45/2)^\circ$$

$$= 0.98$$

$$= 0.9238795.$$

(1) c.

Camlin Page  
Date / /

Q1 (iv) firing angle ( $\alpha$ ) = ?

if avg load power =  $2000 \text{ kVA}$ .

$$V_{avg} = \frac{325}{\pi} (1 + \cos \alpha) . \quad I_d = 20 \text{ A} .$$

$$2000 = \frac{325}{\pi} 20 (1 + \cos \alpha).$$


$$P_0 = V_{avg} I_d .$$

$$1 + \cos \alpha = 0.966$$

$$\cos \alpha = -0.34$$

$$\alpha = 91.94^\circ$$

firing angle,

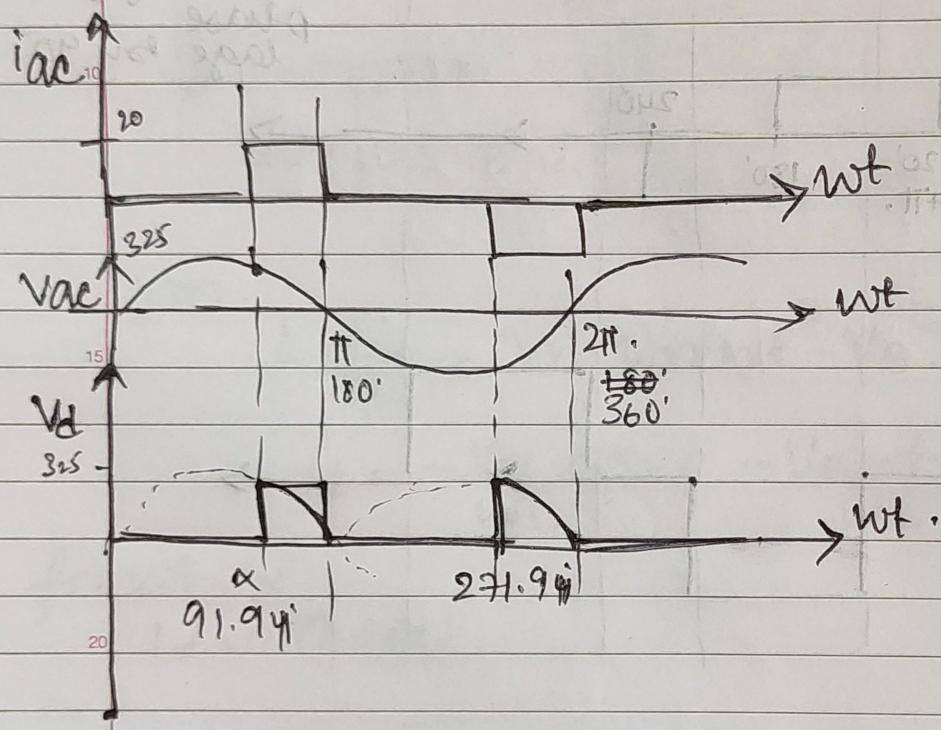

Q2 (i)

$$V_{AC} = 325 \sin(2\pi \times 50t)$$

$$L = 10 \text{ mH}$$

$$V_B = 150 \text{ V}$$

$$\alpha = 60^\circ = \frac{\pi}{3} = 1.0472.$$

$$V_m = 325 \text{ V}$$

$$W = 100\pi = 314.16.$$

$$T = \frac{1}{W} = 0.02.$$

$$F = \frac{SD}{W}$$

$$R = 0 :$$

$$\frac{2V_m \cos \alpha}{\pi} = 2 \times 325 \cos(\pi/3) = 103.45 \text{ V.}$$

$$V_B > \frac{2V_m \cos \alpha}{\pi}$$

$$150 > 103.45 \text{ V.} \quad \text{system in DCM.}$$

$b > 0$ .

$$L \frac{di_d}{dt} = V_m \sin wt - V_B. \quad \text{possible}$$

$$i_d = -\frac{V_m \cos wt - V_B w t + C}{WL} \quad \begin{matrix} \rightarrow \text{integrating} \\ \text{factor} \end{matrix}$$

for  $wt = \alpha$

$$i_d = 0 \text{ (DCM)}$$

$$0 = -\frac{V_m \cos \alpha - V_B \alpha}{WL} + C.$$

$$C = \frac{V_m \cos \alpha + V_B \alpha}{WL} = 101.33$$

$$i_d = -103.45 \cos(100\pi t) - 47.35 (100\pi t) + 101.33,$$






if  $wt = \alpha$ ,  $i_d = 0$ .

$$0 = -103.45 \cos \beta - 47.35 \beta + 101.33.$$

$$\beta < 240^\circ$$

$$\boxed{\beta \approx 104^\circ}$$

Q2 (ii).

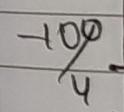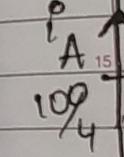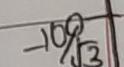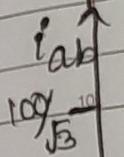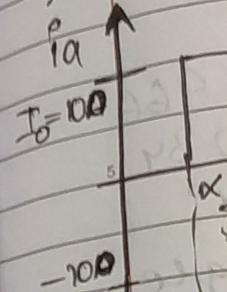

$$i_{\text{avg}} = \frac{2}{T} \int_{\omega T}^{\omega T + \frac{T}{2}} i_a(t) dt.$$


$$= \frac{2}{T} \int_{\omega T}^{\omega T + \frac{T}{2}} (-103.45 \cos \omega t - 47.75 \omega t + 101.38) dt.$$

$$i_{\text{avg}} = \frac{2}{T} \left[ 103.45 \sin \omega t - 47.75 \frac{\omega t^2}{2} + 101.38 t \right]_{\omega T}^{\omega T + \frac{T}{2}}$$

$$i_{\text{avg}} = \frac{2}{T} [0.497 - 0.9984 + 0.885],$$

$$i_{\text{avg}} = \frac{2}{T} \times \frac{3836}{10000} = \frac{100 \times 3836}{10000}$$

$$i_{\text{avg}} = 38.36 \text{ A}$$

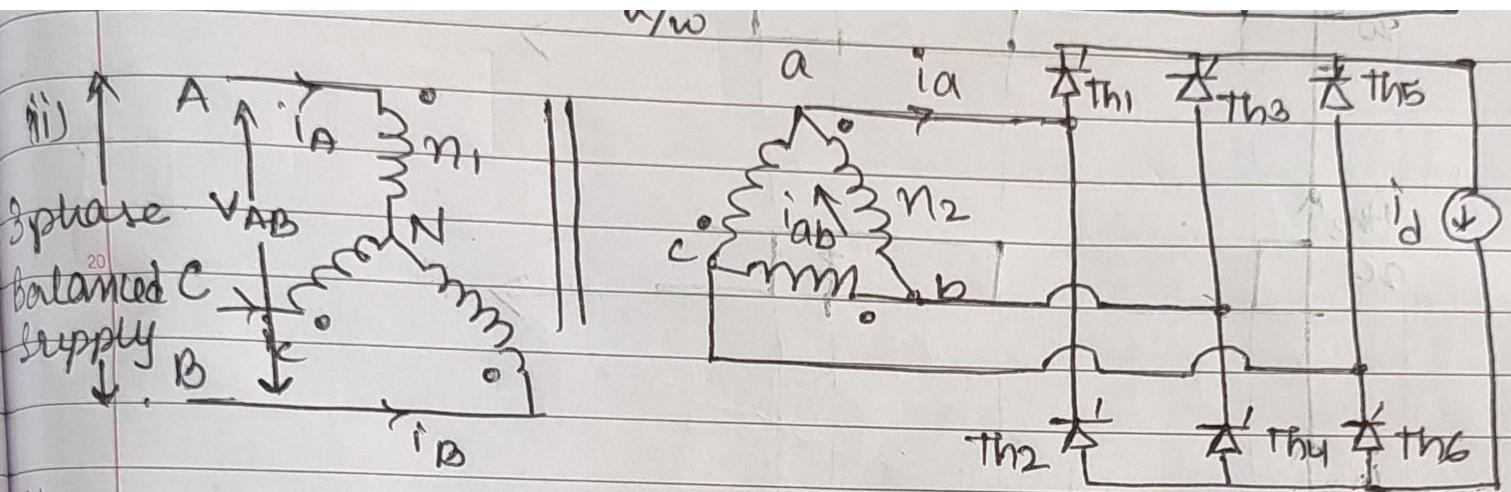

25.  $V_{AB}$ . Voltage supply = 440 V  
 (line to line)

Supply freq = 50 Hz.

Sequence = ABC

$$n_1 : n_2 = 4 : 1$$

$$i_d = 100A \quad \alpha = 30^\circ$$

$$i_a = I_0, \quad \alpha < \omega t \leq \alpha + \pi/3$$

$$i_a = -I_0, \quad \alpha + 2\pi/3 \leq \omega t \leq \alpha + 4\pi/3$$

$$i_a = 0, \quad \alpha + 4\pi/3 \leq \omega t \leq \alpha + 2\pi$$

$$i_a = 0, \quad \text{else.}$$

(2)

3

Camlin Page  
Date / /

$$i_A = n_s = \gamma_4,$$

$$i_a \text{ in P}$$

$$|i_A| = |\bar{i}_a|$$

same phase

Q2 (ii).

$i_a$

$\bar{i}_a = 10\angle 0^\circ$

5

$\alpha + \frac{\pi}{3}$

$150^\circ$

$\alpha + 4\frac{\pi}{3}$

$270^\circ$

$390^\circ$

wt

-10

30

$\alpha - \frac{\pi}{6}$

$90^\circ$

$\alpha + 2\frac{\pi}{3}$

$210^\circ$

$\alpha + 5\frac{\pi}{3}$

$330^\circ$

$\alpha + 2\pi$

$i_{ab}$

10

$\frac{10}{\sqrt{3}}$

$\alpha + \frac{\pi}{16}$

$60^\circ$

$120^\circ$

$\alpha + \pi$

$180^\circ$

$240^\circ$

$i_A$

15

$\frac{15}{\sqrt{3}}$

$109$

$\frac{109}{\sqrt{3}}$

③ A

Camlin Page  
Date / /

Q3. i) 3phase VSI 120° conduction mode (star)


$$R_L = 5\Omega/\text{phase}$$

desired phase sequence  $\rightarrow RYB$ .

freq. of inverter output voltage = 50 Hz.


DC supply

(a) circuit diagram

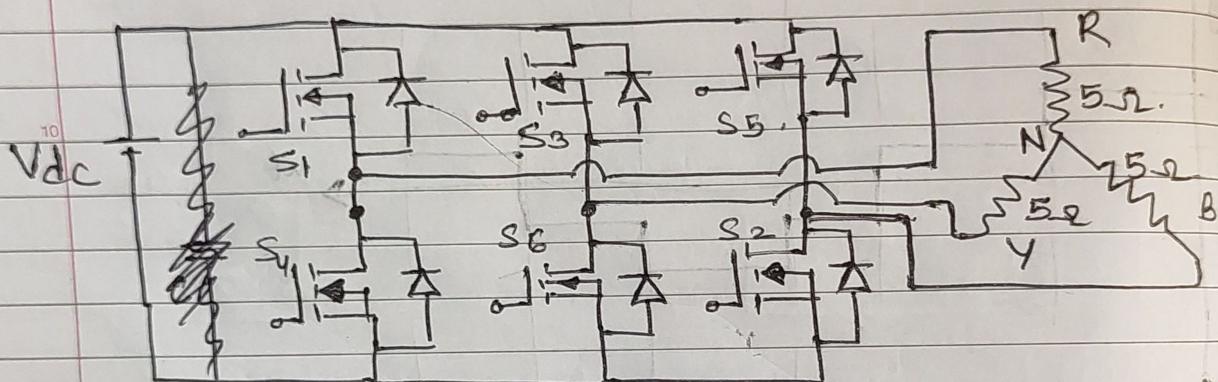


3. waveforms.

(b)

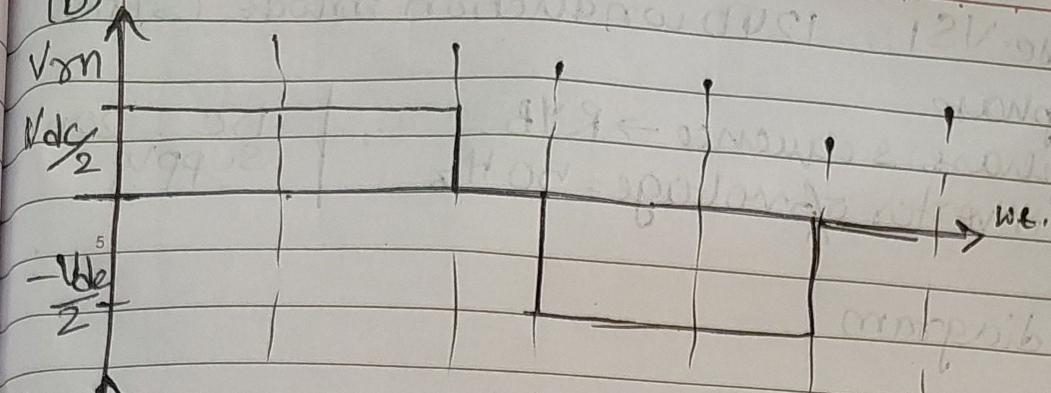

(ii)

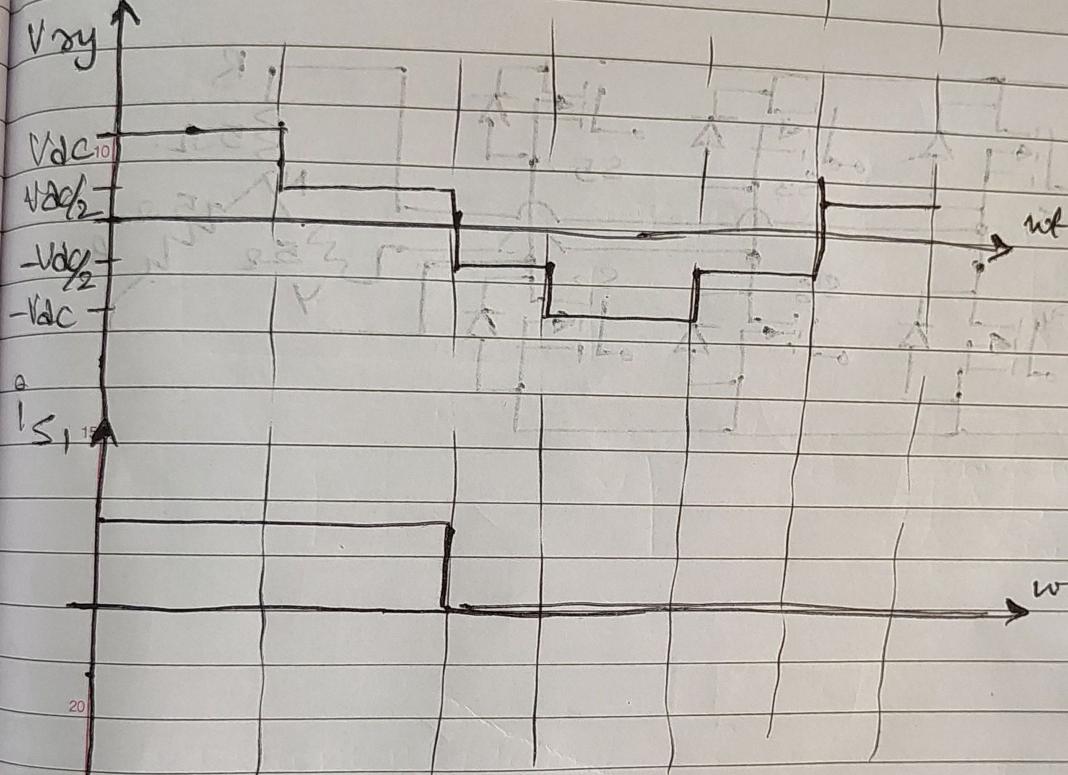

(iii)

20

me  
of

Q 3. (b) 3phase VSI.

Rated line-line voltage = 400V (RMS).

Switching strategy = ?

DC supply = ?  
min.

5

10

15

20

25

30

(ii) Applications of AC-AC converters + type.

- Speed controlling of machines for low freq.

and variable magnitude applications.

circuit diagram

- AC voltage controller, Lighting control, speed of FAN, Static AC switches (temp. control), Pump / Hoist Drivers.

Q4.  
(i)

(b) Bi polar sinusoidal pulse width modulation scheme

$$m_f = \frac{F_s}{F_{control}} = \frac{F_s}{50} \rightarrow \begin{matrix} \text{cutoff} \\ \text{freq.} \end{matrix}$$

(desired O/P)

(c) Unipolar sinusoidal pulse width modulation  
 Next freq. after fundamental freq. scheme.  
 $= (2m_f + 1)$  fundamental.

$$\text{cutoff freq.} = (2F_B \pm 50) \text{ Hz.}$$

$$L = (2F_s \pm 50),$$

$\omega = 2\pi\sqrt{LC}$

(ii) 2 applications of AC-AC converters + type.

20

