

Power Electronics Lab


Experiment-2

-Swarnendu Paul
19EE3FP18


Part-A:

1.

Circuit:

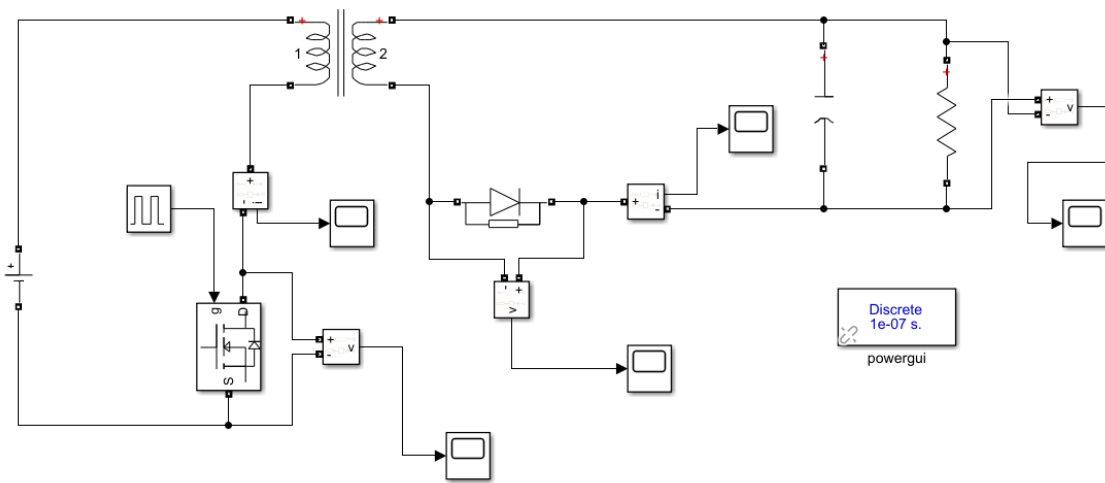


Output voltage:

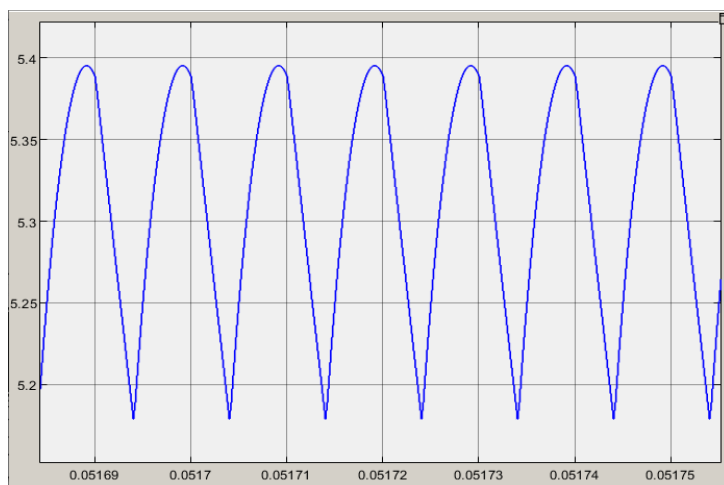


$$V_{avg} = 5.313V$$

MOSFET voltage:

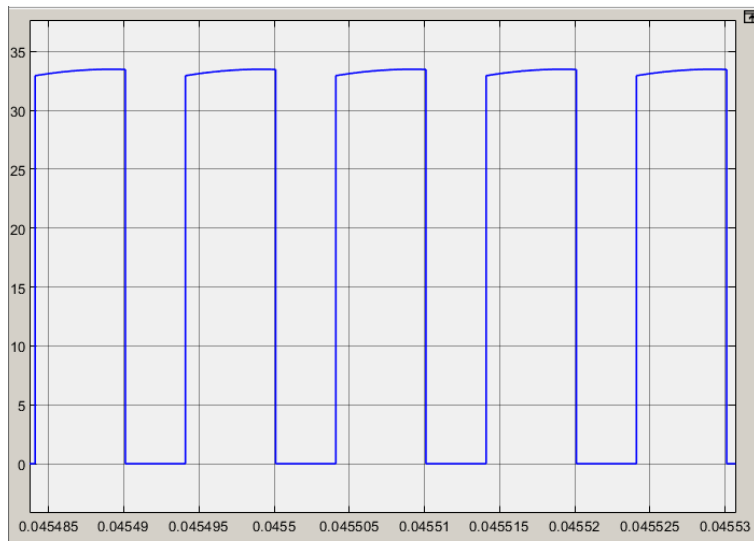


Mean = 20V

MOSFET current:

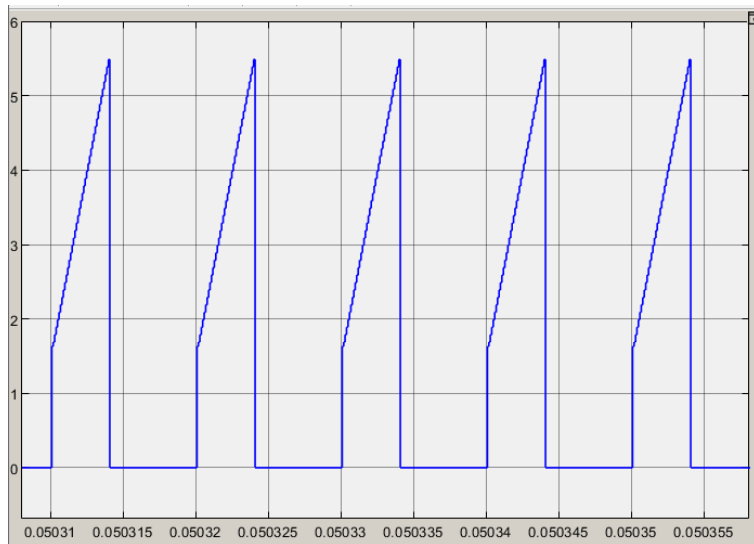


Mean=1.416A

Diode Voltage:

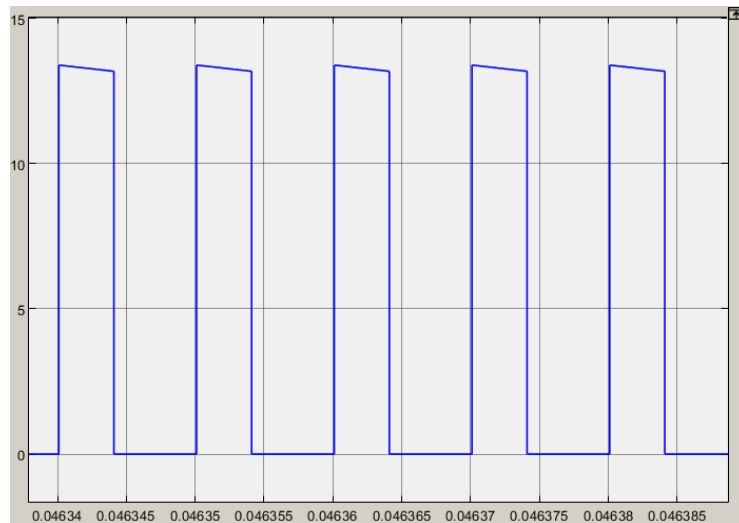

Mean = 5.313V

Diode current:

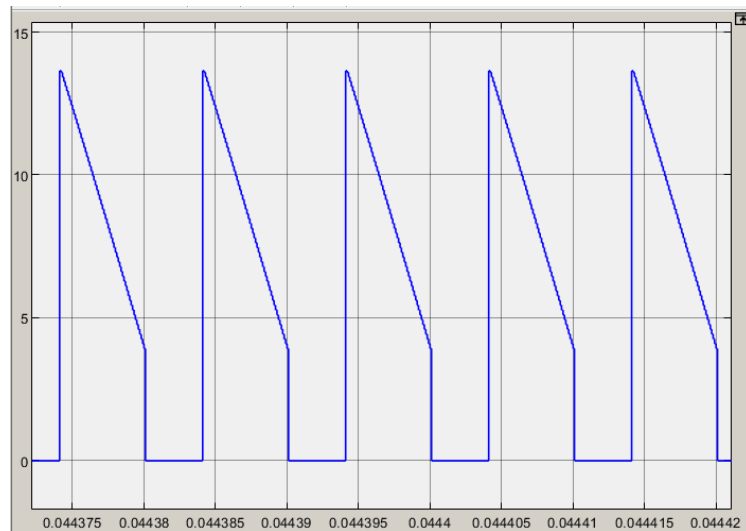


Mean= 5.313A

4.

Load resistance is varied keeping everything else the same.


R_{Load}	V_{out}	Mode
1	7.825	CCM
1.5	7.826	CCM
2	7.826	CCM
2.5	8.526	DCM
3	9.338	DCM
3.5	10.008	DCM

V_{out} vs R_{Load} plot:-

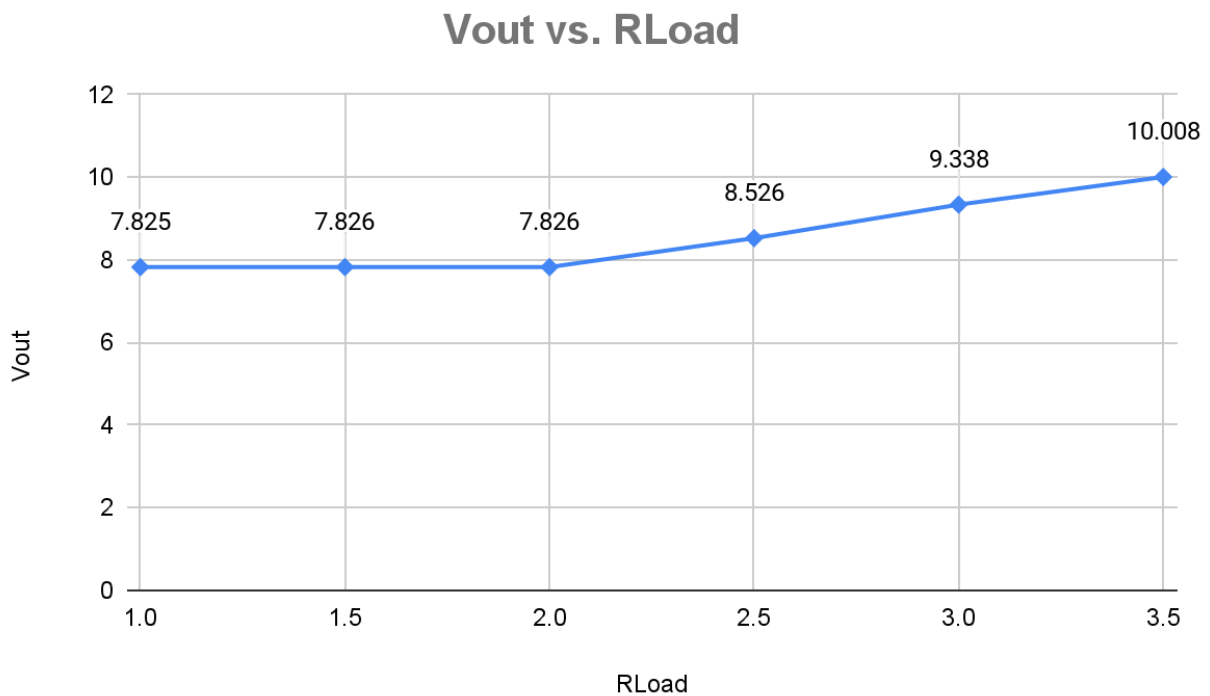


Part B:

Circuit:

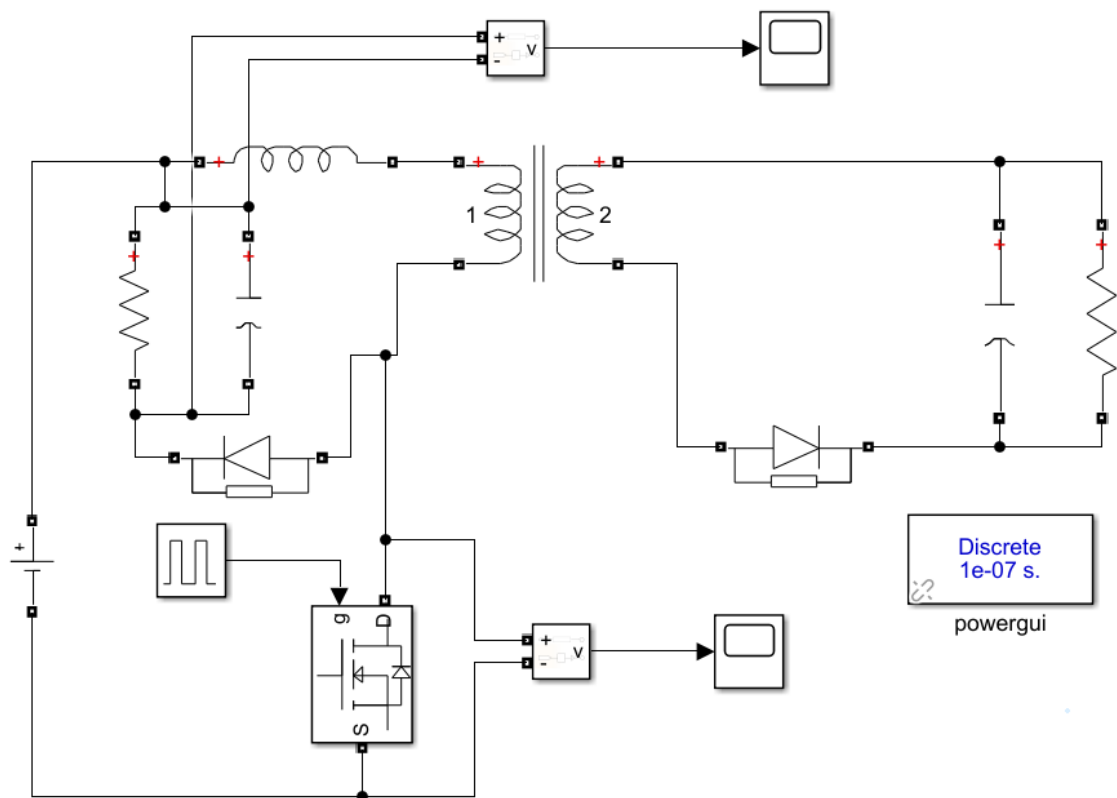


Steady state voltage across switch:

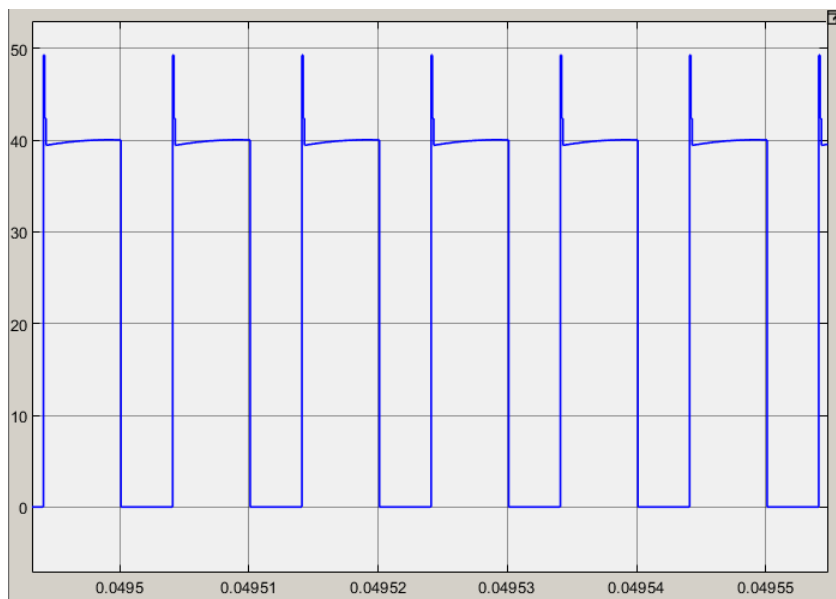

Voltage across Snubber capacitor:

$$V_{avg} = 25.96V$$

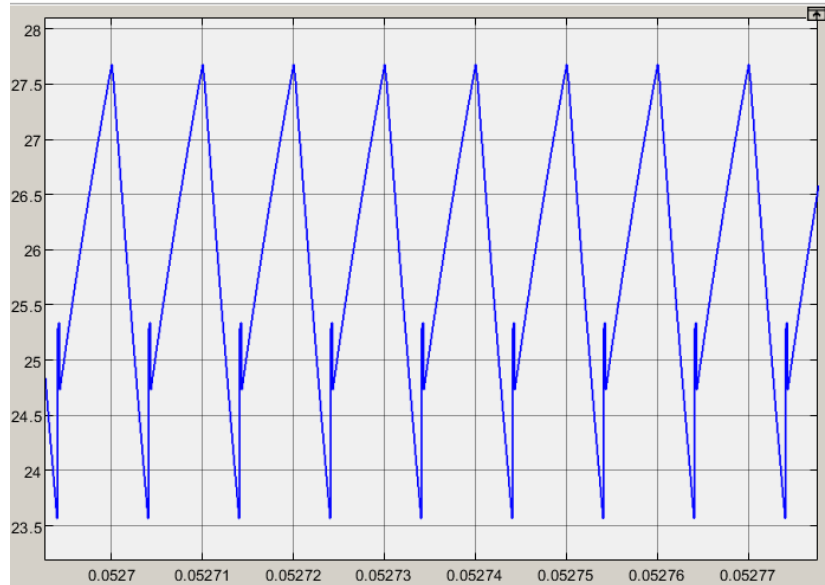

Power dissipation in R_d :

Average voltage across Snubber capacitor = 25.96V

$$\text{So power dissipated across } R_d = \frac{25.96^2}{5000} = 0.1348W$$

-----X-----X-----