

NAME : ARUNDHUTI NASKAR

ROLL NO : 19EE10009

POWER ELECTRONICS LAB

**EXPERIMENT 1 : BUCK, BOOST, BUCK-BOOST
CONVERTER**

PART A :


BOOST CONVERTER :

- Input Voltage (V_{in}) = 24V
- Inductor $L = 115\mu\text{H}$
- Capacitance $C = 54\mu\text{F}$
- Load resistance $R_L = 11.52\Omega$
- Switching Frequency = 50 kHz
- Duty Cycle = 0.5
- MOSFET and diode resistance as $1\mu\Omega$
- diode voltage drop as 0.
- Parasitic resistance of inductor case (i) - $r_l = 0$ in and case (ii) $r_l = 5\%$ of R_L .
- Duty ratio is varied in range 0.1 to 0.9 in steps of 0.1

I.


Duty ratio	$V_{in}(V)$	$V_{out}(V)$ Ideal Case [$r_l = 0$]	Gain in Ideal case	$V_{out}(V)$ $r_l = 5\%$ of r_l	Gain in case $r_l = 5\%$ of R_L
0.1	24	26.7	1.1125	25.14	1.0475
0.2	24	30.05	1.2708	27.87	1.16125
0.3	24	34.4	1.433	31.2	1.3
0.4	24	40.1	1.6708	35.18	1.465
0.5	24	48.32	2.0133	40.29	1.6787
0.6	24	60.53	2.522	45.12	1.88
0.7	24	80.81	3.367	51.97	2.1654
0.8	24	121.6	5.0667	53.99	2.249
0.9	24	243.3	10	40.54	1.689

GAIN vs DUTY RATIO in IDEAL case

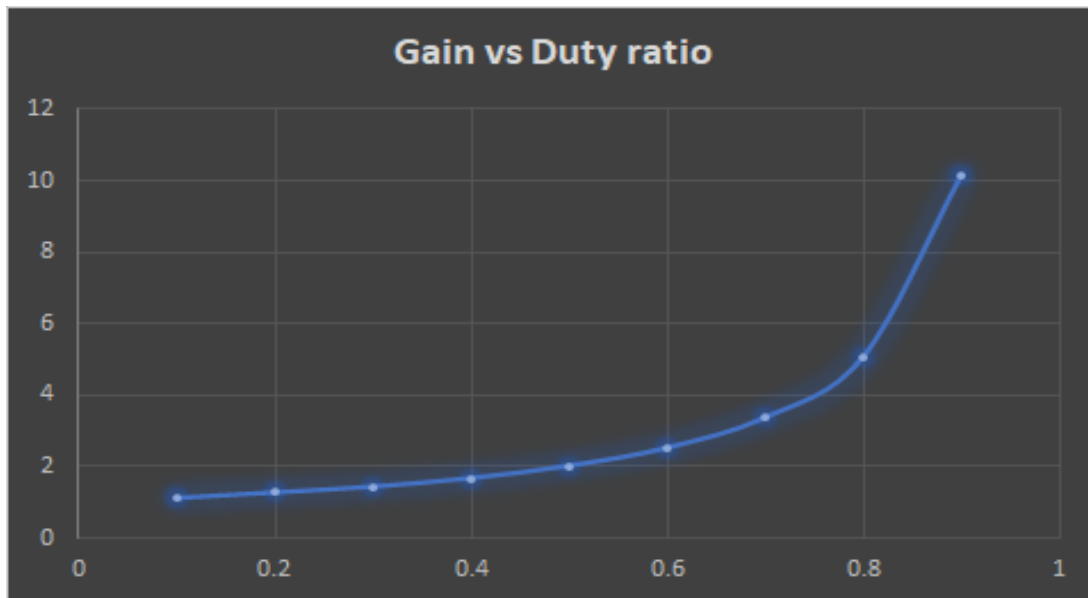


The graph follows the gain of boost converter i.e. $\text{Gain} = 1/(1-D)$. This is the ideal case where there is no parasitic resistance in induction. The curve is exponential and increases with duty ratio.

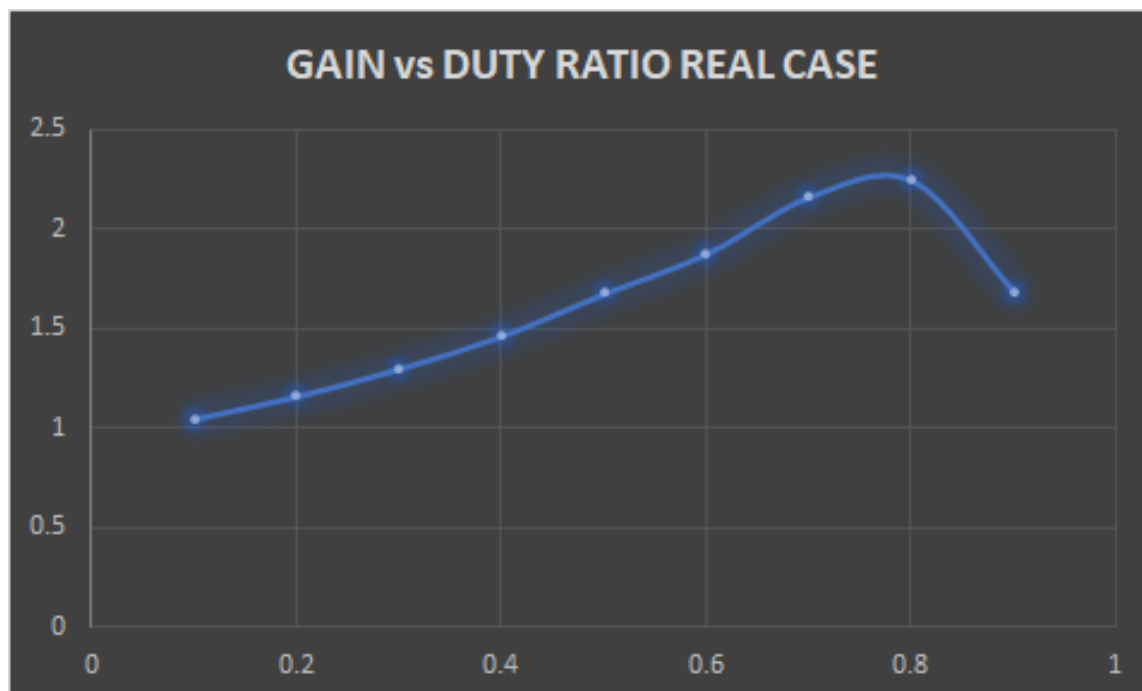GAIN vs DUTY RATIO in CASE II $r_l = 5\%$ of R_L




There is power dissipation in practical cases due to the presence of parasitic inductance. Hence its not exactly a rising exponential curve. For a very high value of duty ratio, gain decreases as more power gets dissipated.

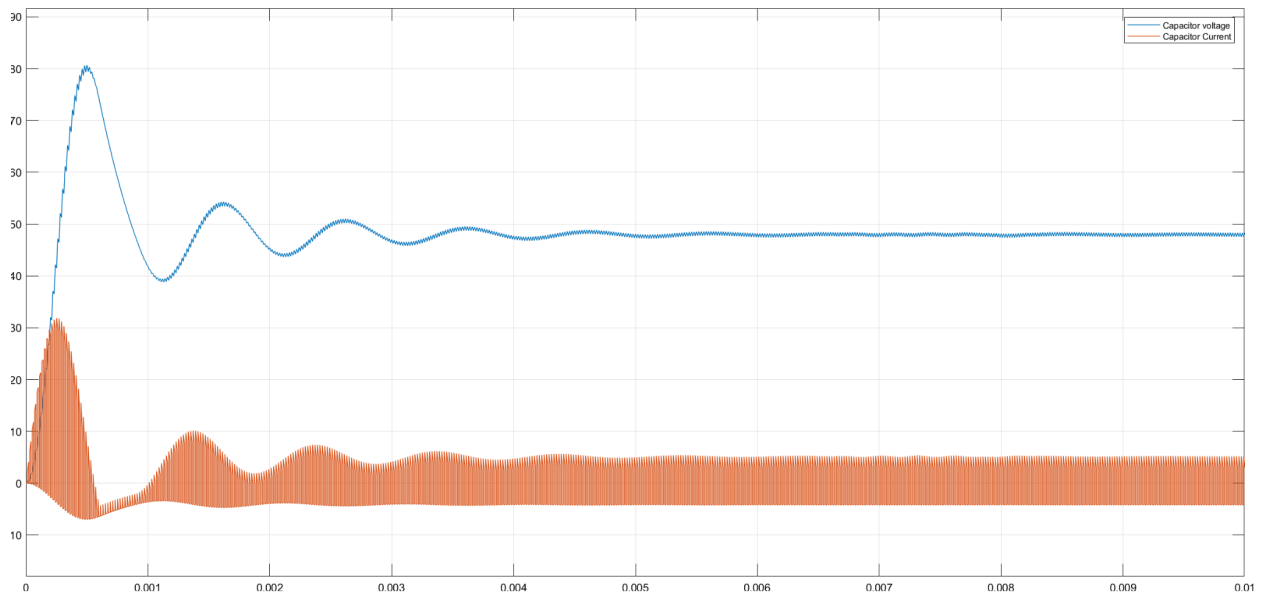
- II. Capacitor voltage and current waveforms in the ideal case at $D=0.5$
 RMS Value of capacitor current = 5.563 A



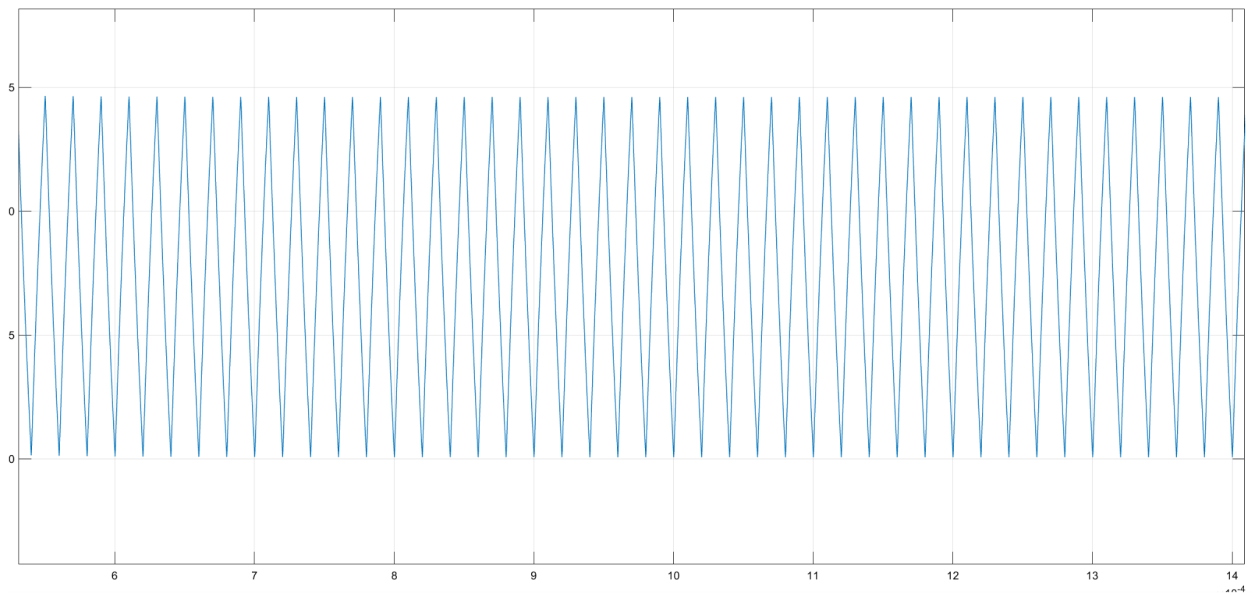- III. When $r_l = 5\%$ RL, the inductance for which converter falls under CCM mode.
 For CCM mode Inductor value = 13.3uH
 The waveform of the practical inductor current




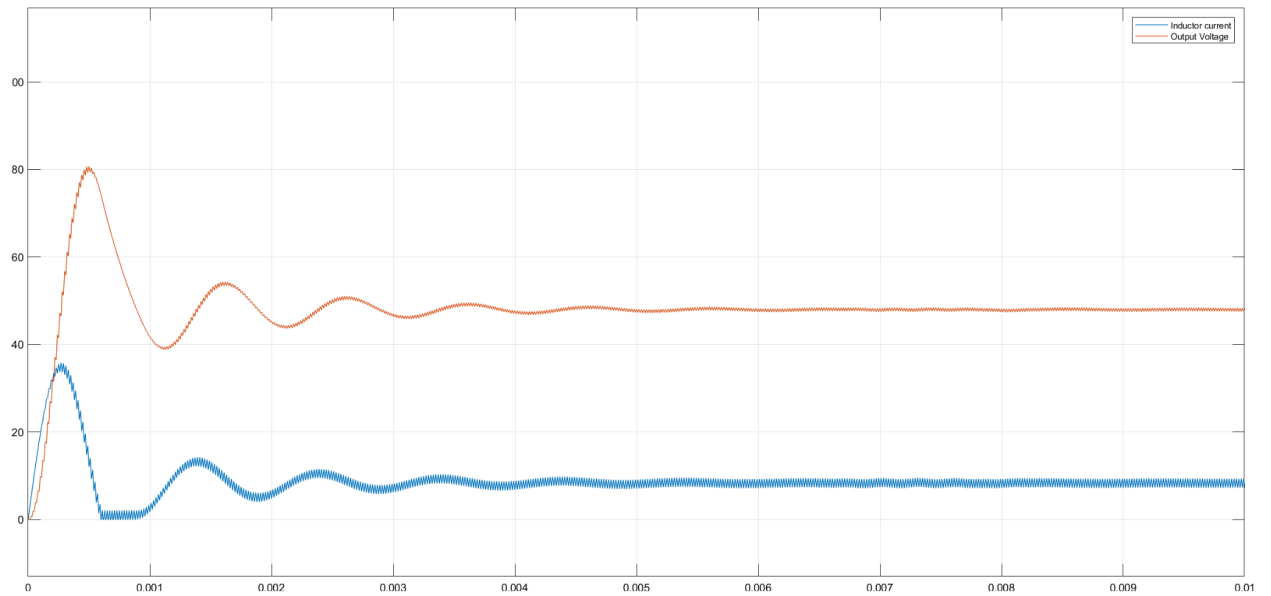IV. For case (i) with $D=0.5$, Initial output voltage = 0 V, Plot of Inductor current, and output voltage builds up from starting to steady state.




INDUCTOR VOLTAGE

Transient Current

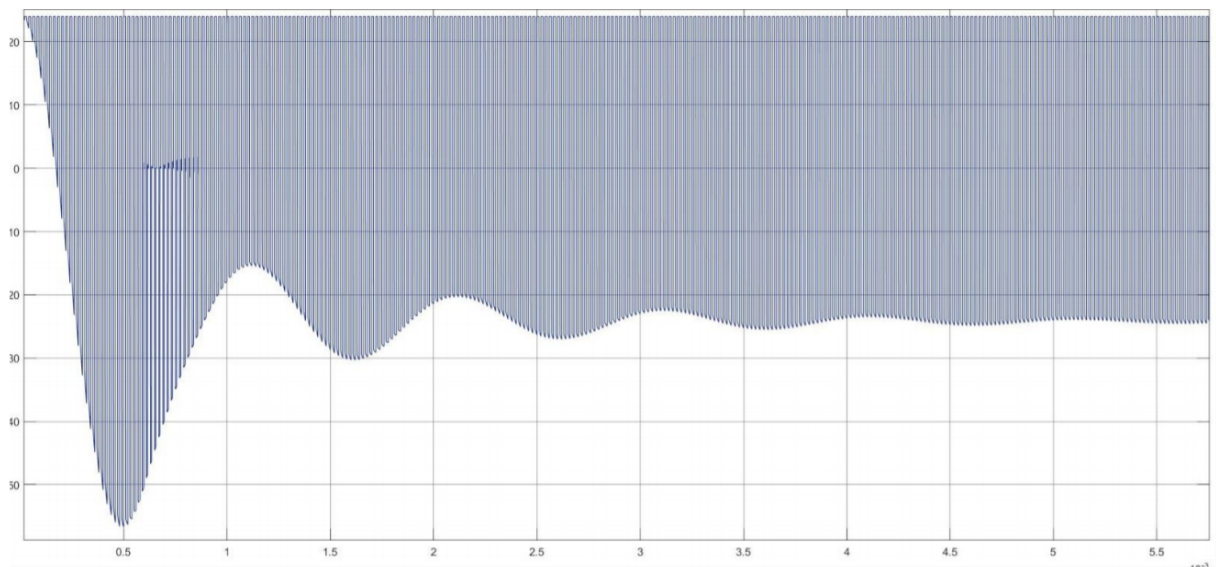

Steady state condition

CAPACITOR CURRENT
Transient State

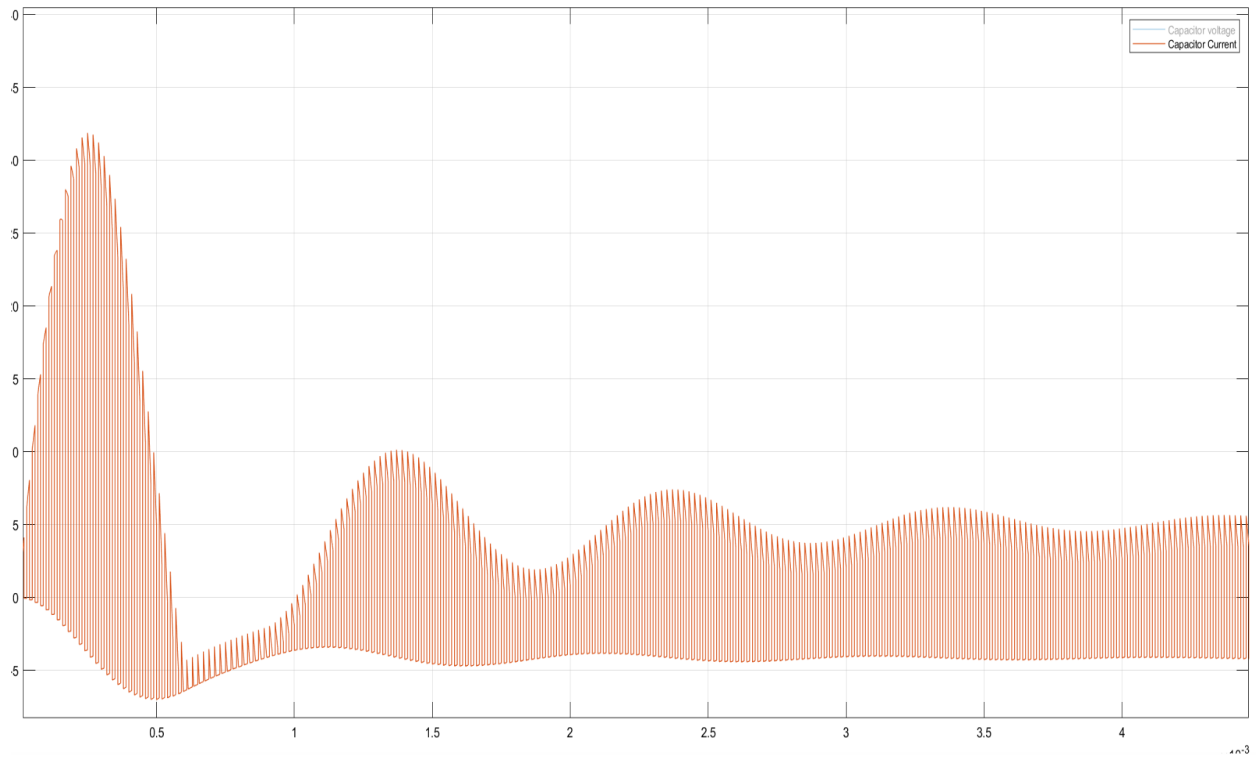


Steady State

V. The load is varied between 0.2 PU to 1 PU in steps of 0.1. Plot of load vs efficiency characteristics

LOAD (PU)	Efficiency
0.2	0.86
0.3	0.87
0.4	0.88
0.5	0.887
0.6	0.896
0.7	0.906
0.8	0.91
0.9	0.92

1	0.93
---	------

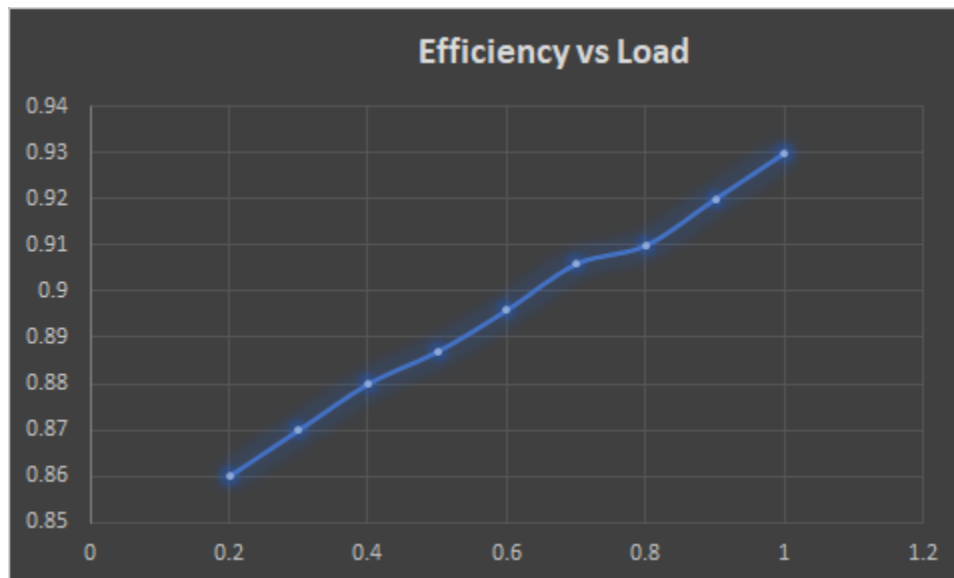

PART - B

BUCK-BOOST CONVERTER :


- Input Voltage (V_{in}) = 57V
- Inductor $L = 226\mu H$
- Capacitance $C = 54\mu F$
- Load resistance $R_L = 11.52\Omega$
- Switching Frequency = 50 kHz
- Duty Cycle = 0.5
- MOSFET and diode resistance as $1\mu\Omega$
- diode voltage drop as 0.
- Parasitic resistance of inductor case (i) - $r_l = 0$ in and case (ii) $r_l = 5\%$ of R_L .
- Duty ratio is varied in range 0.1 to 0.9 in steps of 0.1


I.

Duty ratio	$V_{in}(V)$	$V_{out}(V)$ Ideal Case [$r_l = 0$]	Gain in Ideal case	$V_{out}(V)$ $r_l = 5\%$ of r_l	Gain in case $r_l = 5\%$ of R_L
0.1	24	6.74	0.118	25.14	1.0475

0.2	24	14.53	0.2508	27.87	1.16125
0.3	24	24.85	0.4359	31.2	1.3
0.4	24	38.56	0.6765	35.18	1.465
0.5	24	57.66	1.0115	40.29	1.6787
0.6	24	86.01	1.5089	45.12	1.88
0.7	24	131.5	2.307	51.97	2.1654
0.8	24	223.2	3.9157	53.99	2.249
0.9	24	439.8	8	40.54	1.689

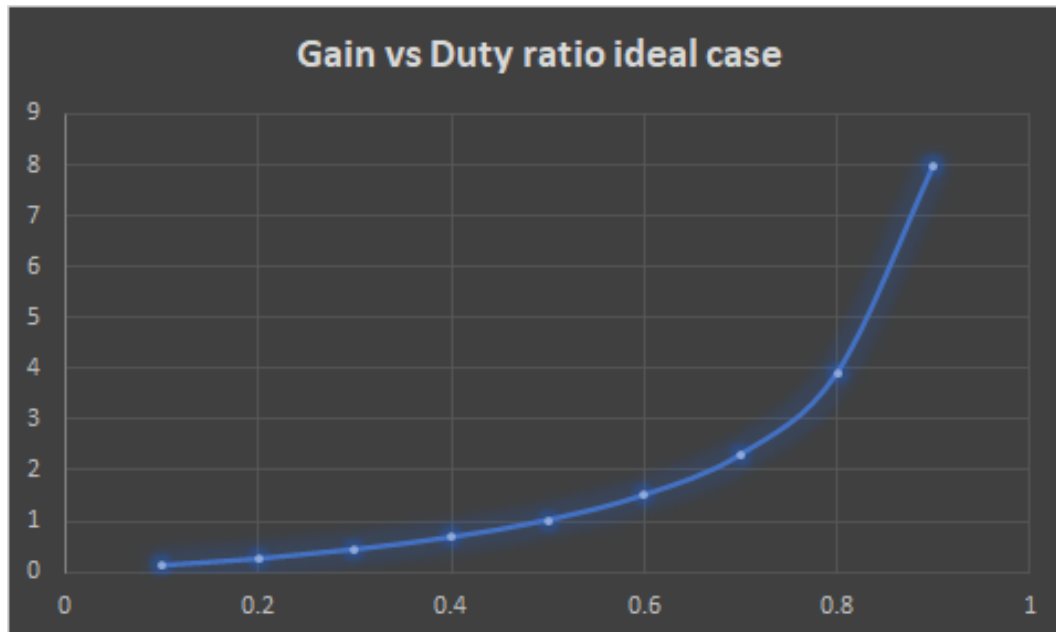For ideal case graph is again exponential, according to the gain formula $\text{Gain} = D/(1-D)$. For practical case where there is parasitic resistance with the inductor, hence there is power dissipation and curve isn't exactly exponential. With high duty ratio there is a greater power loss and gain decreases.



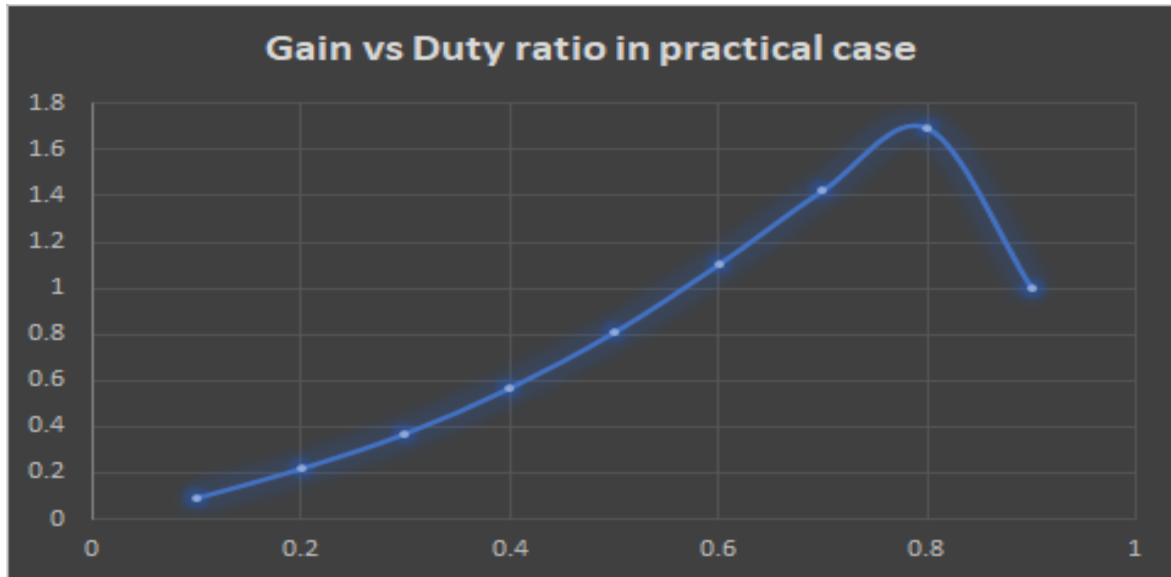

II. CASE I :

Case 1: $V_{in} = 57V$ $C = 59\mu F$ $R_{load} = 11.52\Omega$
 $L = 226\mu H$ $R_L = 0\Omega$
Duty ratio = 0.457

For buck-boost converter to work under CCM condition, $\text{Gain} = \frac{D}{1-D}$ (abs. value)

For DCM $\text{Gain} = \frac{V_{in} D^2 T_{sw}}{2LI_{out}}$

At boundary region, both gain will be same
 $\frac{D}{1-D} = \frac{V_{in} D^2 T_{sw}}{2LI_{out}}$
 $\left(I_{out} = \frac{V_{out}}{R_{load}} \right)$

$f_{sw} = \frac{R_{load} (1-D)^2}{2L}$
 $= \frac{10 \times (1-0.457)^2}{2 \times 226 \times 10^{-6}} = 7.515 \text{ kHz}$

At starting $f_s = 50 \text{ kHz}$, so we can vary switching frequency from 5 kHz slowly to 10 kHz, meaning transition from DCM to CCM state should occur somewhere around this point. ^{Steady state} The current through inductor is observed. When it becomes zero, it means converter operates in DCM.

Switching Frequency (in KHz)	Inductor current (in A)	Mode
5	-0.061	DCM
6	-0.055	DCM
7	-0.050	DCM
8	0.56	CCM
7.2	-0.45	DCM
7.4	-0.010	DCM
7.6	0.164	CCM
7.8	0.33	CCM
7.5	0.032	CCM

Hence we see that around frequency = 7.5 kHz, the converter transitions from DCM to CCM mode.

CASE II : Again, switching frequency is varied from 5 kHz to 10 kHz, and minimum current through inductor under steady state is observed.

Switching Frequency (in KHz)	Inductor current (in A)	Mode
5	-0.043	DCM
6	-0.038	DCM
7	-0.035	DCM
8	-0.0071	DCM
9	0.589	CCM
8.2	0.0566	CCM
8.1	0.0112	CCM

From the table we can clearly observe that when switching frequency is in the range 8-8.1 kHz, the converter transitions from DCM to CCM.

III. Case I : Average input and output current measurement.

Duty Ratio	Input Current (A)	Output Current (A)
0.1	0.2442	0.5619
0.2	0.852	1.261
0.3	1.996	2.157
0.4	4.086	3.347
0.5	8.021	5.002
0.6	15.97	7.468
0.7	34.52	11.54
0.8	91.09	19.36
0.9	379.8	38.21

PART C

DO LATER **** DOUBT


DISCUSSION QUESTIONS :

1. Comment on the comparison of overall (both core and copper loss) loss of the inductor when the inductance is changed from specified value in CCM to critical inductance value. Assume inductor resistance has not changed.

Ans : It is observed from the experiment that when inductance is changed from a specified value in CCM to critical inductance value, core loss increases but copper loss remains constant. Finally when critical state is achieved then, overall loss increases even more.

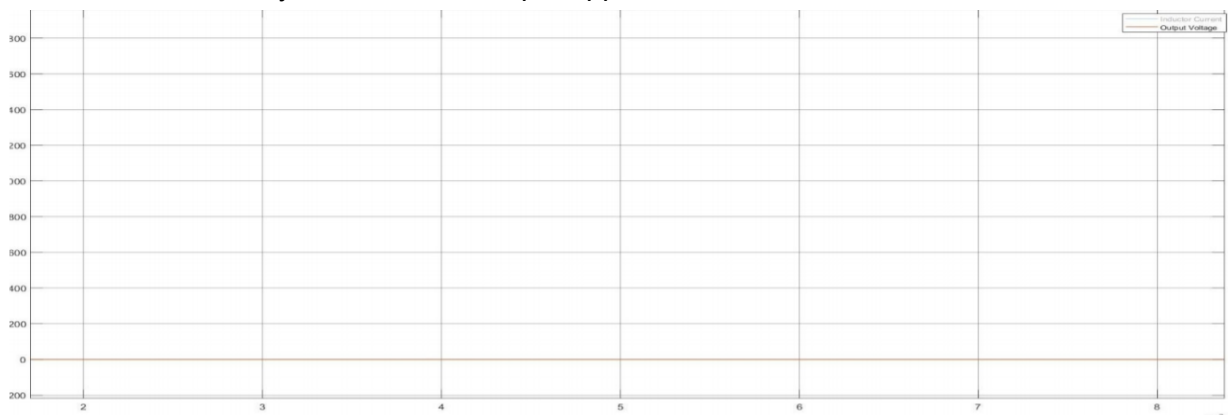2. Assuming ideal boost converter, compare the theoretical and simulated value of V_{out} for duty ratio=1, and write down your observations.

Ans : In theoretical case, the output voltage of ideal boost converter should shoot to infinity. But in the simulation at duty ratio 0.1 , the output appears zero.



3. For a given duty ratio and load, voltage gain is higher in DCM or CCM? Why? (Consider ideal Boost Converter)

Ans : For ideal boost converter, the voltage gain under CCM is greater than DCM condition.

*** doubt***