
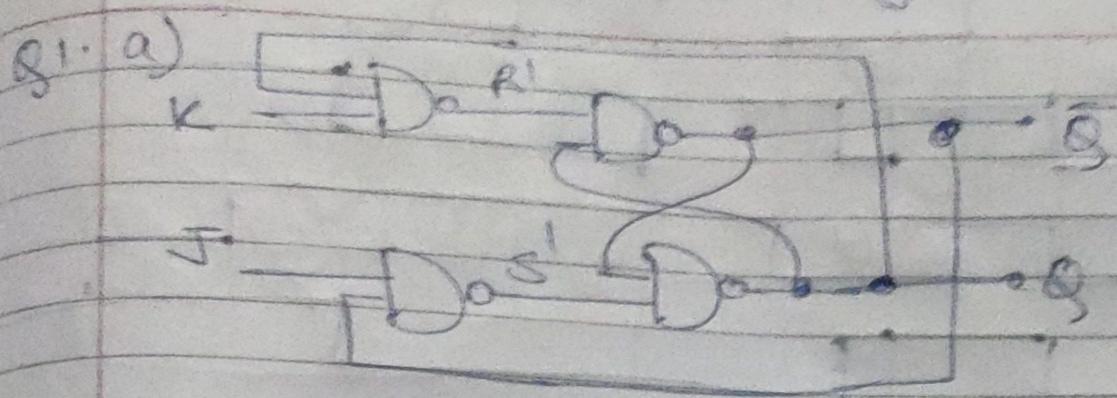


Dee Assignment  
Mawri Qayyal.


QUESTION

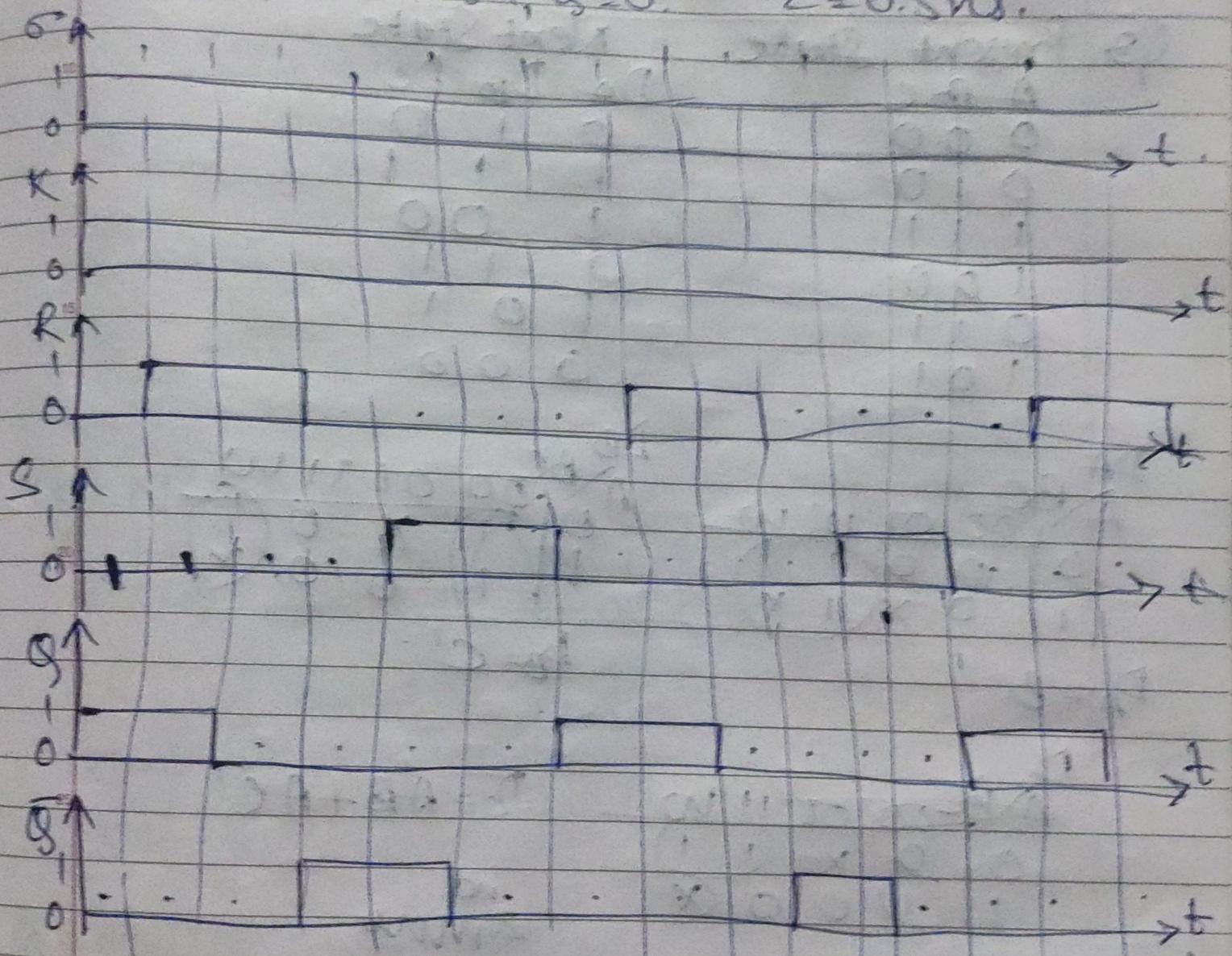

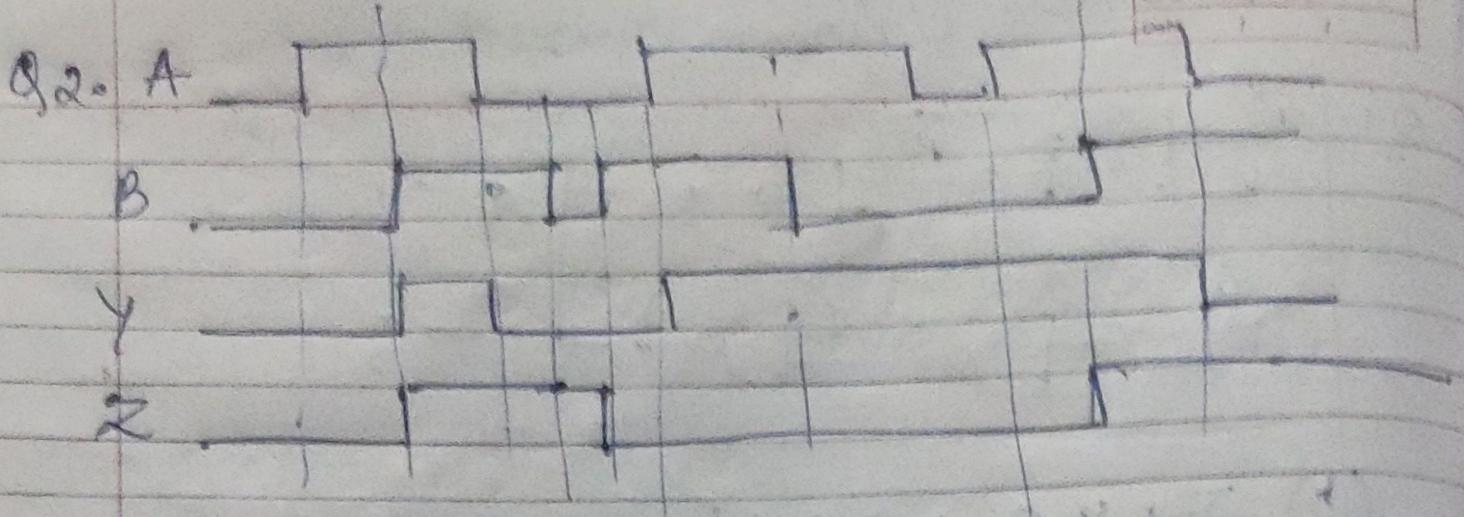(b)  $J=1, K=0 \rightarrow Q=1, Q'=0$ .  $Z=0.5 \text{ ns}$ .



$$f = \frac{1}{T} = \frac{1}{6 \times 0.5} = \frac{1}{3 \text{ ns}} = 333.\overline{3} \text{ MHz}$$



Q3. Present State      Next State

A \ BC	D <sub>A</sub>	D <sub>B</sub>	D <sub>C</sub>
0 0 0	0	1	0
0 1 0	1	1	1
1 1 1	1	0	0
1 0 0	0	1	1
0 1 1	1	0	1
1 0 1	0	0	0
..			

DA	DB	DC
A \ BC	00 01 11 10	00 01 11 10
0   0 0 X 1 X	0   1 1 X 0 X	0   0 0 X 0 X
1   0 0 X 1 X	1   1 1 X 0 X	1   0 0 X 0 X

$$D_A = B$$

DA	DB	DC
A \ BC	00 01 11 10	00 01 11 10
0   0 0 X 1 X	0   1 1 X 0 X	0   0 0 X 0 X
1   0 0 X 1 X	1   1 1 X 0 X	1   0 0 X 0 X



$$D_B = C'$$

DA	DB	DC
A \ BC	00 01 11 10	00 01 11 10
0   0 0 X 1 1	0   1 1 X 0 X	0   0 0 X 0 X
1   0 0 X 1 X	1   1 1 X 0 X	1   0 0 X 0 X


$$D_C = A'B + AC'$$

ind  
2MMS

st  
mms

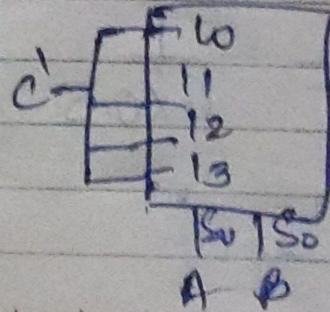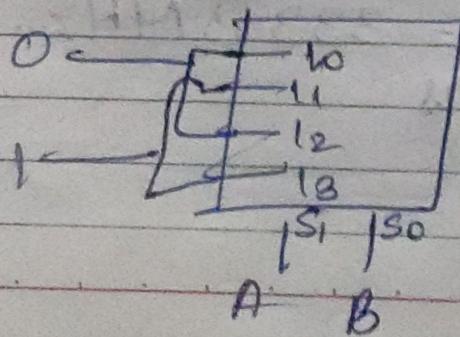

20  
3 MUS

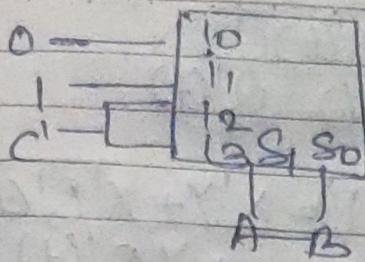


Q4.

a). NOR gates:

$$Q(t+1) = (R\bar{C} + \bar{Q})' = ((R' + C')' + Q)'$$

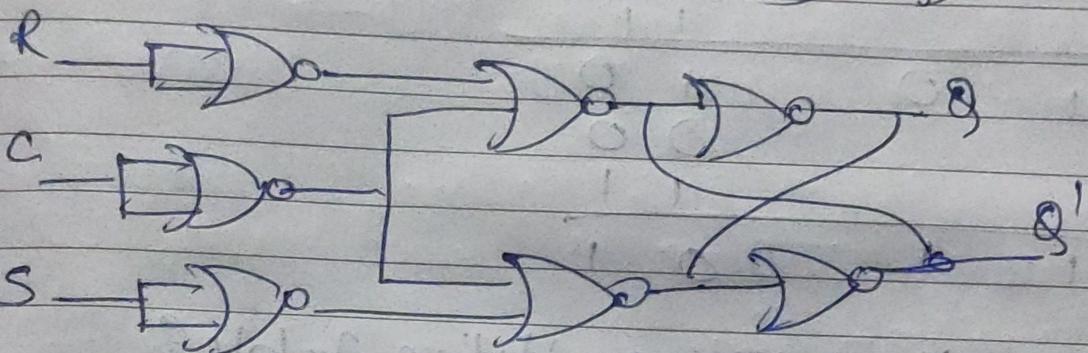
$$Q'(t+1) = (\bar{S}\bar{C} + Q)' = ((S + C')' + Q)'$$



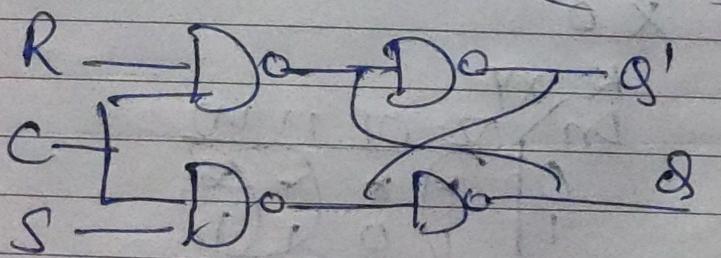
(b) NAND gates

$$Q(t+1) = (R\bar{C} + \bar{Q})' = (R\bar{C})' \cdot Q = (\bar{R}' \cdot \bar{C}') \cdot (\bar{Q})'$$

$$Q'(t+1) = (\bar{S}\bar{C} + Q)' = (\bar{S}\bar{C})' \cdot Q = (S' \cdot C')' \cdot Q$$




(c) AND, OR, Invert gates.

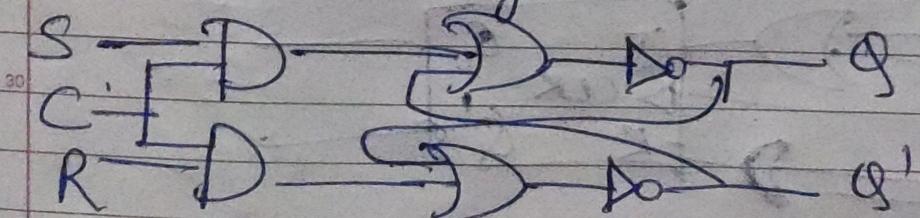

$Q(t)$	$Q(t+1)$
0 0	0 0
0 1	1 0
1 0	0 1
1 1	1 1

$Q(t+1) = Q(t) \oplus X(t)$


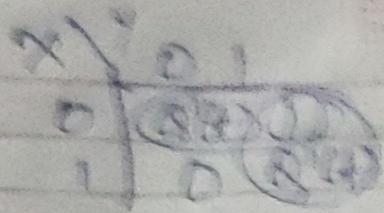


$$Q(t+1) = X \oplus Q(t) \oplus K$$

$Q(t)$	$Q(t+1)$	$X$	$Y$
0 0	0 0	0 0	0 0
0 1	1 0	0 1	0 1
1 0	0 1	0 1	0 1
1 1	1 1	1 1	1 1


(c) JK to XY: JK excitation tables

$Q(t)$	$Q(t+1)$	JK
0 0	0 0	0 X
0 1	1 0	1 X
1 0	0 1	X 1
1 1	X 0	

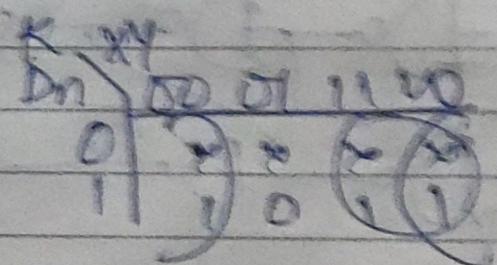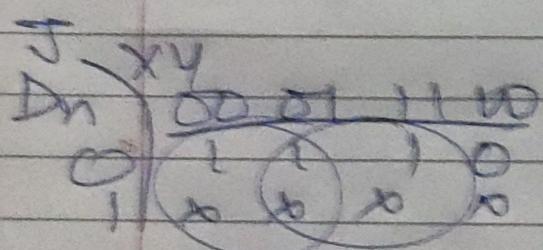

$$J = X \oplus Y$$

$$K = Y' \oplus X$$

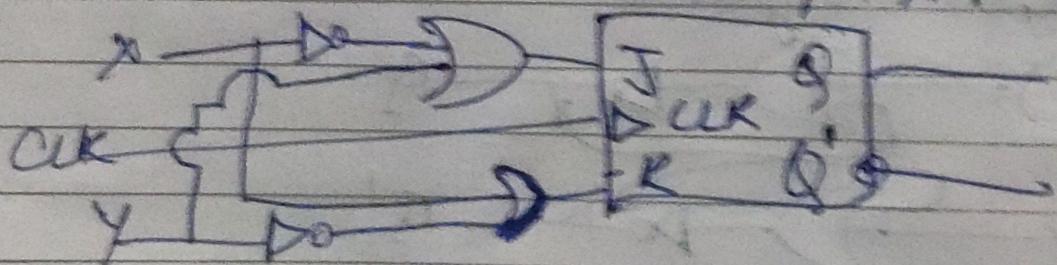


RG(a) 5-8'  
O(g+)

L'Amour des

$$Q(A+D) = J B' + K B = Q'(A').$$

Initially zero, so sequence  
is 10101.

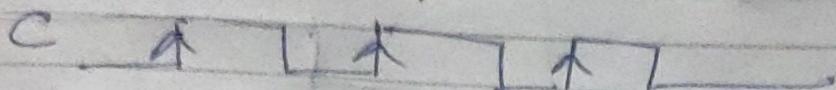(b)  $T=1$ , so output would be complement of given output.



$$Q7. S = (Q \oplus X)', \quad \text{and} \quad R = (Q \oplus X)$$

$$Q(t+1) = S + R'Q(t)$$

$$= (\mathbf{Q} \mathbf{x}' + \mathbf{Q}' \mathbf{x})' + (\mathbf{Q} \dot{\mathbf{x}}' + \mathbf{Q}' \mathbf{x}) \circ \mathbf{Q}.$$

$$= (\varphi x')! \cdot (\varphi' x)' + \varphi x'$$

$$= (Q^1 + x^1) \cdot (Q^2 + x^2) + Q^1 x^2$$


$$= Q'x' + Qx + Qx' = Q'x' + Qx$$

Q8. When clk goes from 0 → 1 and  $x = 0$ ,

$A$  is 1 and  $B = 0$ , so  $Q = 0$ .


when clk goes from 0 → 1 and  $x = 1$

$B=I$ ,  $A=0$  and  $\varrho=1$ .

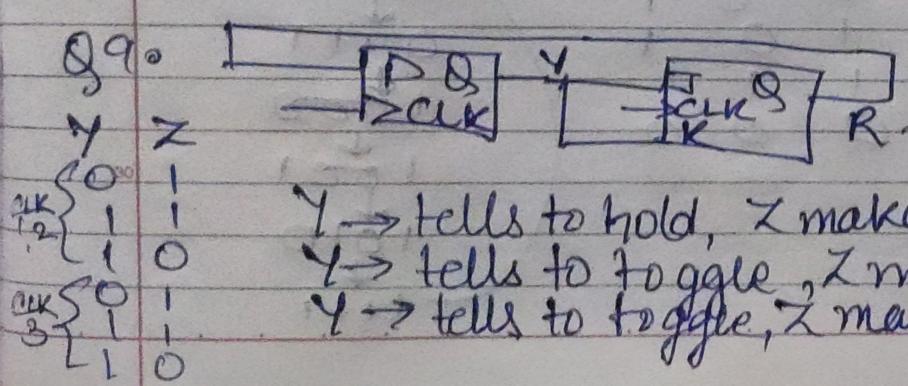


Bit Sequence at Y  
011011011

## 3 flipflops

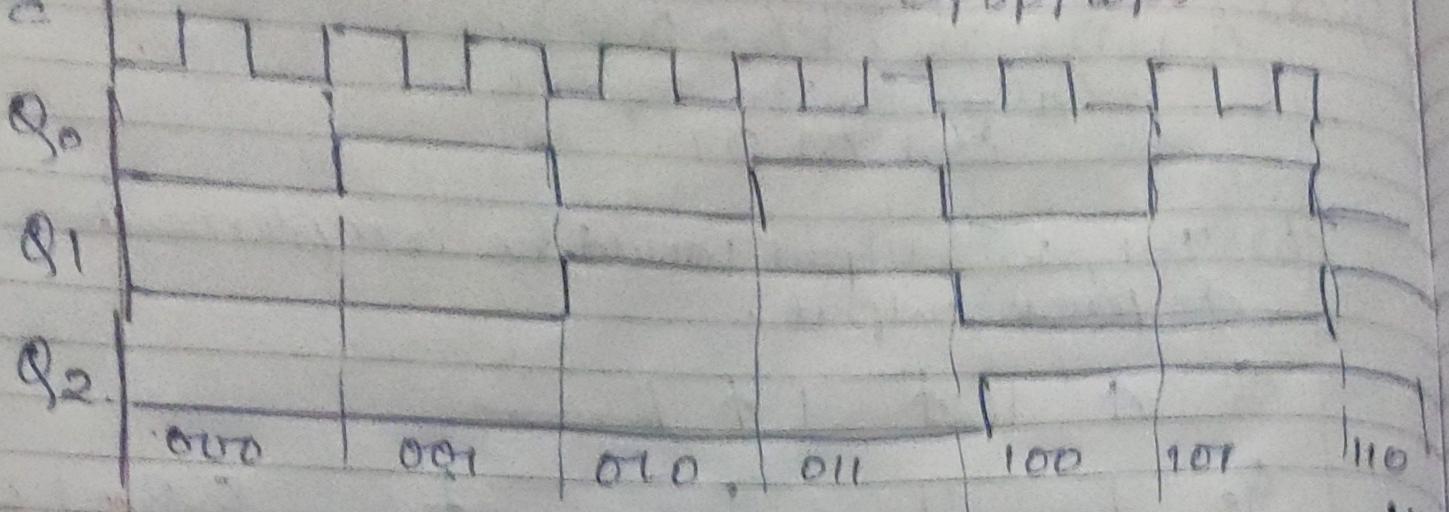

Q<sub>2</sub> Q<sub>1</sub> Q<sub>0</sub>. Starts from 000  $\rightarrow$  111  
and then again 000. Mod value = 8.

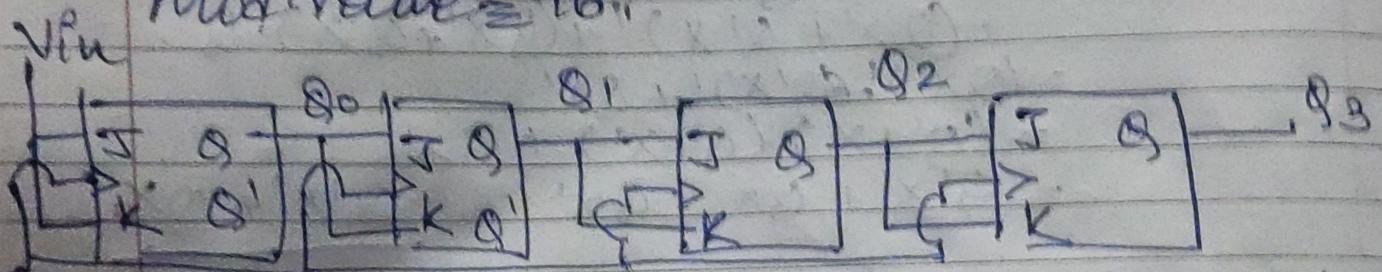Similarly for 4 such flipflop, Circuit will go from 0000  $\rightarrow$  1111 and then 0000.  
Mod value = 16.



	CLK	J, K <sub>1</sub>	Q <sub>0</sub>	Q <sub>1</sub>	Q <sub>2</sub>	Q <sub>3</sub>
1	0	1 1	0	0	0	0
2	1	1 1	1	0	0	0
3	1	1 1	0	1	0	0
4	1	1 1	0	0	1	0
5	1	1 1	1	0	0	1
6	1	1 1	0	1	0	1
7	1	1 1	1	1	1	1
8	1	1 1	0	0	0	0

