

Experiment-1

Buck converter Design document

CONTENTS

S.No	Title	Page No.
1.	SYSTEM UNDER CONSIDERATION	3
2.	KEY BUCK CONVERTER WAVEFORMS	3
3.	VALIDATION OF CCM CONDITION	4
4.	INDUCTANCE CALCULATION	4
5.	CAPACITANCE CHOICE	5
6.	SELECTION OF MOSFET	5
7.	SELECTION OF DIODE	7
8.	DESIGN OF INDUCTOR MAGNETICS	8
7.	TOTAL LOSS AND EFFICIENCY CALCULATION AT RATED LOAD	10
	REFERENCES	10

• SYSTEM UNDER CONSIDERATION:


Let us consider a system:

$$100\text{V} < V_{\text{in}} < 120\text{V V}, P_{\text{out,rated}} = 200\text{ W}, f_{\text{sw}} = 50\text{kHz}, V_{\text{out}} = 48\text{V}.$$

Under a load variation of 20% i.e. ($160\text{W} < P_{\text{out}} < 200\text{W}$), the converter should always be operated under CCM.

Design the system for the worst-case condition considering the above-mentioned criteria such that the inductor current ripple (p-p) *i.e.* $\Delta I_{L(p-p)}$ and capacitor voltage ripple (p-p) *i.e.* ΔV_{Cp-p} should not exceed 30% and 2% respectively for full load condition and find out upto what load the converter will operate in CCM. Consider the non-idealities like R_{dsON} , R_L , V_D and ESR of Capacitance etc.

• KEY BUCK CONVERTER WAVEFORMS :

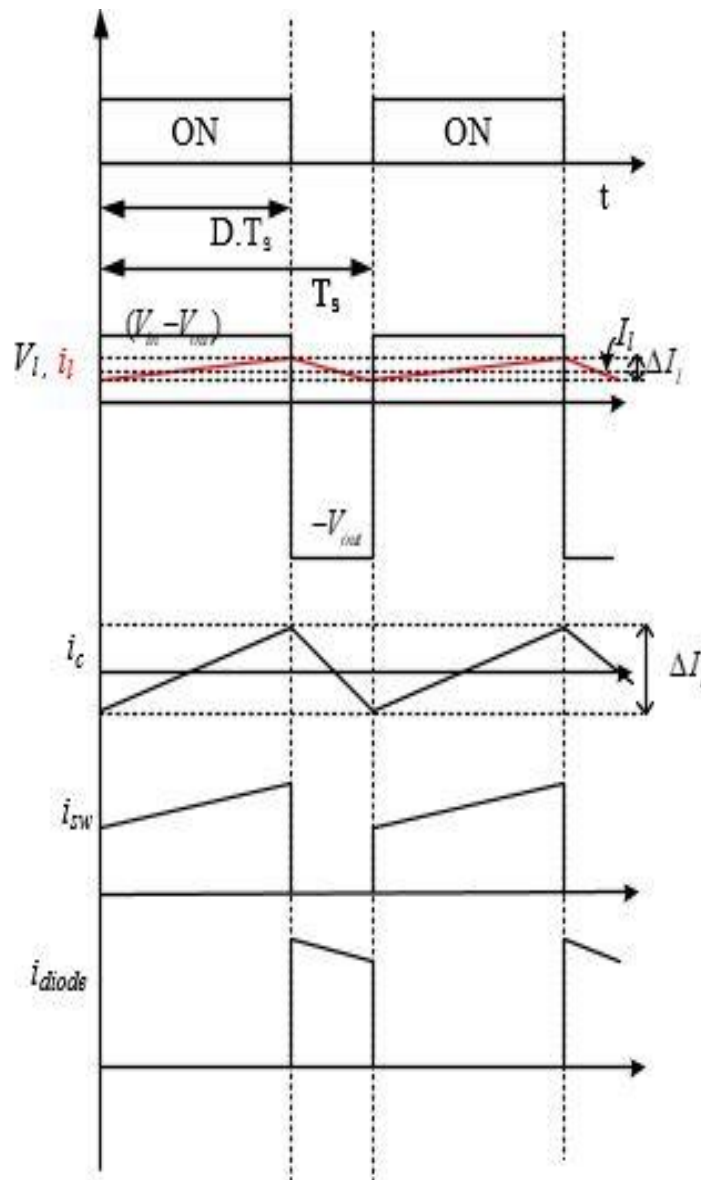

- **Validation of CCM condition:**

$$\frac{\Delta I_L}{2} \leq I_L$$

$$\frac{2L}{RT_s} \geq (1 - D)$$

$$L \geq \frac{(1 - D_{min}) \times R_{max}}{2 \times f_{sw}} = \frac{0.6 \times 14.4}{2 \times 50 \times 1000} = 86.4 \mu H$$

- **Inductance (L) calculation:** In all operating condition the % current ripple should not exceed 30%.

$$\Delta I_L = \frac{V_{out} \cdot (1 - D)}{L f_{sw}}$$

$$\frac{\Delta I_L}{I_L} = \frac{R \cdot (1 - D)}{L f_{sw}}$$

$$\begin{aligned} L &\geq \frac{R_{max}}{f_{sw}} \times (1 - D_{min}) \times \frac{100}{30} \\ &= \frac{14.4}{50 \times 1000} \times 0.6 \times \frac{100}{30} = 576 \mu H \end{aligned}$$

The chosen value of $L = 576 \mu H$. So, as per design the converter is always in CCM. The maximum average current through the converter can be given as-

$$\langle i_L \rangle_{T_s} = I_L = \frac{V_{out}}{R}$$

$$I_{L,max} = \frac{V_{out}}{R_{min}} = \frac{48}{11.52} = 4.17 A$$

The maximum peak current through the inductor is considered as, $i_{L,peak} = I_{L,max} \times 1.3 = 5.421 A$.

- The DCM load condition for the chosen L can be found out as shown below-

$$\frac{2L}{RT_s} \leq (1 - D)$$

$$R \geq \frac{2 \cdot L \cdot f_{sw}}{(1 - D_{max})} = 110.77 \Omega$$

- **Capacitance(C) choice:** In all operating condition output voltage ripple should be less than 2%.

$$\frac{\Delta V_{out}}{V_{out}} = \frac{1}{8} \times \frac{(1-D)}{Lf_{sw}^2} \times \frac{1}{C} \leq \frac{2}{100}$$

$$C \geq \frac{1}{8} \times \frac{(1-D_{min})}{Lf_{sw}^2} \times 50$$

$$= 2.61 \mu F$$

Capacitor current will be maximum when ΔI_L is maximum. Rms capacitor current= 0.3A, Peak-Peak ripple current =1A, Average capacitor voltage= 48V.

- Conductive Polymer Hybrid Aluminum Electrolytic Capacitors (standard product: EEHZA1H100R) has been chosen.
- Rated Voltage =63V.
- Capacitance (C) = $10\mu F$.
- ESR= 120 m Ω .
- Max. ripple current(rms) =1000mA.
- Data Sheet:
http://www.farnell.com/datasheets/2842914.pdf?_ga=2.100048157.249828137.1600968886-1009838117.1593006503

SELECTION OF MOSFET:

Blocking Voltage= 120V. Average switch current can be expressed as-

$$\langle i_{sw} \rangle_{T_s} = D \cdot I_L = D \cdot \frac{V_o}{R_{min}}$$

$$\langle i_{sw} \rangle_{T_s, max} = \frac{0.48 \times 48}{11.52} = 2A$$

Maximum switch current= 5.421A (during transients).

- **BSC12DN20NS3G** is chosen as a MOSFET switch.
- Blocking voltage = 200 V.
- Max. drain current @100⁰ C = 8A.
- R_{ds,on} (at 100⁰C and I_d = 6A, for V_{gs} =10V) = 188 m Ω .
- C_{gd1} = 5 pF, C_{gd2} = 55 pF.
- Gate driver voltage (V_{dr})=10V and gate resistance (R_g) = 10 Ω .
- Current rise time (t_{ri}) = 4ns.
- Current fall time (t_{fi}) = 3ns.
- @150⁰C, V_{gs1} =4V and I_{d1} = 3.75A, V_{gs2} =5V and I_{d2} = 15A

$$V_{th} = \frac{V_{gs1}\sqrt{I_{d2}} - V_{gs2}\sqrt{I_{d1}}}{\sqrt{I_{d2}} - \sqrt{I_{d1}}} = 3V$$

$$k = \frac{I_{d1}}{(V_{gs1} - V_{th})^2} = 3.75$$

$$V_{gs,miller} = V_{th} + \sqrt{\frac{I_{load}}{k}} = 4.05V$$

$$V_{adj} = (100 - 150) \times (-0.007) = +0.35V$$

$$V_{plateau} = V_{gs,miller} + V_{adj} = 4.4V$$

- Average voltage fall time (t_{fv}) can be expressed as-

$$t_{fv} = (V_d - I_d R_{ds,on}) \times \frac{R_g}{(V_{dr} - V_{plateau})} \times \frac{(C_{gd1} + C_{gd2})}{2} = 6.4ns$$

- Average voltage rise time (t_{rv}) can be expressed as-

$$t_{rv} = (V_d - I_d R_{ds,on}) \times \frac{R_g}{V_{plateau}} \times \frac{(C_{gd1} + C_{gd2})}{2} = 8.12ns$$

- Average Switching loss can be expressed as-


$$P_{sw} = \frac{f_{sw}}{2} \times V_{block} I_{load} \times [(t_{ri} + t_{fv}) + (t_{fi} + t_{rv})] = 0.27W$$

- Conduction loss in switch, $P_{conduction} = I_{load}^2 R_{ds,on} = 3.269W$
- Total loss in switch, $P_{loss,sw} = 3.269 + 0.27 = 3.54W$

Data sheet: https://www.infineon.com/dgdl/Infineon-BSC12DN20NS3-DS-v02_02-en.pdf?fileId=db3a30432ad629a6012b146334d419ec

Heat Sink designing:

- Transient thermal impedance junction to case (@ 50 kHz and D=0.48) = 1.3K/W.
- Junction temp. rise w.r.t case = $P_{loss} \times Z_{thc} = 4.6K = 4.6C$
- Let ambient temp. be 40⁰ C and allowable junction temp. 100⁰ C.
- Max. heat sink thermal impedance (Z_a) = $\frac{T_c - T_a}{P_{loss,sw}} = \frac{95.4 - 40}{3.4} = 15.64^0C/W$.
- Selected heat sink thermal impedance(case to impedance): **3.2⁰C/W (1.625" wide × 12" flatback heatsink)**
- Case temp. rise w.r.t ambient with selected heatsink = $P_{loss} \times Z_a = 11.328^0C$
- Junction Temp. = 40 + 11.328 + 4.6 = 55.91⁰C. Hence junction temp. is well within operating temp. of selected MOSFET.

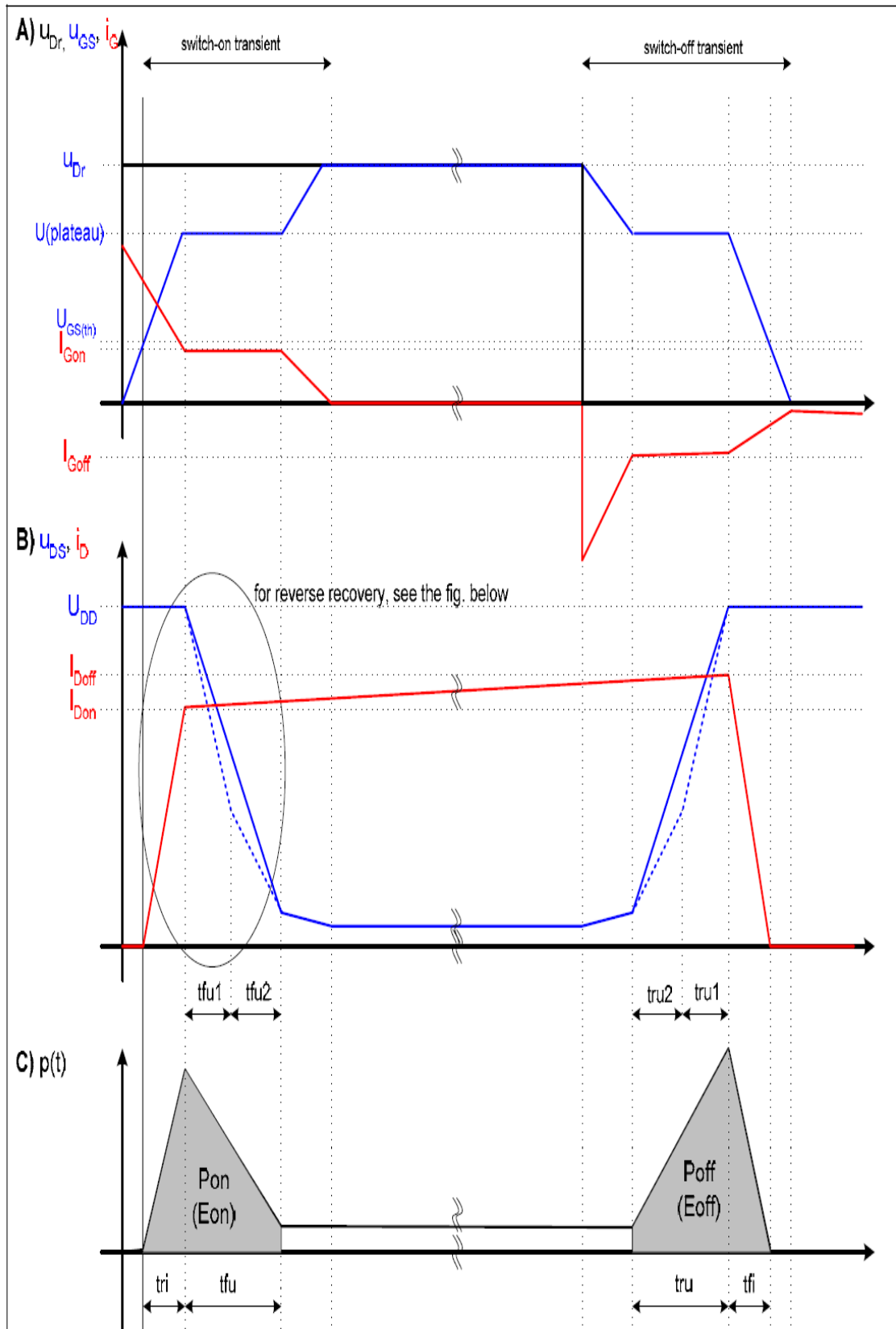

SELECTION OF DIODE:

Blocking Voltage= 120V, Average maximum diode current can be expressed as-

$$\langle i_D \rangle_{T_s} = (1 - D) \cdot I_L = \frac{(1 - D_{min}) \cdot V_{out}}{R_{min}}$$

$$\langle i_D \rangle_{T_s, max} = \frac{0.6 \times 48}{11.52} = 2.5A$$

Maximum diode current= 5.421A (during transients).

- **Schottky diode DSTF10200C** has been chosen for the above mentioned buck converter.
- Peak inverse voltage 200V
- Average forward current per leg (@ 90°C) = 5A
- Forward voltage drop (@ 125°C and 3A) = 0.6V.
- Reverse leakage current (@ 125°C and 120V blocking voltage) = 0.1 mA.
- Conduction loss in diode = $2.5 \times 0.6 = 1.5W$.
- Reverse leakage loss in the diode = $200 \times 0.1 \times 10^{-3} \times 0.6 = 0.012W$
- Total loss in diode, $P_{loss,D} = 1.5 + 0.012 = 1.512W$
- Data Sheet:

https://m.littelfuse.com/~media/electronics/datasheets/power_semiconductors/littelfuse_power_semiconductor_schottky_diode_dstf10200c_datasheet.pdf.pdf

Heat Sink Design:

- Thermal impedance Junction to case per diode = $7^{\circ}C/W$
- Junction temp. rise w.r.t case = $P_{loss,D} \times Z_{thc} = 10.58^{\circ}C$
- Let ambient temp. be 40°C and allowable junction temp. 100°C.
- Max. heat sink thermal impedance (Z_a) = $\frac{T_c - T_a}{P_{loss,sw}} = \frac{95.58 - 40}{3.4} = 32.68^{\circ}C/W$.
- Selected heat sink thermal impedance(case to impedance): **3.2°C/W (1.625" wide × 12" flatback heatsink)**
- Case temp. rise w.r.t ambient with selected heatsink = $P_{loss} \times Z_a = 4.838^{\circ}C$
- Junction Temp. = $40 + 4.838 + 10.58 = 55.4^{\circ}C$. Hence junction temp. is well within operating temp. of selected Diode.

• DESIGN OF INDUCTOR MAGNETICS:

Inductance(L)	576 μH
I _p	5.421A
I _{rms}	4.17A
B _m	0.2 wb/m ²
J(initial)	3A/mm ²
K _w (initial)	0.3

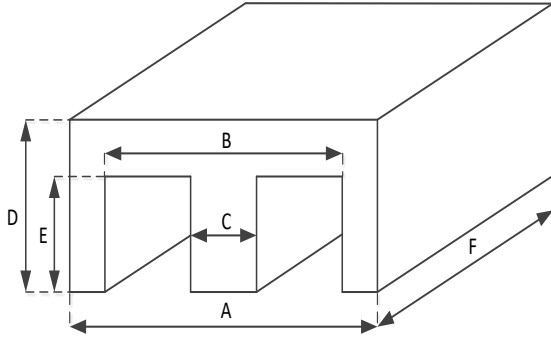


Fig.: E – core

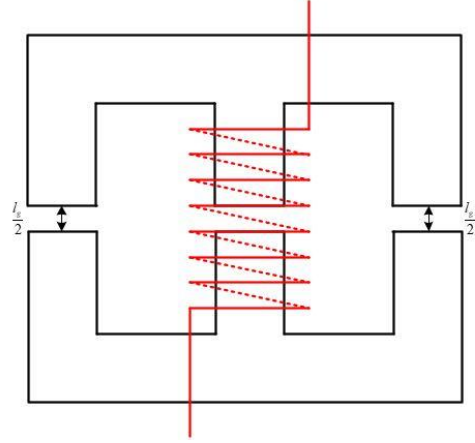


Fig.: Inductor Winding on EE core

Area Product,

$$\begin{aligned}
 A_c A_w &= \frac{L \cdot I_p \cdot I_{rms}}{K_w \cdot B_m \cdot J} \\
 &= \frac{576 \times 10^{-6} \times 5.421 \times 4.17}{0.3 \times 0.2 \times 3} \times 10^6 \\
 &= 72337.8 \text{ mm}^4
 \end{aligned}$$

Selected Core:

E 56/24/19 , $A_c = 364.81 \text{ mm}^2$, $A_w = 271.7 \text{ mm}^2$, $C = 19.1 \text{ mm}$ $F = 19.1 \text{ mm}$

- Number of turns(N) can be found as-

$$N = \frac{L \cdot I_p}{B_m \cdot A_c} = \frac{576 \times 10^{-6} \times 5.421}{0.2 \times 364.81 \times 10^{-6}} \approx 43$$

- Calculated wire size, $a_w = \frac{I_{rms}}{J} = 1.39 \text{ mm}^2$
- From wire table, the chosen wire is SWG 17.
- Updated wire size, $a_w^* = 1.589 \text{ mm}^2$.
- Updated current density, $J^* = \frac{I_{rms}}{a_w^*} = 2.624 \text{ A/mm}^2$.
- Updated winding factor, $K_w^* = \frac{N \times a_w^*}{A_w} \approx 0.251$
- Air gap length, $l_g = \frac{N^2 \cdot A_c \cdot \mu_0}{L} = 1.47 \text{ mm} \ll \sqrt{A_c}$
- Average length of each turn of coil = $2 \times (C + F) = 76.4 \text{ mm}$
- Average length of inductor coil = $N \times 76.4 = 3285.2 \text{ mm} = 3.28 \text{ m}$
- Coil resistance of inductor = $\frac{10.85}{1000} \times 3.28 = 35.64 \text{ m}\Omega$.
- Updated area product: $A_c A_w = 98858.57 \text{ mm}^4$

• **TOTAL LOSS AND EFFICIENCY CALCULATION AT RATED LOAD:**

$$\text{Total Power Loss} = 0.0108\text{W} + 3.54\text{W} + 1.512\text{W} + 0.619\text{W} = 5.68\text{W}$$

$$\text{Full load efficiency of Buck converter} = \frac{\text{Output Power}}{\text{Output Power} + \text{Losses}} * 100\% = \frac{200}{205.68} * 100 = 97.2\%$$

REFERENCES

1. Dr. Dušan Graovac , Marco Pürschel, and Andreas Kiep ,“*MOSFET Power Losses Calculation Using the Data-Sheet Parameters*”, Application Note, V 1.1, July 2006, by infenion
2. “*Calculation of reverse losses in a power diode, AN4021*” Application Note by ST Microelectronics.
3. V. Ramanarayanan, “Course Material on Switched Mode Power Conversion”, Department of Electrical Engineering Indian Institute of Science Bangalore 560012, second edition 2006.