


Assignment 2.

Mansi Uniyal, 19EE10039.

Date _____

Page _____

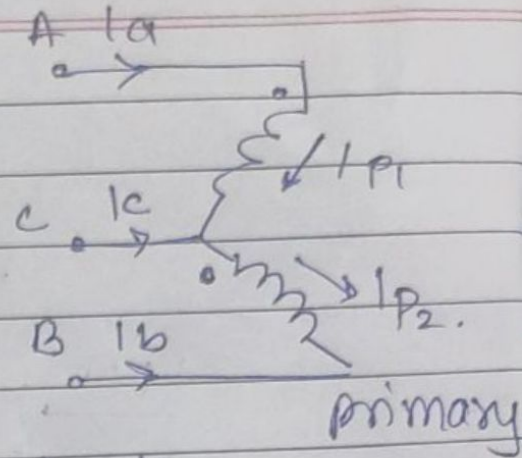- Q1. 3 phase V connected transformer 6600V (L-L)
50Hz supply voltage
star connected 415V (L-L)
load with $(8+6j)\Omega$ /phase load.
Impedance.



$V_{AB} \rightarrow$ reference.

$$V_{AB} = 6600 \angle 0^\circ \text{ V}$$


$$V_{BC} = 6600 \angle -120^\circ \text{ V}$$

$$V_{CA} = 6600 \angle 120^\circ \text{ V}$$

$$V_{ab} = 415 \angle 0^\circ \text{ V}$$

$$V_{bc} = 415 \angle -120^\circ \text{ V}$$
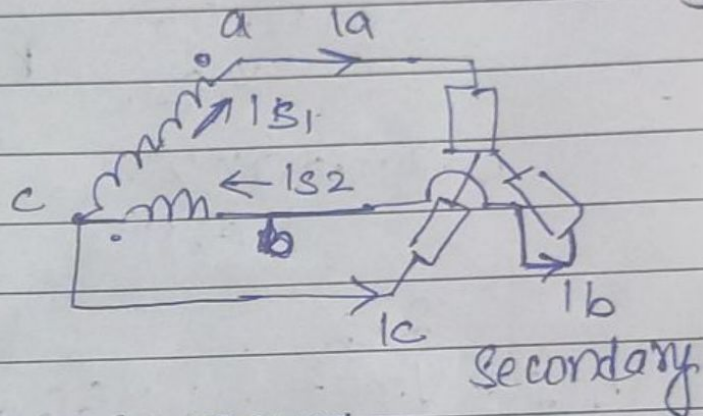
$$V_{ca} = 415 \angle 120^\circ \text{ V}$$



$$6600 : 415 \\ \Rightarrow 15.903 : 1$$

$$V_{an} = 415/\sqrt{3} \angle -30^\circ \text{ V}$$

$$V_{bn} = 415/\sqrt{3} \angle -150^\circ \text{ V}$$

$$V_{cn} = 415/\sqrt{3} \angle 90^\circ \text{ V}$$

$$I_a = \frac{V_{an}}{Z} = \frac{415/\sqrt{3} \angle -30^\circ}{8+6j} \\ = 23.96 \angle -66.86^\circ \text{ A}$$

$$I_b = \frac{V_{bn}}{Z} = \frac{415/\sqrt{3} \angle -150^\circ}{8+6j} \\ = 23.96 \angle -173.13^\circ \text{ A}$$

Phase currents in secondary of transformer

$$(i) \quad I_{S1} = I_a = 23.96 \angle -66.86^\circ \text{ A}$$

$$I_{S2} = -I_b = 23.96 \angle 6.87^\circ \text{ A}$$

primary side currents in transformer.

$$I_{P1} = \frac{415}{6600} * (23.96 \angle -66.86^\circ)$$

$$I_{P1} = 1.5 \angle -66.86^\circ \text{ A}$$

$$I_{P2} = \frac{415}{6600} * (23.96 \angle -6.87^\circ)$$



$$I_{P2} = 1.5 \angle -6.87^\circ \text{ A}$$

$$(ii) \text{ power} = \sqrt{3} V_L I_L \cos \theta$$

$$= \sqrt{3} * 415 * 23.96 * \cos(-30 + 66.86)$$

$$\text{Power} = \underline{13.78 \text{ KW}}$$

(iii)

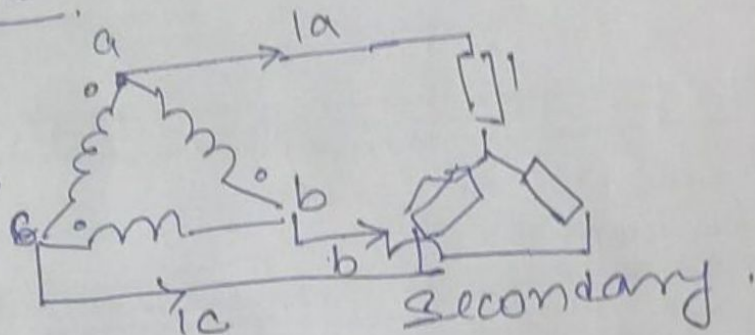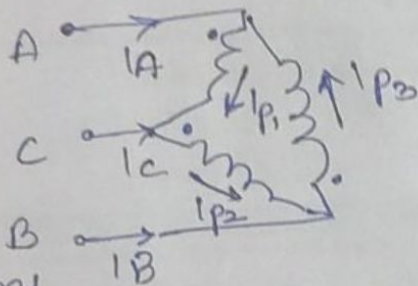

primary

$$V_{AB} = 6600 \angle 0^\circ \text{ V}$$

$$V_{BC} = 6600 \angle -120^\circ \text{ V}$$

$$V_{CA} = 6600 \angle 120^\circ \text{ V}$$

$$V_{ab} = 415 \angle 0^\circ \text{ V}$$

$$V_{bc} = 415 \angle -120^\circ \text{ V}$$

$$V_{ca} = 415 \angle 120^\circ \text{ V}$$

$$V_{an} = 415/\sqrt{3} \angle -30^\circ \text{ V}$$

$$V_{bn} = 415/\sqrt{3} \angle -150^\circ \text{ V}$$

$$V_{cn} = 415/\sqrt{3} \angle 90^\circ \text{ V}$$

$$I_a = 23.96 \angle -66.86^\circ \text{ A}$$

$$I_b = 23.96 \angle 173.13^\circ \text{ A}$$


$$I_c = 23.96 \angle 53.13^\circ \text{ A}$$

$$I_{S1} - I_{S3} = I_a$$

$$I_{S2} - I_{S1} = I_c$$

$$I_{S3} - I_{S2} = I_b$$

$$|I_{S1}| = |I_{S2}| = |I_{S3}|$$

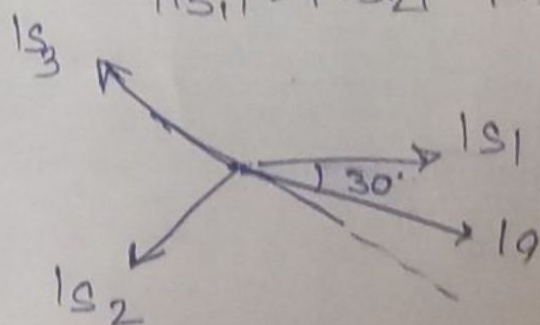

$$I_a = \sqrt{3} I_{s1} \angle -30^\circ$$

$$\text{or } I_{s1} = \frac{1}{\sqrt{3}} I_a \angle 30^\circ$$

$$I_{s1} = 13.83 \angle -26.86^\circ \text{ A}$$

$$I_{s2} = \frac{1}{\sqrt{3}} I_a \angle 30^\circ = 13.83 \angle 83.13^\circ \text{ A}$$

$$I_{s3} = \frac{1}{\sqrt{3}} I_a \angle 30^\circ = 13.83 \angle -156.87^\circ \text{ A}$$

} secondary phase currents


$$I_{p1} = 0.87 \angle -26.86^\circ \text{ A}$$

$$I_{p2} = 0.87 \angle 86.13^\circ \text{ A}$$


$$I_{p3} = 0.87 \angle -156.87^\circ \text{ A}$$

} primary phase currents

Phasor for V connected transformer:

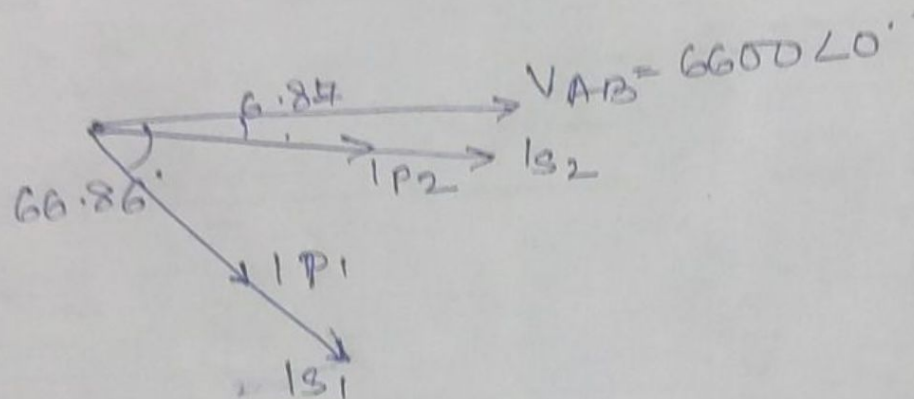

Phasors for Δ-Δ transformer:

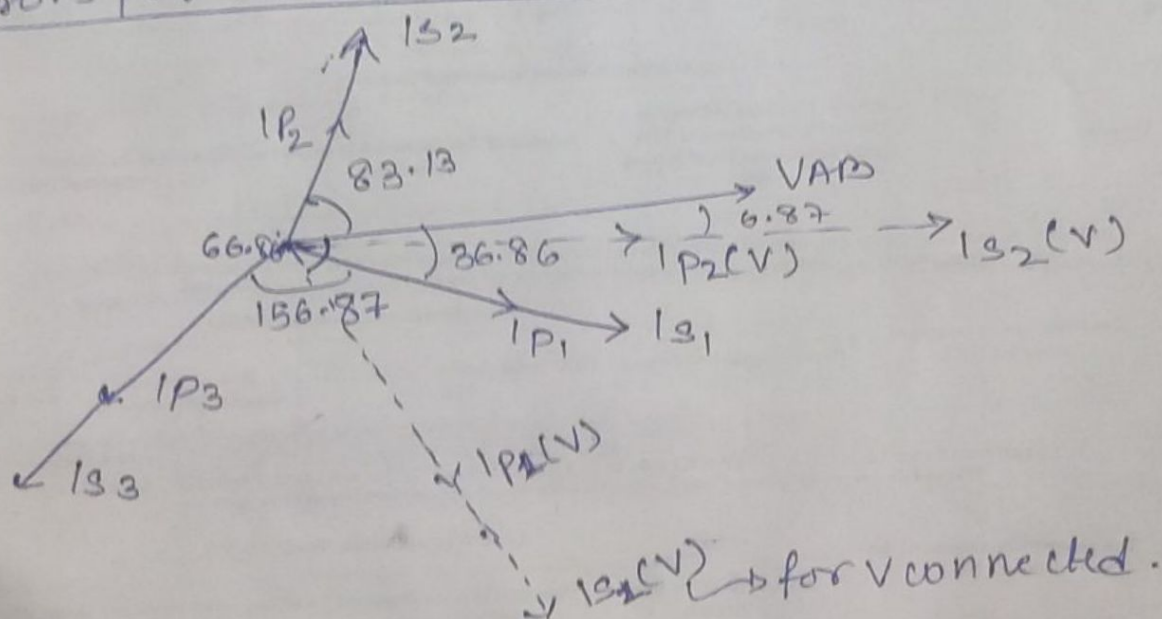

Q2 Scott connected transformer

415 V (L-L)
3 phase 50 Hz → two 120 V
50 Hz 1 phase supply

S_{P1} leads S_{P2} by 90°

load on $S_{P1} = 400 \text{ kW}$ at 0.8 pf

load on $S_{P2} = 900 \text{ kW}$ at 1 pf (lag)

V_{AB} → reference.

$$V_{AB} = 415 \angle 0^\circ \text{ V}$$

$$V_{BC} = 415 \angle -120^\circ \text{ V}$$

$$V_{CA} = 415 \angle 120^\circ \text{ V}$$

$$|V_{AO}| = \frac{\sqrt{3}}{2} 415$$

$$V_{AO} = \frac{\sqrt{3}}{2} 415 \angle -30^\circ \text{ V} = 359.4 \angle -30^\circ \text{ V}$$

$$V_{AO} = n_1 V_{AO}$$

$$V_{bc} = n_2 V_{BC}$$

$$n_1 = \frac{V_{AO}}{V_{AO}} = \frac{120}{359.4} = 0.333$$

$$n_2 = \frac{V_{bc}}{V_{BC}} = \frac{120}{415} = 0.289$$

$$I_{AO} = \frac{400 \times 10^3}{120 \times 0.8} \angle -30^\circ - 36.85^\circ = 4166.67 \text{ A} \angle -66.85^\circ$$

$$I_{bc} = \frac{900 \times 10^3}{120 \times 1} \angle -120^\circ = 7500 \text{ A} \angle -120^\circ$$

Line currents are:

$$I_{AO} = n_1 I_{AO} = 1.37 \angle -66.85^\circ \text{ kA} = I_{L1}$$

$$I_{BC} = n_2 I_{bc} = 2.167 \angle -120^\circ \text{ kA}$$

$$I_{L3} = I_{BC} - I_{AO}/2 = 1.83 \angle -137.33^\circ \text{ kA}$$

$$I_{L2} = -I_{BC} - I_{AO}/2 = 2.63 \angle 72^\circ \text{ kA}$$

$$\left\{ \begin{array}{l} I_{L1} = 1.37 \angle -66.85^\circ \text{ kA} \\ I_{L2} = 2.63 \angle 72^\circ \text{ kA} \\ I_{L3} = 1.83 \angle -137.33^\circ \text{ kA} \end{array} \right\} \text{Line currents.}$$

