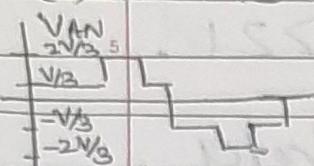


Tutorial

Mansi Uniyal.

- Q1. Star connected Resistive load of  $15\ \Omega/\text{phase}$ ,  
 420V DC source via 3phase full bridge source

(a)  $180^\circ$  conduction.(i) RMS (load current) =  $13.18\ A$ .

$$i_{AN} = \frac{V_{AN}}{R_{load}} = \frac{1}{15} \sqrt{\left(\frac{V}{3}\right)^2 + 4 \times \left(\frac{V}{3}\right)^2 + \left(\frac{V}{3}\right)^2} \times 2 = \sqrt{3} \times 13.18 = 13.18\ A$$

(ii) RMS (switch current) =  $9.32\ A$ .

$$(i s)_sw = \frac{V}{45} \times \frac{1}{\sqrt{2}} A = 9.32\ A$$

(iii) Load power = ~~70.883 kW~~  $0.00021\ kW$ .

$$\langle V_{dc} i_{AN} \rangle = 3 \langle i_{AN}^2 R \rangle = 3R \langle i_{AN}^2 \rangle = 15 \times (13.18)^2 = 3 \times 2605.69 = 78.4\ kW$$

(iv) Avg (source current) =  $6.22\ A$ .

$$V_{dc}(i_s)_{avg} = 2613.6 ; (i_s)_{avg} = 6.22\ A$$

(b)  $120^\circ$  conduction.(i) RMS (load current) =  $11.43\ A$ .

$$i_{AN} = \frac{V_{AN}}{R_{load}} = \frac{1}{15} \sqrt{\frac{V^2}{4} \times \frac{2}{3}} = \frac{V}{15\sqrt{6}} = 11.43\ A$$

(ii) RMS (switch current) =  $6.6\ A$ .

$$(i s)_{avg} = \frac{i_{AN}}{2\sqrt{3}} \times \frac{1}{\sqrt{3}} = 6.6\ A$$

(iii) Load power =  $5.88\ kW$ .

$$3 \times 15 \times 11.43^2 = 5.879\ kW$$


(iv)  $(i_s)_{avg} = \frac{P}{V_{dc}} = \frac{5.88 \times 10^3}{420} = 13.997\ A$ .

Q2 (a)

180° conduction

(2)

$$V = L \frac{di}{dt}$$

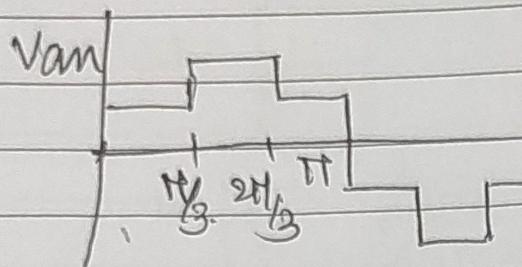

$$\frac{di}{dt} = \frac{V}{L} = \frac{V}{3L}$$

+ ε(0)

$$\Delta i = \frac{V}{3L} \Delta t = \frac{V}{3L} \times \frac{\pi}{3\omega}$$

$$i\left(\frac{\pi}{3\omega}\right) - i(0) = \frac{V\pi}{3\omega L}$$

$$\frac{di}{dt} = \frac{2V}{3L}$$

$$+ \epsilon\left(R_B, \frac{2\pi}{3\omega}, \frac{3\omega}{3\omega}\right)$$

$$\Delta i = \frac{2V}{3L} \times \frac{\pi}{3\omega}$$

$$i\left(\frac{2\pi}{3\omega}\right) = \frac{2V\pi}{3\omega L} + \frac{V\pi}{3\omega L} + i(0)$$

$$i(\pi) = \frac{2V\pi}{3\omega L} + \frac{2V\pi}{3\omega L} + i(0)$$

$$\therefore i_{\text{peak}} = \frac{2V\pi}{3\omega L} = \frac{28.64 A}{3\omega L}$$

Q3 - 3phase sinusoidal PWM inverter  
DC link 500V.

Modulation index = 0.8.

RMS (fundamental line-line Voltage).

$$V_{dc} = 500 \text{ V}$$


$$M_a = 0.8$$

$$V_{\text{line-line}} = \frac{1}{2} \sqrt{3} M_a V_{dc} = 0.612 \times 0.8 \times 500$$

Ans

$$V_{\text{line-line}} = 244.8 \text{ V}$$

Q4.

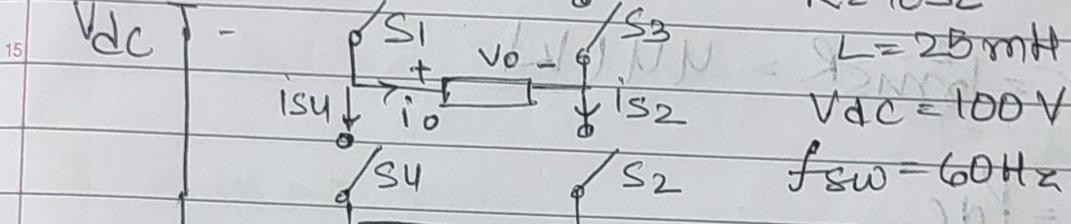

$$R = 10 \Omega$$

$$T = Y_f = 0.0167 \text{ s.}$$

$$L = 25 \text{ mH}$$

$$V_{dc} = 100 \text{ V}$$

$$f_{sw} = 60 \text{ Hz.}$$

(a) load current.

$$Q4. \tau = L/R = \frac{0.025}{10} = 2.5 \times 10^{-3}$$

(4)

$$T = Y_p = 0.0167$$

$$(a) I_{min} = -I_{max}$$

$$I_{max} = \frac{V_{dc}}{R} \left( \frac{1 - e^{-T/2\tau}}{1 + e^{-T/2\tau}} \right)$$

$$= 10 \left( \frac{1 - e^{-3.33}}{1 + e^{-3.33}} \right) = 9.31 A.$$

$$I_{min} = -I_{max} = -9.31 A.$$

$$i_o(t) = 10 + (-9.31 \div 10) e^{-t/0.0025}$$

$$= 10 - 19.31 e^{-t/2.5 \times 10^{-3}}$$

for  $t \in [0, Y_{120}]$ .

$$\begin{cases} -10 + 19.31 e^{-t+0.00835/0.0025} \\ \end{cases}$$

for  $t \in [Y_{120}, Y_{60}]$

Q6. (a) Sq wave op. d = 90°

$$V_{O1} = \frac{4V_s}{\sqrt{2}\pi} = 207.10V.$$

$$Z_{O1} = \sqrt{10^2 + (2\pi \times 50 \times 0.03)^2} = 13.74 \Omega.$$

$$I_{O1} = \frac{V_{O1}}{Z_{O1}} = 15.07A.$$

$$\begin{aligned} \text{Power} &= V_{O1} I_{O1} \cos \theta = 88 \\ &= 207.10 \times 15.07 \times 0.48 = \underline{\underline{3058.57W}} \end{aligned}$$


(b) quasi square output.

$$2d = 0.5 \times 180^\circ \quad d = 45^\circ.$$

$$V_{O1} = \frac{4V_s}{\sqrt{2}\pi} \sin \phi = 146.43V.$$

$$Z_{O1} = 13.74 \Omega. \quad I_{O1} = 10.65A.$$
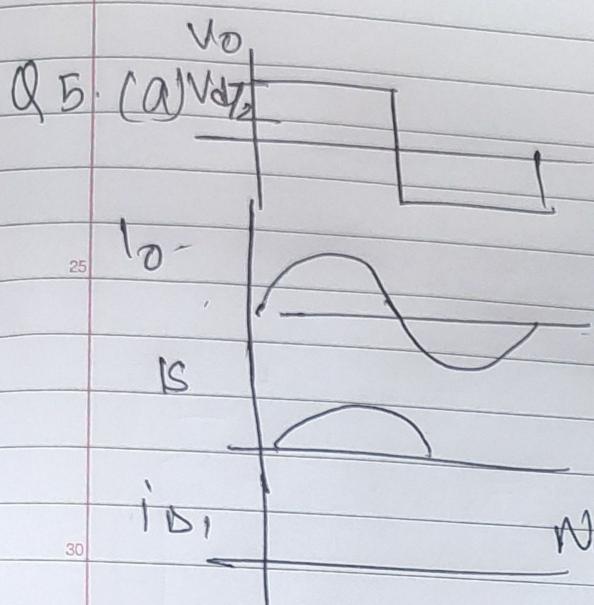
$$\begin{aligned} \text{Power} &= V_{O1} I_{O1} \cos \theta = 148.43 \times 10.65 \times 0.98 \\ &= 1528.3W. \end{aligned}$$



(b)

$$P = I_{rms}^2 R = \left(\frac{13.2}{\sqrt{2}}\right)^2 \times 2$$

$$= 5.36 \text{ kW}$$

(c) for high switching freq., forced communication may be required

No current