
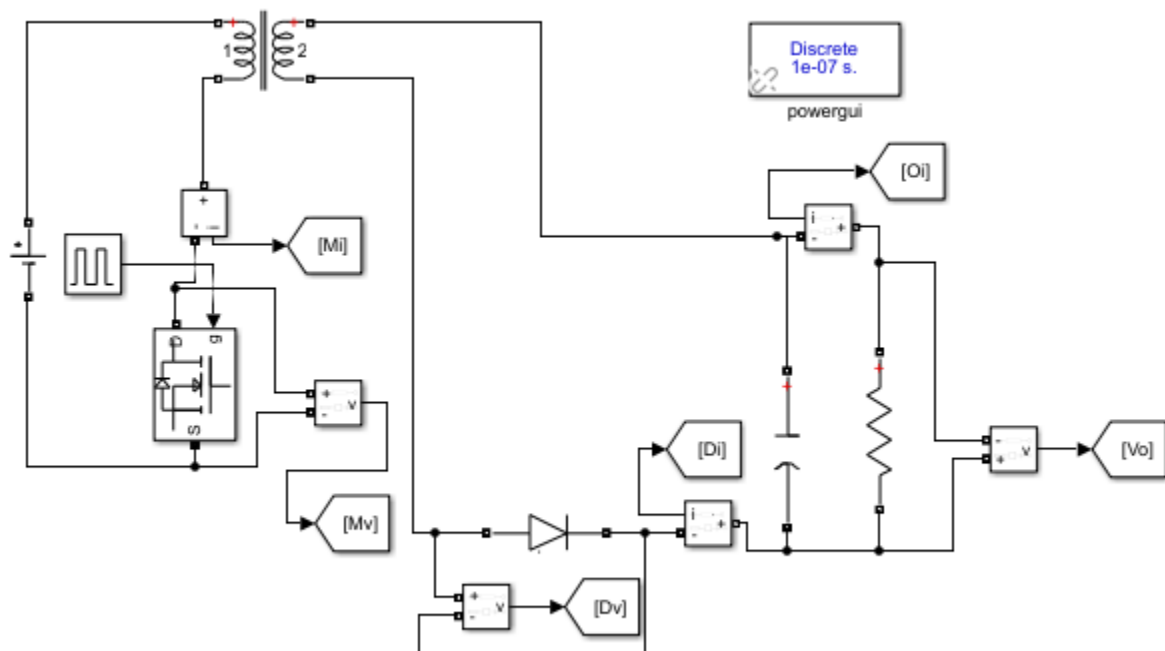



PART A:

1. The turn ratio=3:1

2.

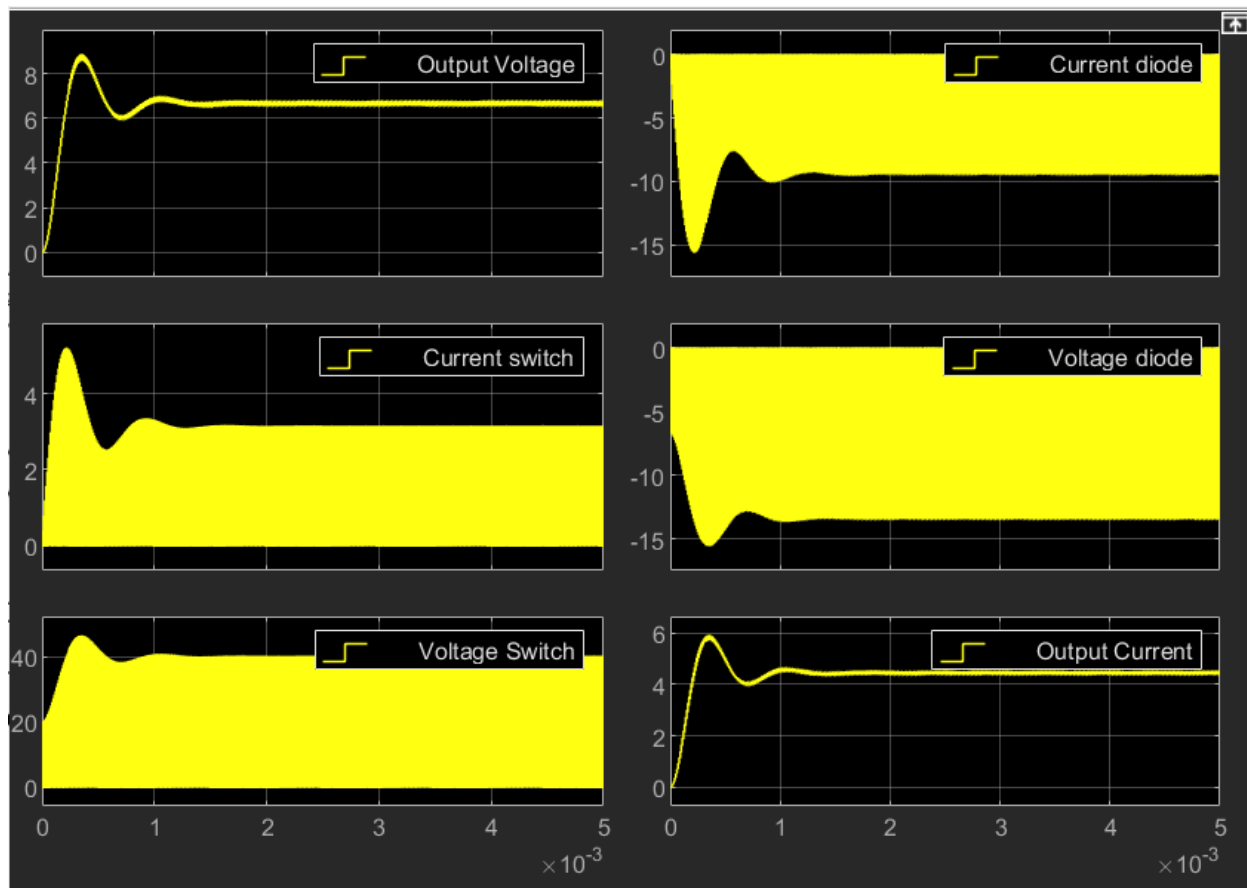



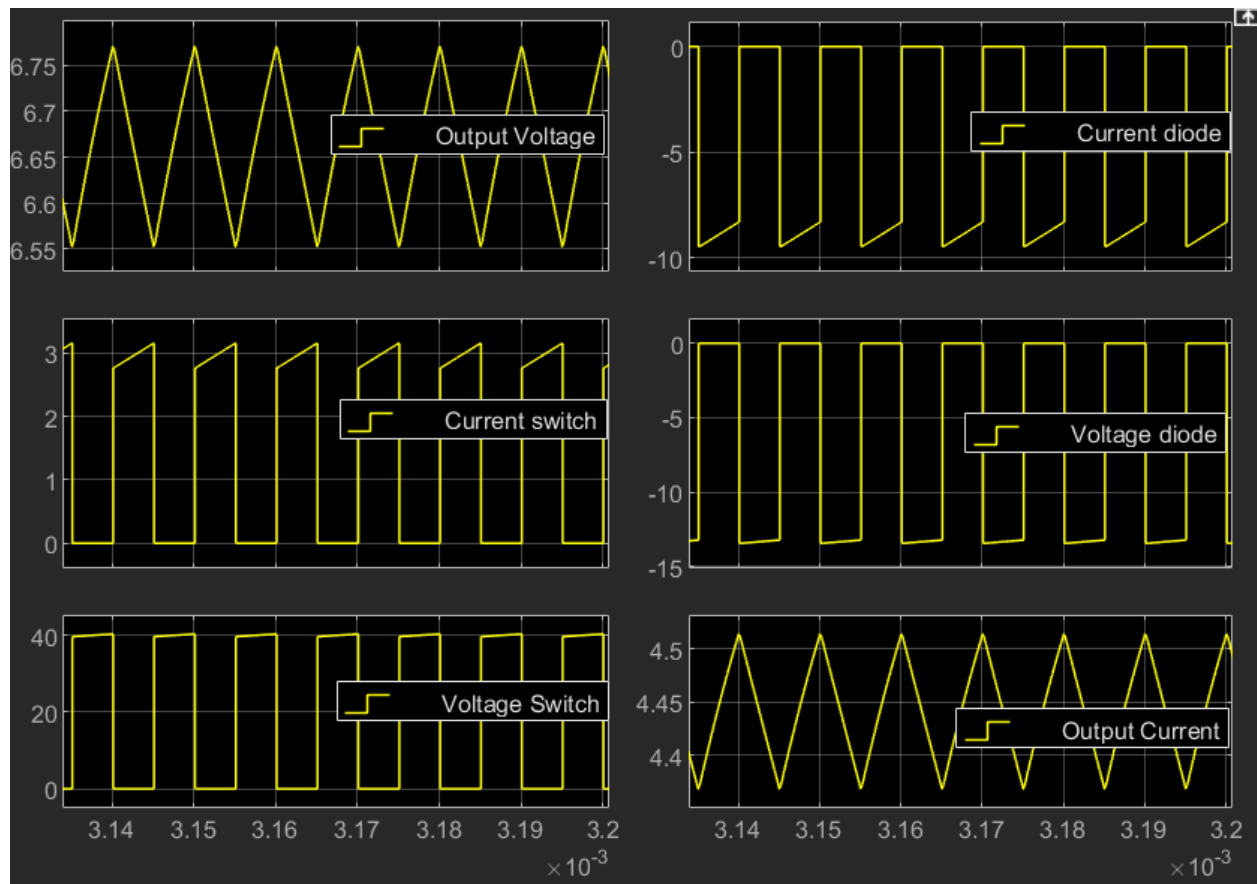

$I_{rms} = 3.961$ A diode current

$I_{rms} = 1.096$ A switch current

$V_{rms} = 7.396$ V diode voltage



$V_{rms} = 25.82$ V switch voltage


$V_{rms} = 4.44$ V output voltage

3. The input voltage is varied from 15 V to 20 V (in steps of 1 V) with a fixed load resistance of 15 Ω , and a fixed duty ratio of 45%.

4. $V_{in} = 18$ V, and duty ratio of 45 %.

PART B:

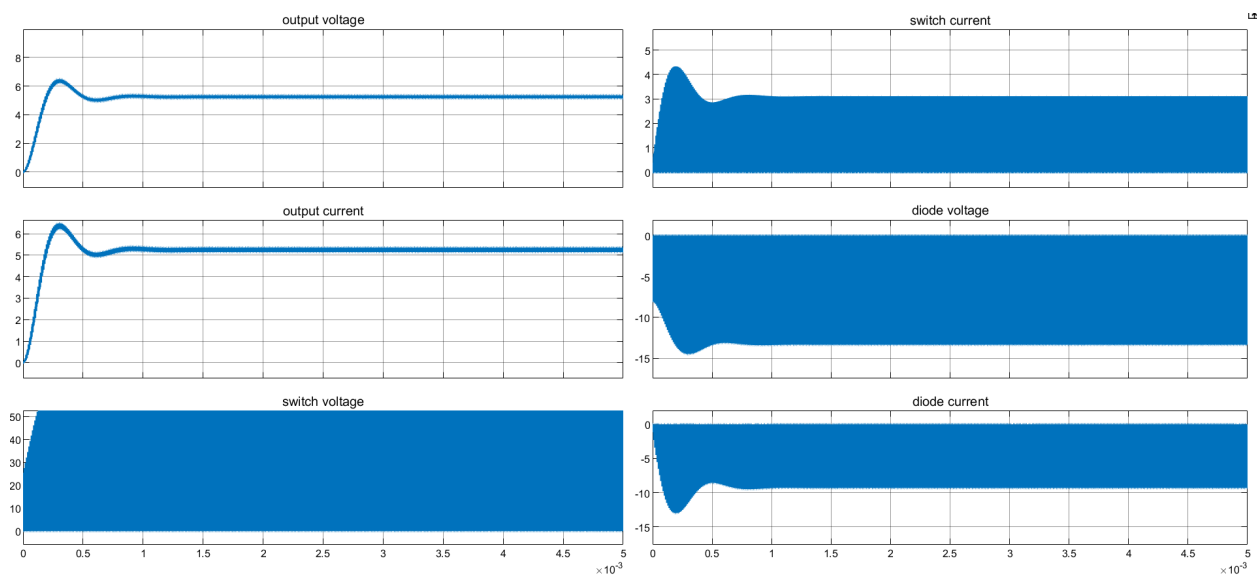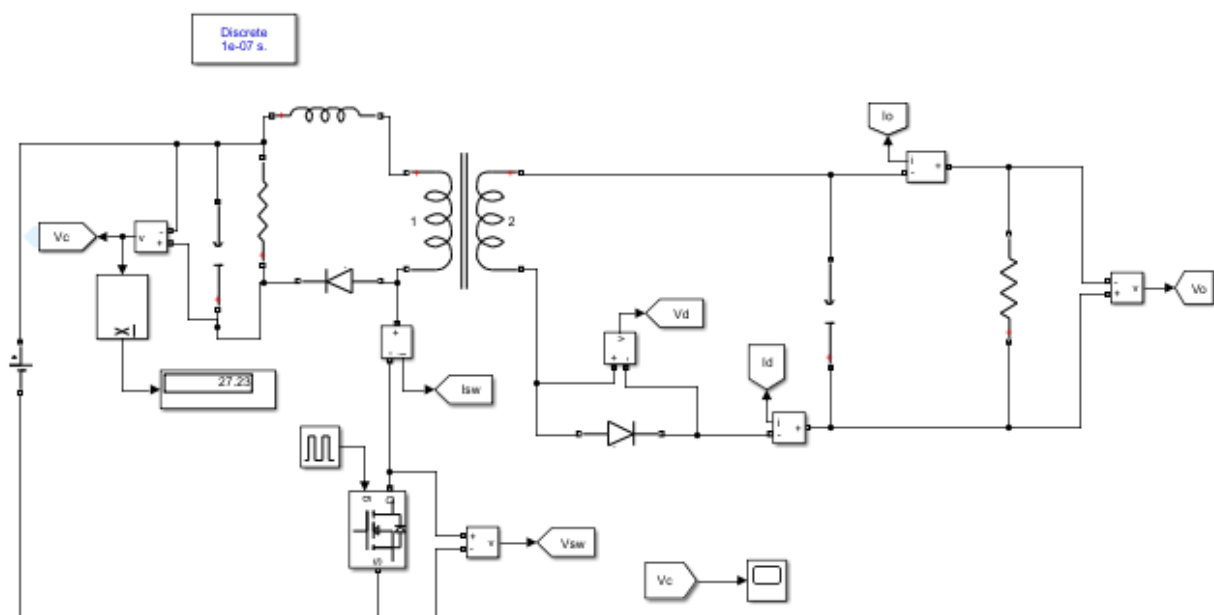

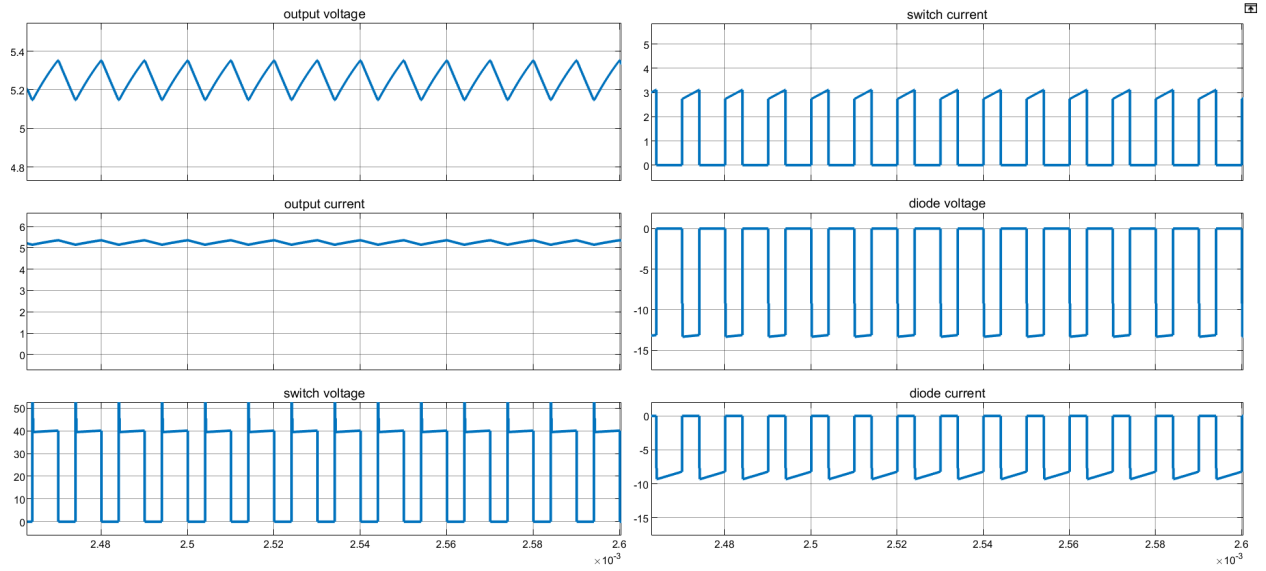

Snubber capacitor voltage 27.36V

$$\text{Power} = 27.36^2 / 5000 = 0.1497$$