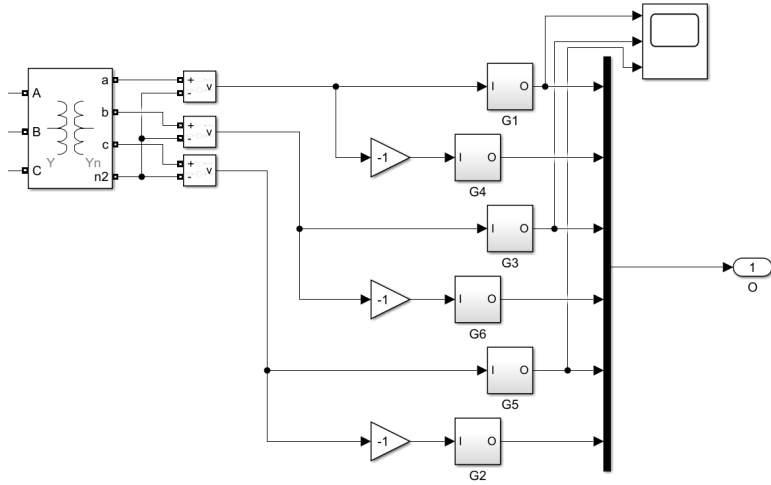



**Mansi Uniyal**  
**19EE10039**

## PART - A

### Triggering Circuit:




**G1:**

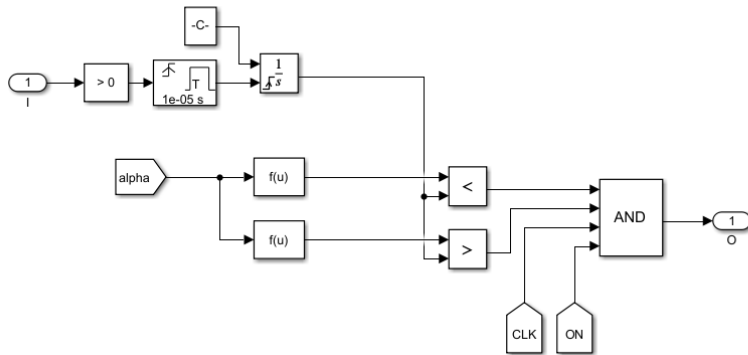

## PART - B

**Circuit Diagram:**

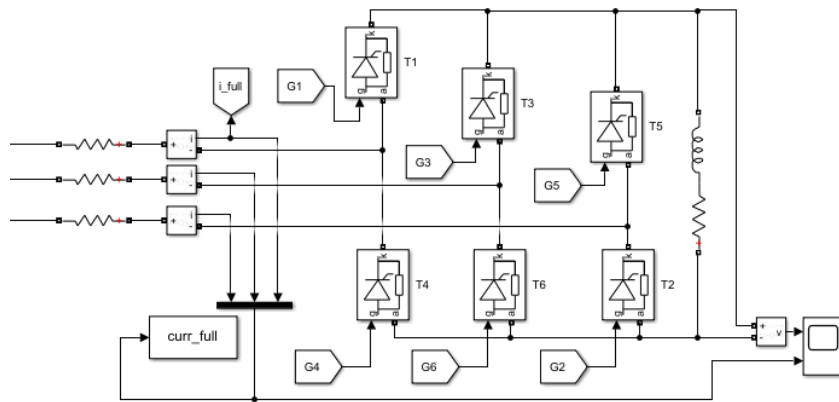

1.

$$V_{rect} = (3 \cdot \sqrt{3} / \pi) \cdot V_m \cdot \cos(a)$$

$$I_{d,R} = (3 \cdot \sqrt{3} / \pi) \cdot V_m \cdot \cos(a)$$


$$I_d = 5A$$

$$a = 0$$

$$V_m = 220 \cdot \sqrt{2/3}$$

$$5 \cdot R = 220 \cdot \sqrt{2/3} \cdot (3 \cdot \sqrt{3} / \pi) \cdot \cos(0)$$

$$R = 59.42 \text{ ohm}$$

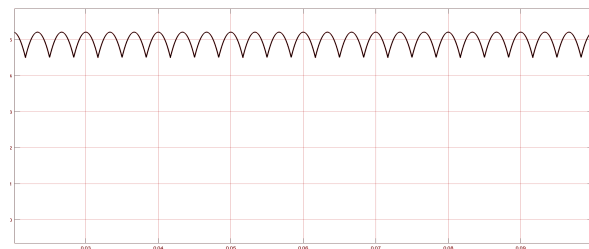

Average load current = 4.972 A

2.


$$V_{rect} = (3 \cdot \sqrt{2} / \pi) \cdot 220 \cdot \cos(a) = 220$$

$$\cos(a) = \pi / (3 \cdot \sqrt{2}) = 0.7405$$

$$a = 42.23 \text{ deg}$$


3.

Output Voltage:

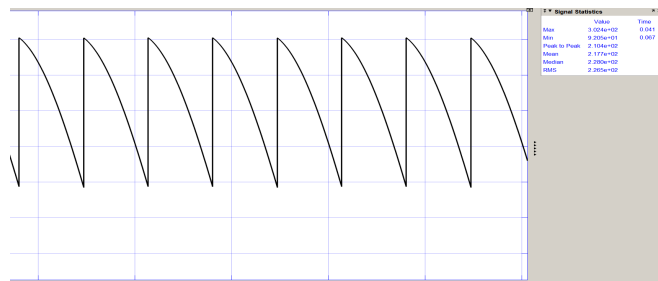

Average output voltage = 217.7 V


AC side currents:

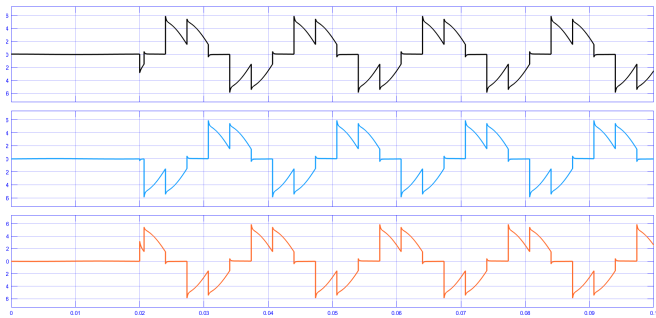

4.  
 $R = 59.421\ \Omega$


Alpha (degree)	Average output Voltage (V)	AC side current (RMS) (A)
0	295.5	4.06
15	284.8	3.93
30	255.2	3.57
45	208.54	3.00
60	146.3	2.30
75	87.32	1.57
90	39.20	0.87

5.

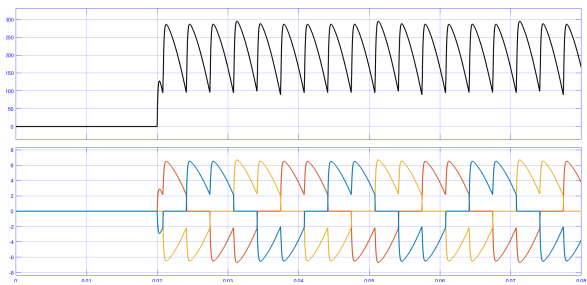

PART - C

Circuit Diagram:

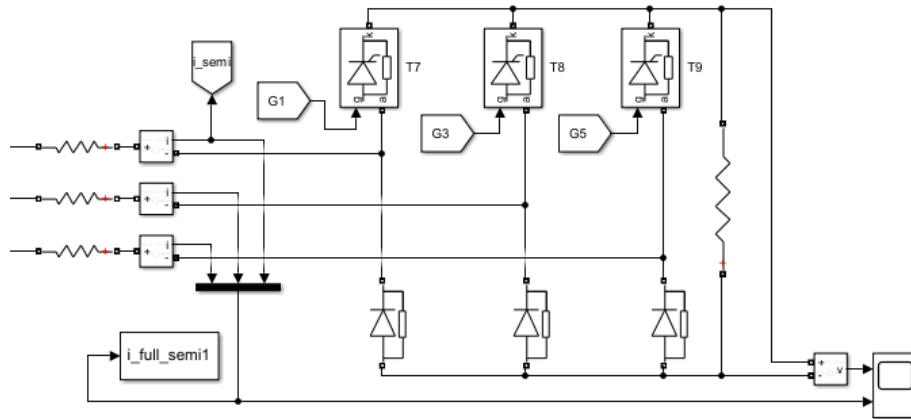

1.

$$V_{\text{rect}} = \left( \frac{3 \sqrt{3}}{2\pi} \right) V_m (1 + \cos(\alpha)) = I_d R$$


$$I_d = 5 \text{ A}$$

$$\alpha = 30^\circ$$

$$V_m = 220 \sqrt{\frac{2}{3}}$$

$$5R = \left( \frac{3 \sqrt{3}}{2\pi} \right) 220 \sqrt{\frac{2}{3}} (1 + \cos(\alpha))$$


$$R = 55.44 \text{ ohm}$$

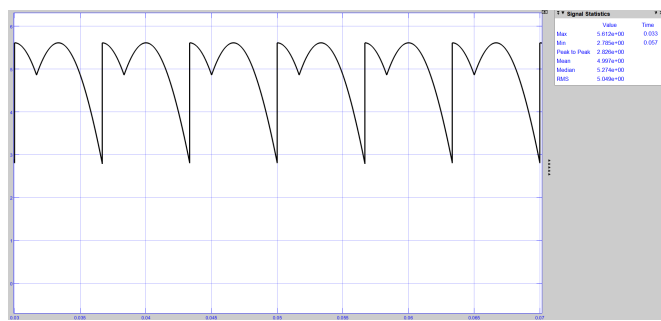


Average Load current = 4.997 A

2.


Load current at  $\alpha = 59^\circ$

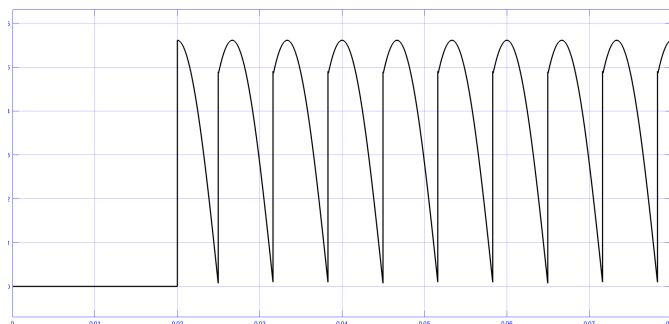

Load current at  $\alpha = 60^\circ$

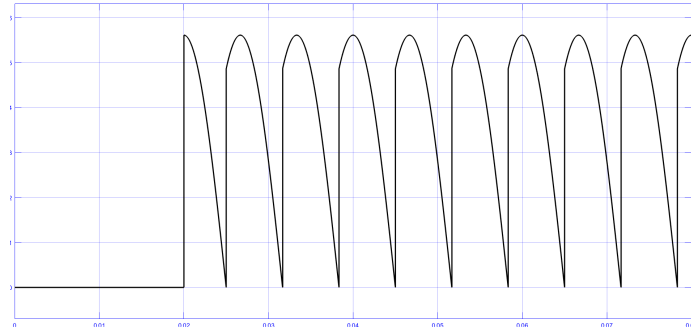


Load current at  $\alpha = 61^\circ$

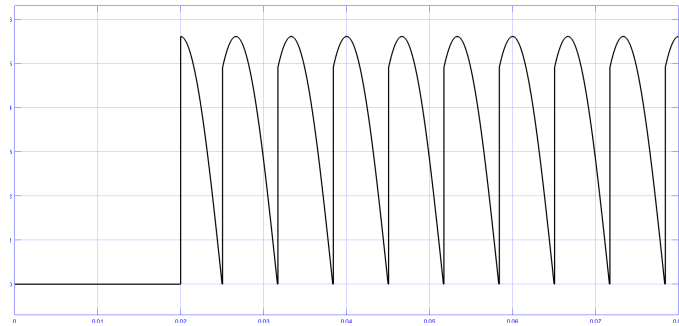

Hence, the load current becomes discontinuous as soon as it crosses  $\alpha = 60^\circ$

3.

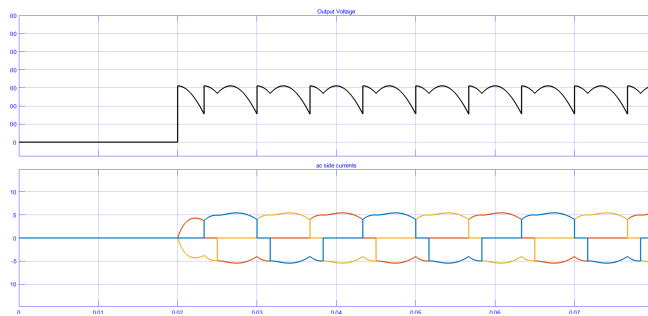

Average output voltage = 277.1 V

4.

$R = 55.44 \, \Omega$

Alpha (degree)	Average output Voltage (V)	AC side current (RMS) (A)
0	296.8	4.31
15	292.1	4.23
30	277.3	4.01
45	254.3	3.68
60	223.1	3.28

75	185.2	2.86
90	148.0	2.42

## PART - D

Parameter	Full-controlled Converter	Semi-controlled Converter
AC side currents (RMS)	4.08	4.08
Fundamental component of the AC side currents (RMS)	3.89	3.86
THD (%) of the AC side currents	31.13	34.10
Input power factor	0.922	0.913
Fundamental active power (W)	2025.60	2009.41
Fundamental reactive power (VAr)	542.7	538.4

## Discussion Questions:

1. Consider an ideal three-phase full-controlled converter with an R load. Obtain the expression of the average output voltage (for  $\alpha \in [0, \pi/2]$ ).

Avg output voltage of ideal 3 phase fully controlled converter with R load:


(i)  $\alpha$  in  $[0, \pi/3]$

$$V_{\text{rect}} = \frac{3}{\pi} \int_{\alpha + \pi/6}^{\alpha + \pi/2} \sqrt{3} V_m \sin(\omega t + (\pi/6)) \dots \text{from limit } \alpha + \pi/6 \text{ to } \alpha + \pi/2 \\ = 3\sqrt{3} V_m \cos(\alpha) / \pi$$

(ii)  $\alpha$  in  $[\pi/6, \pi/2]$

$$V_{\text{rect}} = \frac{3}{\pi} \int_{\alpha + \pi/6}^{\pi} \sqrt{3} V_m \sin(\omega t + (\pi/6)) \dots \text{from limit } \alpha + \pi/6 \text{ to } \pi \\ = 3\sqrt{3} V_m \cos(\alpha + \pi/3) / \pi$$

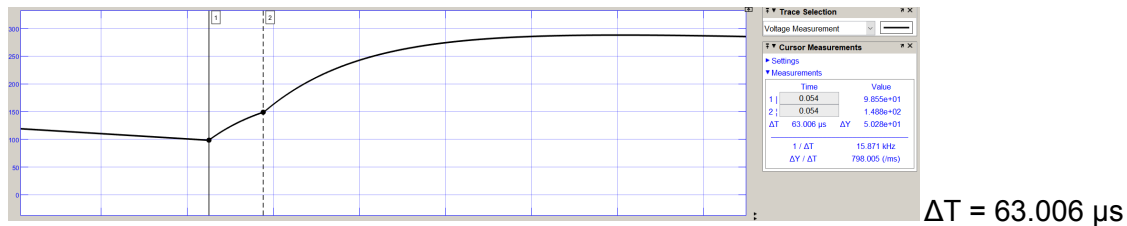2. Refer to Part B(5), what is the commutation overlap angle  $\mu$ ? What is the average output DC voltage?



Commutation overlap angle =  $(63.01 \times 10^{-3} / 3.33) \times 180 \text{ deg} = 3.41 \text{ deg}$

Average DC voltage = 212.1 V

3. Refer to Part D, compare the distortion factor of the two converters. Why is the distortion factor less in the case of the semi-controlled rectifier?

Distortion factor of three-phase fully controlled AC to DC converter =  $I_1/I = (3/\pi) = 0.955$

Distortion factor of three-phase semi-controlled AC to DC converter =  $I_1/I = \sqrt{(6/\pi(\pi-a))} \times \cos(a/2) = 0.807$  for  $a = \pi/12$ .

For a semi-controlled rectifier, the diodes allow more harmonics in the output. That is why the distortion factor is less for semi-controlled AC to DC converter.